


\$1.00

*hr*

focus  
on  
communications  
technology ...

# *ham* **radio** *magazine*

SEPTEMBER 1975

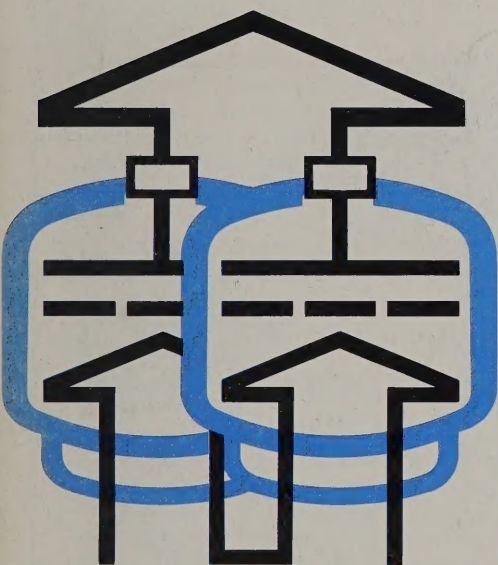

*inductively-tuned*  
**six-meter  
kilowatt**

## *this month*


- RTTY terminal unit 22
- ssb speech splatter 28
- 432-MHz power amplifier 36
- hand-held touch-tone 44
- vhf mobile antenna 54

# QUALITY & PRICE

## CUSHCRAFT ANTENNAS OFFER YOU BOTH

Don't be misled by our prices . . . they are based on experience, large quantity buying of materials, great engineering and efficient office personnel. We are happy hams trying to hold the line on prices for you. So . . . why pay more when you can get the best for less!

### FM 2 METER ANTENNAS

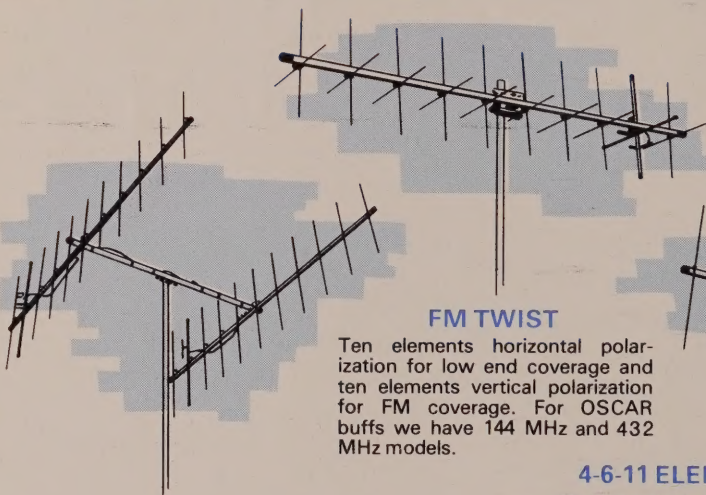

#### POWER PACK

The big signal (22 element array) for 2 meter FM uses two A147-11 yagis with a horizontal mounting boom, coaxial harness and all hardware.

#### FM TWIST

Ten elements horizontal polarization for low end coverage and ten elements vertical polarization for FM coverage. For OSCAR buffs we have 144 MHz and 432 MHz models.

#### 4-6-11 ELEMENT YAGIS

The standard of comparison in VHF-UHF communications, now cut for FM and vertical polarization. There are models covering the 450 MHz, 220 MHz and 147 MHz bands. All are rated at 1000 watts with direct 52 ohm feed and PL-259 connectors.

IN STOCK WITH YOUR LOCAL DISTRIBUTOR



621 HAYWARD ST., MANCHESTER, N. H. 03103



# in the last five years E.T.O. has introduced a// these advances in linear amplifier design:


1. Full kilowatt 'locked-key-continuous' capability in self-contained desk-top cabinet.
2. Rugged, highly-linear, ceramic grounded-grid triode tube(s).
3. Ducted-air cooling with rear intake and exhaust to keep cabinet cool, noise and dirt intake to a minimum.
4. Thermally-controlled, whisper-quiet computer-grade centrifugal blower.
5. Electronic bias control for minimal power waste, lowest heat generation.
6. Full CW break-in capability with integral electronic T/R switch.
7. Complete 10 through 160 meter coverage.
8. Vacuum tuning for precise resetability, quick bandchange, hi-band efficiency.
9. No-tune-up instant bandchange even at maximum-legal-power level.
10. Plug-in power transformer with tape-wound Hipersil® core for efficiency, shipping & handling convenience.
11. 'Toropad'® - suspended shipping pack.
12. Full coverage 160 through 6 meters.
13. Metering of peak power input.
14. LED instant drive level indication.
15. Grid-current-derived, amplified I<sub>Z</sub>-output ALC.
16. Easy-access, modular extruded aluminum cabinet.
17. Six and two meter coverage with a full continuous kilowatt (2+ KW PEP) dc input capability in all modes.
18. Improved vacuum relay/solid state QSK (break-in) system to preserve the full capability of high-performance receivers.
19. ??? Coming soon . . .

These features, so far as we know, are still not available in any competitive linear amplifier at any price: 1, 3, 4, 5, 6, 7, 9, 10, 11, 12, 13, 14, 15, 17, 18!

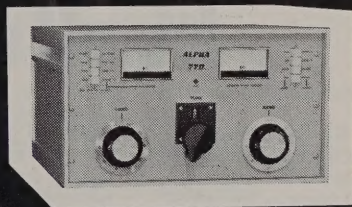
**WHY NOT PUT ONE OF THESE SUPERB ALPHA MAXIMUM-LEGAL-POWER LINEAR AMPLIFIERS IN YOUR STATION NOW — FOR A BETTER SIGNAL AND GREATER OPERATING ENJOYMENT THIS SEASON AND IN THE YEARS AHEAD?**



**The 'NO-TUNE-UP' ALPHA 374 . . . Features 1, 2, 3, 5, 9, 10, 11, 13, 14, 15, 16.**  
**\$1295**



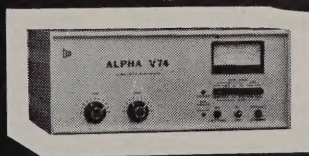**'THE ULTIMATE' ALPHA 77D — Features 1, 2, 3, 4, 5, 8, 10, 11, 12, 13, 14, 15, 16, 18 . . . AND the knowledge that you own the most advanced linear amplifier available.**  
**\$2695**



**The new VHF ALPHA V74 — Six and two meter 'cool kilowatt' offered by popular request. Features 1, 2, 3, 10, 11, 14, 15, 16, 17. A full kilowatt FM/FSK input requires just 20 watts drive; 2 KW PEP highly-linear SSB only 35 watts PEP drive.**  
**\$1195**



**EHRHORN TECHNOLOGICAL OPERATIONS, INC.**  
**BROOKSVILLE, FLORIDA 33512**  
**(904) 596-3711**



# For the best RTTY, you need all the help you can get.



## It's all right here.

The HAL ST-6 terminal unit has been hailed by experienced RTTY amateurs. Its immunity to interference and noise is the talk of the RTTY world as the best in the business. In fact, we built it to highest standards — but kept the price in a range that you can afford.

The features of this unit tell the story of why it's so popular: Auto-start operation, separate input filters for each shift, an antispace feature, and switch selection of 850 and 170 Hz shifts are standard. An extra discriminator for a 425 Hz shift is available as an option. A space-saving special power transformer is part of the package; it includes windings for low voltage and loop supplies, and a 115/230 VAC primary. Dual-in-line IC's are mounted in sockets for ease of testing and replacement. Seven G10 epoxy glass boards with reliable wiping contacts hold all circuitry. Tuning is read from a 1 ma. panel meter which, at the flick of a switch, serves as a loop current readout. Other visual indicators display AC power on, Mark, and Space conditions. Two other lamps indicate whether the ST-6 is in the receive or standby mode. For maximum safety, a three-wire grounding

cord and grounding outlet for the printer are included. The power supply card contains easy-to-replace clip-in fuses. The ST-6 is available factory assembled and aligned, or in kit form. The PC boards and cabinet only are also available.

A popular option designed to plug right in to the ST-6 is HAL's AK-1 AFSK oscillator. Available assembled or in kit form, the AK-1 is an AFSK oscillator that demonstrates stability and reliability. It provides switch selection of 170 Hz and 850 Hz shift using standard AFSK tones. The AK-1 may also be mounted in its own cabinet for use as an independent unit. Frequencies are set by 15-turn trimmers for ease of accurate tone adjustment. The AK-1 operates on 12 VDC, or directly from the ST-6 power supply.

If you're ready for the very best RTTY at an attractive price, look into the HAL ST-6 TU, the 425 Hz discriminator, and the AK-1 AFSK oscillator. They'll give you all the help you need. Order yours today!

Prices:

Assembled:

\$310 — ST-6 Terminal Unit

\$350 — ST-6/425 Hz Disc.

\$350 — ST-6/AK-1

\$390 — ST-6/425 Hz Disc/AK-1

Kit Form:

\$147.50 — ST-6 Terminal Unit

\$ 35.00 — ST-6 Table or Rack Cabinet

\$ 29.00 — 425 Hz Discriminator

\$ 29.00 — AK-1 AFSK Unit

All prices postpaid, USA. For air shipment add \$4 for the ST-6 kit or cabinet, \$1 each for the 425 Hz kit or the AK-1 kit, \$10 for the assembled ST-6 with any options.



HAL Communications Corp.  
Box 365, Urbana, Illinois 61801  
Telephone: (217) 367-7373

- ☐ Enclosed is \$\_\_\_\_\_ for the following items: ☐ ST-6 Assembled, ☐ With all options; ☐ ST-6/425 Hz Disc; ☐ ST-6/AK-1; ☐ ST-6 kit; ☐ ST-6 Cabinet; ☐ 425 Hz Disc kit; ☐ AK-1 kit.
- ☐ Charge to my Master Charge # \_\_\_\_\_  
BankAmericard # \_\_\_\_\_  
Master Charge/Interbank # and Exp. date \_\_\_\_\_

☐ Please send me the HAL catalog.

Name \_\_\_\_\_

Address \_\_\_\_\_

City/State/Zip \_\_\_\_\_

Illinois residents add 5% sales tax. H



September, 1975  
volume 8, number 9

**staff**

James R. Fisk, W1DTY  
editor-in-chief

Patricia A. Hawes, WN1QJN  
assistant editor

J. Jay O'Brien, W6GO  
fm editor

James A. Harvey, WA6IAK  
James W. Hebert, WA8OBG  
Joseph J. Schroeder, W9JUV  
Alfred Wilson, W6NIF  
associate editors

Wayne T. Pierce, K3SUK  
cover

T.H. Tenney, Jr., W1NLB  
publisher

Fred D. Moller, Jr., WN1USO  
advertising manager

Cynthia M. Schlosser  
assistant  
advertising manager

**offices**

Greenville, New Hampshire 03048  
Telephone: 603-878-1441

**ham radio** magazine is  
published monthly by  
Communications Technology, Inc  
Greenville, New Hampshire 03048

**subscription rates**

U.S. and Canada: one year, \$8.00  
two years, \$13.00; three years, \$18.00  
Worldwide: one year, \$10.00  
two years, \$17.00; three years, \$24.00

Foreign subscription agents  
Canada  
Ham Radio Canada  
Box 114, Goderich  
Ontario, Canada, N7A 3Y5

Europe  
Ham Radio Europe  
Box 444  
194 04 Upplands Vasby, Sweden

France  
Ham Radio France  
20 bis, Avenue des Clarions  
89000 Auxerre, France

United Kingdom  
Ham Radio UK  
Post Office Box 64, Harrow  
Middlesex HA3 6HS, England

African continent  
Holland Radio, 143 Greenway  
Greenside, Johannesburg  
Republic of South Africa

Copyright 1975 by  
Communications Technology, Inc  
Title registered at U.S. Patent Office  
Printed by Wellesley Press, Inc  
Framingham, Massachusetts 01701, USA

Microfilm copies of current and  
back issues are available from  
University Microfilms  
Ann Arbor, Michigan 48103

Second-class postage  
paid at Greenville, N.H. 03048  
and at additional mailing offices



# contents

**8 inductively-tuned six-meter kilowatt**

Donald J. Cook, K1DPP

**16 tunable notch filter**

Courtney Hall, WA5SNZ

**22 optimizing the phase-locked loop  
RTTY terminal unit**

P. Edward Webb, W4FQM

**26 toroidal coil inductance**

Charles G. Miller, W3WLX

**28 single-sideband speech splatter —  
its causes and cure**

Robert P. Haviland, W4MB

**36 100-watt solid-state power  
amplifier for 432 MHz**

R. Keith Olsen, WA7CNP

**44 hand-held touch-tone**

Albert L. Lowenstein, K7YAM

**48 how to use meters**

Guy Black, W4PSJ


**54 magnet-mount vhf mobile antenna**

George R. Allen, W1HCI

**58 300-Hz crystal filter for  
Collins receivers**

James R. Fisk, W1DTY

- |                              |                           |
|------------------------------|---------------------------|
| <b>4 a second look</b>       | <b>68 new products</b>    |
| <b>110 advertisers index</b> | <b>110 reader service</b> |
| <b>62 comments</b>           | <b>67 short circuit</b>   |
| <b>99 flea market</b>        | <b>6 stop press</b>       |
| <b>66 ham notebook</b>       |                           |

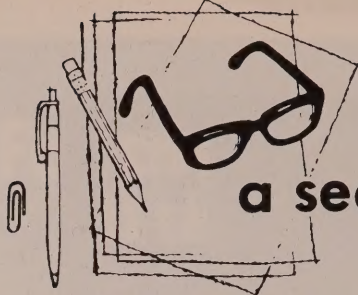

# a second look

by jim  
fisk

Recently there has been rising concern over the possible harmful effects to living tissue due to heating by electromagnetic radiation in the frequency range from 10 MHz to 100 GHz. Although microwave engineers have been aware of the potential hazards of working around high-power microwave transmitters for 25 years or more, few people expressed much concern about the possible radiation hazards of lower-frequency equipment. However, from 150 to 1200 MHz the internal body organs are susceptible to damage from rf heating, and the eye is especially prone to damage from radiation above 1000 MHz.

The scientific community is not at all satisfied that there has been sufficient research for formulating rf exposure standards, but based on present knowledge, various governmental and industrial organizations involved in establishing radiation safety standards have recommended exposure limits referred to as Radiation Protection Guide Numbers (RPGN). At the present time the generally accepted RPGN value is 10 milliwatts per square centimeter, and the Occupational Safety and Health Admin-

istration (OSHA) has promulgated a standard which limits exposure to power densities greater than 10 mW/cm<sup>2</sup> of body area.

Authorities generally agree that rf power levels one-tenth the OSHA standard (1 mW/cm<sup>2</sup>) do not have any noticeable effect. Using this as a basis, what are typical safe distances from a high-frequency amateur antenna?

Since the safe distance from an antenna depends on its radiated power in a given direction, the most direct approach to finding the distance is to use a graph such as that shown in fig. 1. These curves are based on an isotropic radiator so antenna gain (power ratio, *not* dBi) must be factored in for the practical case. A half-wave dipole, for example, has a power gain of 1.64 over an isotrope (2.14 dBi). Assuming 1000 watts into the antenna, what is the minimum safe distance? The effective isotropic radiated power (EIRP) is 1.64·1000 or 1640 watts and the distance for a power density of 1 mW/cm<sup>2</sup> is about 24 feet.

Since most dipoles are installed at least 25 feet above ground, they obviously pose little threat at amateur power levels, but what about multi-element beams and stacked arrays? Assuming the array is at the top of a 54-foot tower, and not facing into a building, an EIRP of about 29 kW would be required to produce 1 mW/cm<sup>2</sup> in the center of the main lobe 100 feet away. With 1000 watts into the antenna, this corresponds to a power gain of 29 or 14.6 dBi.

Few amateur antennas exhibit this much gain, but EME operators who use large arrays or big parabolic reflectors should use caution. A 30-foot dish with only 10 watts input at 432 MHz, for example, is hazardous at distances of less than 18 feet!

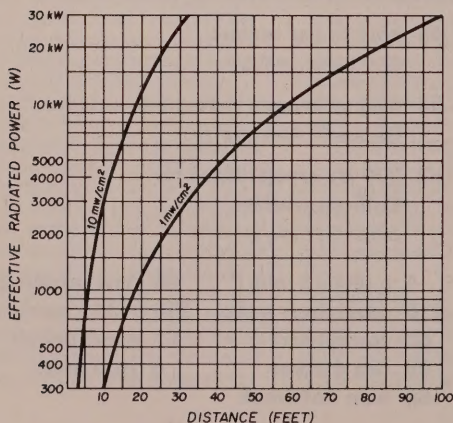



fig. 1. Minimum distances from radiators at which Radiation Protection Guide Numbers are not exceeded vs effective isotropic radi-

Jim Fisk, W1DTY



# THE FIRST AND STILL THE LEADER!

## the exciting super compact IC230

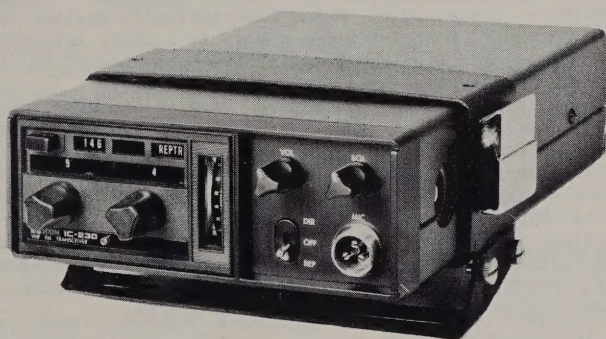

PUT OVER 67 CHANNELS IN THE PALMS OF YOUR HANDS

### SPECIAL FEATURES:

- **No More Crystals** . . . Over 67 . . . fully synthesized channels available.
- **All Channel Capability** . . . Travel with confidence that you'll be able to work all repeaters along the way.
- **Super Compact** . . . 2.28" high x 6.14" wide x 9.72" deep at a weight of only 5.5 lbs.
- **Quick Dismount Mobile Mount** . . . Allows quick car installation.
- **Easy Operation** . . . Punch up frequency, select repeater or simplex mode, and you're on the air. (A crystal may be added for a unique repeater frequency.)
- **Modular Construction** . . . In case of a problem, modules can easily be removed and sent for repair. A replacement module will be air mailed to minimize down time.
- **Super Hot Receiver** . . . Better than .4uv / 20db. sensitivity, helical filters to eliminate intermod . . . plus a super E filter and a mosfet front end.

IF THERE IS A SIGNAL, YOU'LL HEAR IT ON THE IC-230!

*LATCH ON TO THE IC-230 AT YOUR AUTHORIZED ICOM DEALER*

Distributed by:



**ICOM**

— Dealerships Available —

**ICOM WEST, INC.**  
Suite 3  
13256 Northrup Way  
Bellevue WA 98005

**ICOM EAST, INC.**  
Suite 307  
3331 Towerwood Drive  
Dallas TX 75234

# presstop

AN IMPORTANT STORY is still Prose Walker's decision to step down as chief of the Amateur and Citizens Division on July 31st. Deputy Division Chief Dick Everett is presently serving as Acting Division Chief.

In The Long Term the question of who'll be filling Prose's shoes is a tough one. Ideally the job requires an engineer-ham with strong managerial experience — plus appropriate Civil Service status. Though the new chief is likely to come from within the Commission it isn't an absolute must. However, candidates without Civil Service Ratings must establish their qualifications with Civil Service before they can be considered for the post.

CB RESTRUCTURING — DOCKET 20120 — has been partially decided in a recently released Report and Order. Most important change is a sharp relaxation of prohibited communications effectively permitting the hobby use of CB that has already characterized the service legal or not.

Also Relaxed are identification procedures, with an operator required to give only his call sign instead of both; the "quiet" period between five-minute series of transmissions has been reduced from five minutes to one minute; inter-licensee communications are now permitted on all 23 channels. Channel 9 continues to be classified as the emergency calling channel, and channel 11 has been designated a general calling channel.

Notable Emissions from this initial Report and Order on the Docket are the expansion to additional channels above the present band and the proposed conversion to all SSB. Though action on these can be expected eventually, it will probably rest to some degree on what happens with Class-E CB.

MANDATORY REVIEW OF LOGGING TAPES for repeaters operating under "automatic control" will not be required as a result of recent FCC decision. Logging tapes must still be made and kept for 30 days, and if any operating problems are reported to the control operator or licensee during that period the tapes must be reviewed and corrective action taken within 72 hours or the system must shut down.

This Easing Of Requirements for repeater operators takes most of the sting out of the Commission's Report and Order — mandatory review had been the principle objection raised by the repeater fraternity.

AMSAT MEMBERS not planning to attend AMSAT's annual meeting at the ARRL Convention in September are reminded that their ballots for the Director's election are needed to insure a quorum. The annual meeting is scheduled Sunday, September 14, at Reston, Virginia.

New Two-Color Bumper Sticker Decals are now available from AMSAT. They are being sent free to new members and renewing old members, or sold three for \$1 plus SASE from AMSAT, Box 27, Washington, DC 20044.


TV TUNER WITH MEMORY has some interesting design features for Amateur radio applications. Announced in July by General Instrument, the tuner uses a non-volatile memory chip that contains 100 lines of 14 bits each. Each line can be programmed for one TV channel, and when needed the memory information is fed to a 14-bit CMOS D/A converter to produce an analog voltage which is applied to a varactor diode and tunes in the station.

HAM GEAR SHORTAGES have been plaguing dealers for some time and are likely to get worse before they get better. The major cause of the problem is the CB explosion, since many manufacturers — particularly those in the Far East — supply both the Amateur and CB markets and it pays them to put their major effort in the market with the most money.


TYPE ACCEPTANCE OF AMATEUR GEAR is still a hot issue around the FCC. Don't be surprised to see a Notice of Proposed Rule Making come out of the Commission soon.

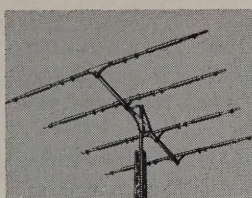Continued Abuses By CBers using Amateur transceivers and manufacturers building "broadband" linears for the "Amateur Radio market" that just happen to deliver full output with only 4 watts drive (on ten meters, of course) have pretty well forced the FCC to act.





# HOT

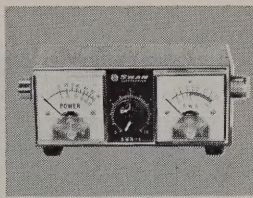

# COMBO

Element for element, our rugged High-Q beam antennas are designed to give you the biggest signal your transmitter is capable of.

Now when you install one of these Swan antennas you can make sure you're running full bore all the time by hooking our new SWR/RF Power meter in the coax.

## Heavy duty 4-element Tribander

Four elements work on 10, 15 and 20 meters. Optimum spacing for maximum performance. Precision tuned, weatherproof traps. 100-mph winds. TB-4HA. \$249.95

## Heavy duty 3-element Tribander

Three elements work on 10, 15 and 20 meter bands. Rugged construction. Precision tuned, weatherproof traps. Excellent performance on lighter tower. TB-3HA. \$189.95

**Economy 2-element Tribander** Light enough for standard TV rotator but

withstands 80 mph winds. Two working elements on 10, 15 and 20 meters. TB-2A. \$129.95

## Heavy duty 2-element 40-meter Beam

Two elements on steel beam. Maximum performance for 40-meter CW or phone. Big, weatherproof high-Q loading coils. Easily takes 100 mph winds. MB-40H. \$199.95

**SWR/RF Power meter** Combination meter measures standing wave ratio and antenna power. Low insertion loss lets you leave it in circuit. 3.5 to 150 MHz. \$21.95

**All Swan Beam Antennas are Rated for 2000 Watts and designed to use 52 Ohm coaxial feedlines.**

**SWAN BEAM ANTENNA SPECIFICATIONS**


| Antenna Model Number | Average Forward Gain | Front to Back Ratio | Boom Length & Diameter | Longest Element | Turning Radius | Maximum Wind Survival | Wind Load @ 80 mph | Wind Surface Area | Net Weight |
|----------------------|----------------------|---------------------|------------------------|-----------------|----------------|-----------------------|--------------------|-------------------|------------|
| TB-4HA               | 9 dB                 | 24-26 dB            | 24' x 1.5"             | 28'-10"         | 18'-6"         | 100 mph               | 148 lbs.           | 6 sq. ft.         | 54 lbs.    |
| TB-3HA               | 8 dB                 | 20-22 dB            | 16' x 1.5"             | 28'-2"          | 16'            | 100 mph               | 110 lbs.           | 4 sq. ft.         | 44 lbs.    |
| TB-2A                | 5 dB                 | 16-18 dB            | 6.5' x 1.5"            | 27'-8"          | 14'-3"         | 80 mph                | 60 lbs.            | 1.8 sq. ft.       | 18 lbs.    |
| MB-40H               | 4 dB                 | 16-18 dB            | 15.75' x 1.5"          | 30'-4"          | 17'-6"         | 100 mph               | 80 lbs.            | 2.5 sq. ft.       | 40 lbs.    |



**SWAN®**  
**ELECTRONICS**  
A subsidiary of Cubic Corporation

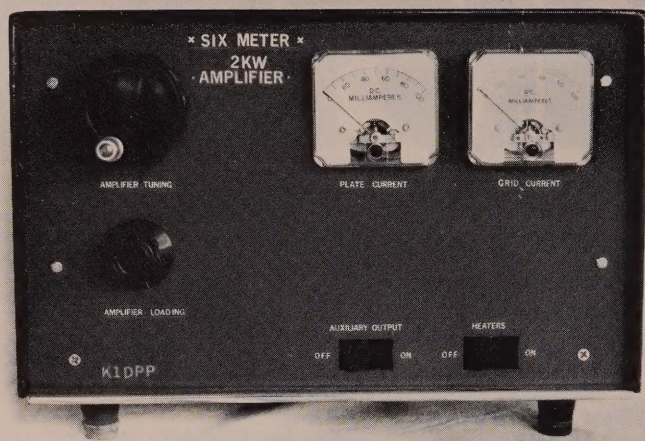305 Airport Road, Oceanside, Calif. 92054





## inductively-tuned six-meter kilowatt

Construction details  
for a high performance  
grounded-grid  
six-meter linear  
using 3-500Zs

At one time or another most serious six-meter operators have appreciated the value of having a high-power amplifier for extending their communications range — scatter, extended ground wave and aurora contacts are enhanced considerably by the proper use of an amplifier. I decided to build a two-kilowatt PEP linear amplifier around a pair of grounded-grid Eimac 3-500Zs because I have a Swan 250C which easily provides the 100 watt PEP input drive requirement. In addition, I have two other rf power amplifiers using 3-500Zs which have given me trouble-free service for

the past several years. A spare pair of tubes that were sitting on the shelf helped convince me to go in this direction.

After acquiring operating manuals from different manufacturers and going through the various amateur magazines, scanning articles and circuits which used 3-500Zs, I built the six-meter kilowatt described here.

The 3-500Z tubes are air-cooled power triodes designed for zero bias operation and are rated to 110 MHz. They are cathode driven with the grids at rf and dc ground. The tuned-cathode input circuit (**fig. 1**) provides good linearity and minimizes the drive requirements. The filaments are isolated from rf ground with the high-current bifilar rf choke, RFC1. The tuned plate circuit in this amplifier, however, is a bit unusual — the normal pi-network tuning capacitor has been replaced by an inductively-tuned or shorted-turn plate tank coil. Most circuit losses at 28 MHz and up are due to residual circuit capacitance and much of this undesired effect is due to the pi-network input tuning capacitor commonly used at lower frequencies.<sup>1</sup>

Donald Cook, K1DPP, 628 Rindge Road, Fitchburg, Massachusetts



In this circuit the pi-network input capacitance, C5, consists of stray circuit and tube capacitance.

The control relay, K1, which switches the amplifier into the circuit and shorts out the 10k, 10 watt resistor, allowing normal plate and grid current to flow, is operated from a low current dc supply derived from a winding on the filament transformer. External interlocks (not shown here) make it impossible to apply plate voltage without first turning on the filaments and blower.

The two meters on the front panel of the amplifier shown in the photographs are used to read the grid and plate circuits. Since the meters I used had 100-milliamperre movements, I used resistance shunts to provide a multiplier of five for the grid current meter (500 mA) and ten for the plate current meter (1 ampere).

## construction

The pi-network inductor is wound from ¼-inch (6.5mm) diameter copper tubing and the shorted turn is made from a section of 1½-inch (38mm) copper water pipe. This slug is moved in

Plate compartment of the six-meter kilowatt showing construction of the pi-network inductor, parasitic chokes and RFC2. The neutralizing capacitor is located between the two tubes. The pi-network loading capacitor is positioned underneath the tunable inductor.

and out of the inductor to tune the plate tank circuit to resonance. Construction details for this assembly are shown in fig. 2.\* Although I used a simple spinner knob on the inductor tuning screw, a turns-counting dial could be used to provide a logging reference for various operating frequencies.


The grid pins on the 3-500Z sockets are directly grounded to the chassis with ¼-inch (6.5mm) wide copper strap. One end of the strap is soldered to the socket pins and the other end is attached to the chassis with 6-32 (M-3.5) screws and nuts. Make sure that both contact surfaces are clean for low-resistance, trouble-free grounding. The homebrew filament choke consists of 12½ bifilar turns number-12 (2.1mm) Formvar on a ½-inch (13mm) diameter ferrite rod (suitable filament choke kits are available from Amidon Associates†).

The shunt-feed rf choke, RFC2, is connected directly across the plate tank circuit, so it must provide good isolation over the entire six-meter band. Hand winding, as described here, is highly recommended as no commercially available rf choke is apt to provide as good performance. The winding is most easily accomplished by feeding *two* number-20 (0.8mm) wires through one hole in the coil form and winding a bifilar coil of 30 turns, ending at the other hole in the form. Remove *one* of the bifilar windings and you will have a tight, evenly spacewound winding that makes an excellent six-meter choke. The cold end of the rf choke is bypassed to ground with a 500 pF TV-type doorknob capacitor.

The 500-pF dc blocking capacitors, C3 and C4, are mounted between two

\*Major components for the shorted-turn inductor are available from Edward A. Stoltzfus, Engineering Machinist, Beacon Light Road, Parkesburg, Pennsylvania 19365.

†Amidon Associates, 12033 Otsego Street, North Hollywood, California 91607. Filament choke kit is \$2.50, postpaid.

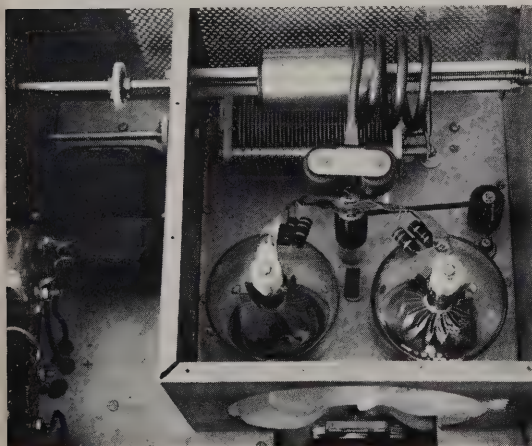

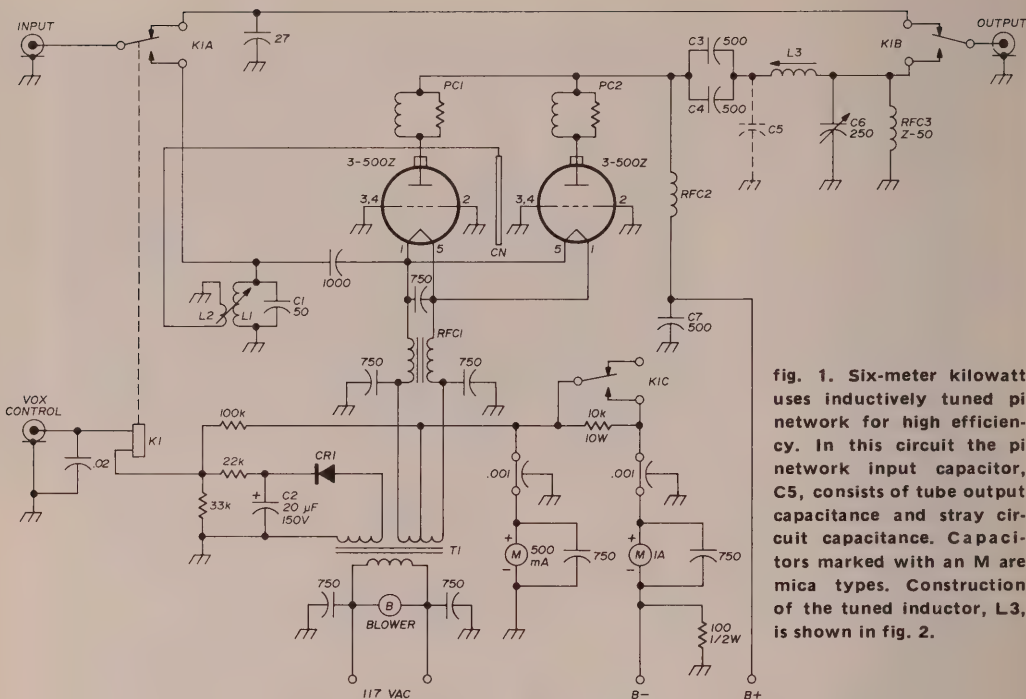


fig. 1. Six-meter kilowatt uses inductively tuned pi network for high efficiency. In this circuit the pi network input capacitor, C5, consists of tube output capacitance and stray circuit capacitance. Capacitors marked with an M are mica types. Construction of the tuned inductor, L3, is shown in fig. 2.

- C1 50 pF compression mica trimmer (AR-CO 462). Adjust L1 for resonance with C1 compressed 90 percent
- C3,C4 500 pF, 5 kV doorknob capacitor (Centralab 858S)
- C5 residual circuit and tube output capacitance
- C6 250 pF air variable (E. F. Johnson 154-1)
- C7 500 pF, 10 kV doorknob capacitor (TV type)
- CN Neutralizing capacitor, copper strap 1/2" (13mm) wide by 3 1/2" (89mm) long
- CR1 Silicon diode, 600 PIV, 1 A
- K1 110 Vdc relay, 3 pole, double throw (Potter & Brumfield KA14DG or Heath 69-55)
- L1 3 turns no. 14 (1.6mm), airwound, 1/2" (13mm) diameter, 5/8" (16mm) long
- L2 2 turns no. 18 (1.0mm) insulated wire, 1/2" (13mm) diameter, placed between turns of L1 (note polarity)

- L3 3 1/2 turns 1/4" (6.5mm) copper tubing, 3" (76mm) long, 2-1/8" (54mm) inside diameter. Tuning slug details are shown in fig. 2.
- PC1,2 Parasitic suppressors, Each consists of three 50 ohm, 2 watt resistors shunted across 1/2" (13mm) wide copper plate strap. Install as close to the plate cap as possible (see photo)
- RFC1 12 1/2 turns no. 12 (2.1mm) Formvar, bifilar wound on 1/2" (13mm) diameter, 3 1/2" (89mm) long ferrite rod (Amidon Associates filament choke kit)
- RFC2 30 turns no. 20 (0.8mm) enamelled wire, space wound on 3/4" (19mm) round, 3-3/4" (95mm) long ceramic or Teflon rod. Drill holes for wire ends 1/2" (13mm) and 2-3/4" (70mm) from top or rod
- T1 dual secondary transformer. 5 Vac at 30 amps (filaments), 120 Vac (relay K1 dc supply)

brass plates, one of which is attached to the top of RFC2. The other plate is connected to the pi-network inductor L3 (see photo of the rf compartment).

The amplifier is built on a homemade

chassis made from 3/32-inch (2.5mm) thick aluminum sheet and is 1-3/4 inch (4.5cm) high, 12 inches (30.5cm) wide and 13 inches (33cm) deep. The front and rear panels are 1/8-inch (3mm)




thick aluminum, 8 inches (20.5cm) high by 13 inches (33cm) wide. The inner right- and left-hand panels are 1/16-inch (1.5mm) thick aluminum, 7½ inches (19cm) high by 13 inches (33cm) long. These two panels can be made from perforated stock or solid sheets can be drilled to provide for ample air intake and exhaust to cool the plate and filament seals.

The rf compartment is 10 inches

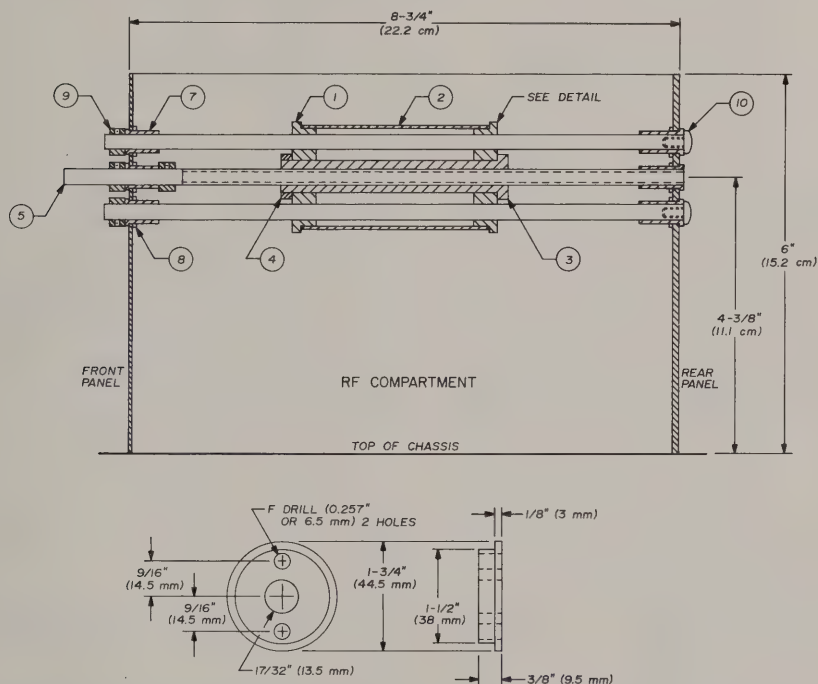(24.5cm) wide, 8-¾ inches (22cm) deep and 6 inches (15cm) high. The top cover for this compartment is made from perforated aluminum sheet and should be installed at all times to protect the operator from the lethal voltages which are used to operate this equipment.

The bottom cover is 1/16-inch (1.5mm) thick aluminum, 13 inches



1. Insulating disc, 1-3/4" (44.5mm) diameter, 3/8" (9.5mm) long (2 required).
2. Tuning slug. 1-5/8" (41.5mm) OD, 1/16" (1.5mm) wall copper water pipe, 3" (76mm) long.
3. Tuning mechanism, make from brass rod, 1/2" (13mm) OD, 3-5/8" (92mm) long. Drill and tap for ¼-20 (M7) thread for full length. Thread outside diameter ½-13 (M12) 1" (25mm) on both ends.
4. Brass nuts, ½-13 (M12), split into two pieces about 3/16" (5mm) long.
5. Lead screw. ¼" (6.5mm) diameter brass rod, 9-7/8" (25cm) long, threaded ¼-20 (M7) for 8" (21cm).
6. Guide rods. Plastic or fiberglass rods, ¼" (6.5mm) diameter, 9¼" (23.5mm) long (2 required). Drill and tap one end ½" (13mm) deep for 6-32 (M3.5) machine screw.
7. Panel bushings for ¼" (6.5mm) shaft (6 required).
8. Panel bushing nuts (6 required).
9. Shaft stops, for ¼" (6.5mm) shafts (4 required).
10. Machine screws, 6-32 x ¼" long (M3.5x6.5) (2 required).

fig. 2. Construction of the tuned pi-network inductor, L3. This arrangement requires a minimum of machine work and uses readily available materials.

(33cm) wide by 14 inches (35.5cm) deep with 1/2-inch (13mm) lips formed on two sides to provide a mating surface for the top cover. The U-shaped top cover is also made from perforated alu-

minum. The trim around the raw edges on the top and bottom covers is car door protective edging that is available from most department and automotive stores; it is very easy to work and cut

with simple hand tools. The vox connector and power plugs are all brought out on the rear panel along with the input and output coaxial connectors.


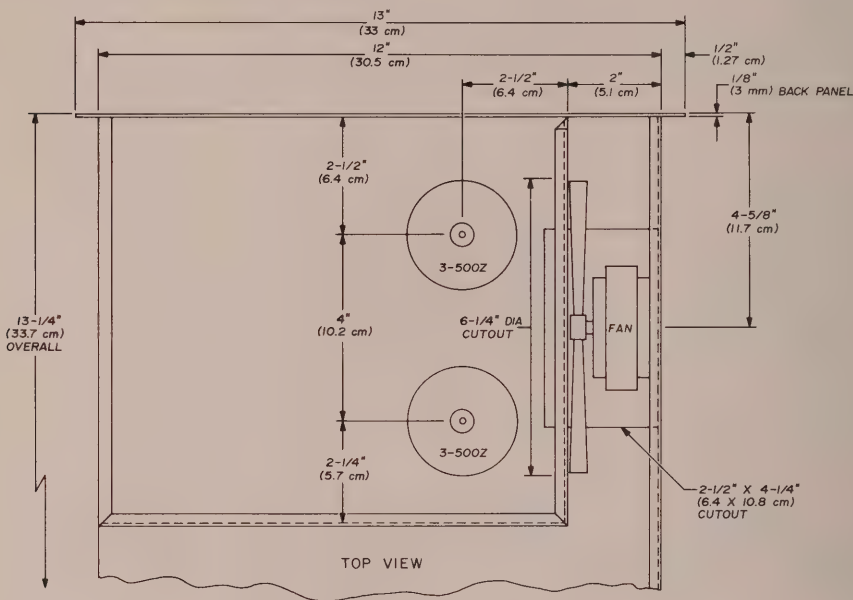


fig. 3. Air-system layout. The cooling air passes across the tube envelopes and the warm air exhausts out the side of the amplifier enclosure. Fan should provide 13 CFM at 0.2 inch (5mm) back pressure. Author used a 6" (15cm) diameter, six-bladed fan (Heath 266-259) and Heath 420-83 fan motor. Suitable substitute is a no. 3 impeller at 3100 rpm (Ripley 8472, Dayton 1C180 or Redmond AK-2H-01 Ax).

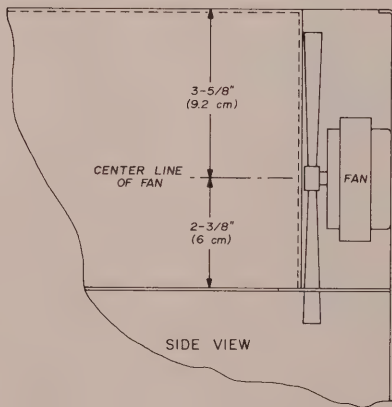

maintain the plate seals of the 3-500Zs below 225°C and the filament seals below 200°C. Many 3-500Z power amplifiers are designed around a system of air-system sockets and chimneys, along

with simple hand tools. The vox connector and power plugs are all brought out on the rear panel along with the input and output coaxial connectors.



with a centrifugal blower. The noise generated by the blower motor and air movement through the cooling system, however, is very distracting. Extensive tests by Eimac have shown that for CW

Eimac HR6). The Johnson 122-275-1 ceramic tube sockets are mounted off the chassis about 1/8 inch (3mm) to allow air flow around the base of the tubes to cool the filament pins.

**table 1. Typical operating data for the 3-500Z in rf linear amplifier service, class B (two tubes).**

| Dc plate voltage                         | 1500 | 2000 | 2500 |
|--|------|------|------|
| Zero signal plate current (mA)           | 130  | 190  | 260  |
| Single tone dc plate current (mA)        | 800  | 800  | 800  |
| Single tone dc grid current (mA)         | 260  | 260  | 240  |
| Two-tone dc plate current (mA)           | 520  | 540  | 560  |
| Two-tone dc grid current (mA)            | 160  | 160  | 140  |
| PEP useful output power (watts)          | 660  | 1000 | 1200 |
| Intermodulation distortion products (dB) | -46  | -38  | -33  |

and ssb operation at legal amateur power limits the 3-500Zs may be adequately cooled by a lateral air blast blown against the tubes by a small, properly positioned rotary fan.<sup>2</sup>

The arrangement of the cooling fan in the six-meter kilowatt is shown in fig. 3. The fan is mounted in the rf compartment wall, between the tubes, in line with the center of the glass envelopes, and blows cooling air across the envelope and plate caps (use a good heat-dissipating plate connector such as the


With this arrangement maximum plate dissipation of about 450 watts per tube is achieved for the 3-500Z. While this is about 10 percent short of the maximum rating, dissipation is sufficiently high that the pair of tubes will easily handle the maximum amateur power limit for CW or ssb operation under normal operating conditions. For continuous operation (RTTY or sstv, for example) the power input must be reduced to about 750 watts.

### neutralizing


The neutralizing capacitor, CN, is formed from a 0.032-inch (0.8mm) thick copper strip, 1/2-inch (13mm) wide and 3½-inches (89mm) long into an L-shape with the foot of the L about 3/8-inch (10mm) long. The foot is drilled for mounting to the threaded stud of a small ceramic feedthrough bushing. The feedthrough bushing is centrally located between the two 3-500Zs and in line with the socket mounting holes toward the rf choke (see photograph). This capacitor is adjusted to lean in toward the center line of the tubes.

Inductor L2 is inserted between the turns of L1, the input circuit coil, and adjusted until the amplifier is neutralized (stabilization occurs when maximum grid current, maximum output

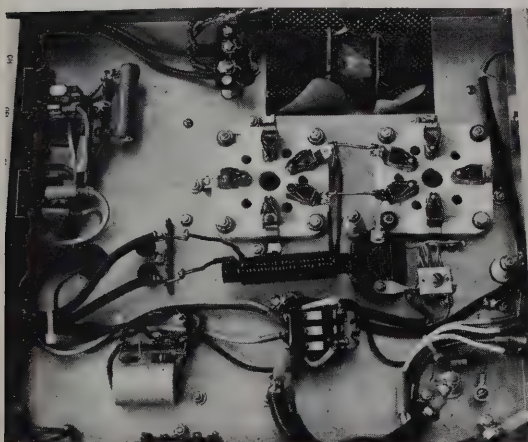**Under-chassis view of the six-meter kilowatt showing placement of major components. The tuned cathode circuit is located at right center.**



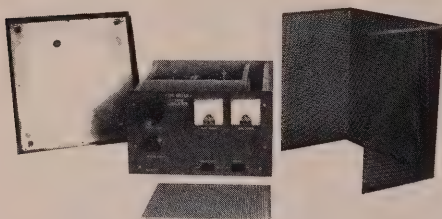and minimum plate current all are reached at one setting of the plate tank circuit). With the amplifier turned on but with no drive signal, grid current should be zero. I used an insulated rod to adjust L2 through a small hole in the bottom compartment. The neutralizing capacitor should be adjusted with the power turned off.



Two views of the power amplifier which show the various pieces of metalwork which were used in its construction.

## tune up

Before applying any voltages to the amplifier, carefully check all the wiring. Then install the two tubes and use a grid-dip oscillator to approximately set the tuned cathode circuit and pi network output circuit to the desired operating frequency. I used 50-ohm resistors across the input and output coaxial fittings during the grid-dipping operation and made sure that all relay contacts were closed.

After the amplifier has been cold tuned with the grid-dip meter, remove the 50-ohm resistors and connect the six-meter exciter to the input and a dummy load (or antenna) to the output. A monitor scope or relative power meter (an swr bridge works well) will provide a good output indication during initial testing of the amplifier.

First tune up the exciter for full normal CW output with the amplifier switched out of the line. Reduce exciter output, apply power to the amplifier and tune the amplifier for maximum output with reduced B+. Gradually in-

crease the excitation and high voltage to get the feel of a very smoothly tuning six-meter power amplifier.

For CW operation with a 2500-volt power supply tune the plate circuit and adjust the exciter drive for a plate current reading of about 400 mA (about 125 mA grid current). I am using a power supply with a tapped primary which I can switch from 2300 volts for CW and tuning, and then to 2800 volts for ssb operation.



I usually tune for maximum output with the lower voltage and then switch to the higher voltage for ssb. Apply ssb drive from the exciter and advance the microphone gain control for an average plate current reading of 350 mA. An occasional voice peak may boost this up to 600 mA. A monitor scope will show you more than any plate meter can be expected to, and should be used at all times when you are running high power. The manufacturer's operating data for the 3-500Z is published in most handbooks and should be consulted as a guide for proper use of these tubes in amateur service.


## references

1. William Orr, W6SAI, "Inductively-Tuned High-Frequency Tank Circuit," *ham radio*, July, 1970, page 6.
2. William Orr, W6SAI, *Radio Handbook*, 19th edition, Editors and Engineers, Indianapolis, 1972, page 22-35.

ham radio


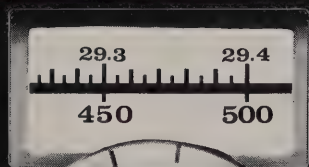
# How to make a good transceiver better...



## Increase the frequency coverage

*Introducing the new*

# ATLAS 210X

(and Atlas 215X)

Even though the Atlas 210 and 215 have been the hottest selling solid state SSB transceivers on the market, we never stop looking for ways to improve our products.

The new Atlas 210X/215X have the same compact size (9½" x 3½" x 9½") and light weight (7 lbs.), with the same 200 watt power rating, and same super selectivity. But several improved features have been engineered into the new 210X/215X.

- Full band coverage of 160 through 15 meters
- 1000 kHz coverage on 10 meters.
- Extended coverage for MARS operation when used with the Model 10X crystal oscillator. Special MARS model no longer required.
- Improved Automatic Gain Control (AGC).
- Improved S-meter calibration.
- Improved image suppression.
- Plus all the performance, reliability and

versatility that have made Atlas transceivers the talk of the ham bands.



**\$649**

For complete information on the new 210X/215X and accessories, see your Atlas dealer, or drop us a card and we'll mail you a brochure and dealer list.

AMERICAN MADE AND GUARANTEED BY:  
 **ATLAS**  
**RADIO INC.**

417 Via Del Monte Oceanside, CA 92054  
Phone (714) 433-1983

# tunable RC notch filter

Discussion of an  
RC notch filter  
which can be tuned  
with a single  
variable resistor

Of the host of RC notch filters that have been devised, the twin-T (also called parallel-T) has enjoyed the greatest popularity by far. This is surprising because, in order to make this circuit adjustable or tunable, three components, either resistors or capacitors, must be varied simultaneously. To make matters worse, these three components don't all have the same value as shown in the basic circuit of fig. 1. One of the resistors is one-half the value of the other two, and one capacitor is twice the value of the others. Therefore, an adjustable twin-T notch filter requires a three-gang potentiometer, and the tracking and alignment problems can be troublesome if not expensive.

There is another circuit, however, which has performance comparable to the twin-T, but which can be tuned over a wide frequency range by means of a single potentiometer. Although this circuit has been around for about 20 years, it has seldom appeared in the electronics literature and is not widely used.

To my knowledge, this tunable notch filter first appeared in print in 1955 when it was mentioned by Henry P. Hall of the General Radio Company in the September issue of *IRE Transactions on Circuit Theory*. He discussed it further in the July, 1961, issue of the *General Radio Experimenter*. That same year, General Radio brought out its Type 1232-A Tuned Amplifier and Null Detector; this instrument used Hall's tunable notch filter as a feedback element around an amplifier to produce a continuously tunable, narrow-band audio amplifier. General Radio still markets this instrument for about \$700.

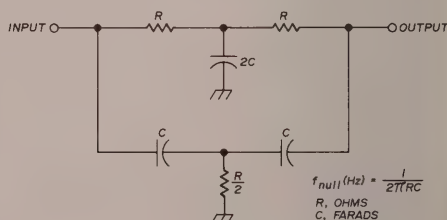


fig. 1. The twin-T notch filter is difficult to tune because three components must be varied simultaneously.

Courtney Hall, WA5SNZ, 7716 La Verdura Drive, Dallas, Texas 75240



In the October, 1969, issue of *EEE Magazine*, Ralph Glasgal, in his article, "Tunable RC Null Networks," referred to the circuit as a "bridged differentiator." These articles are the only ones on this circuit of which I am aware. The following sections describe my own investigations.

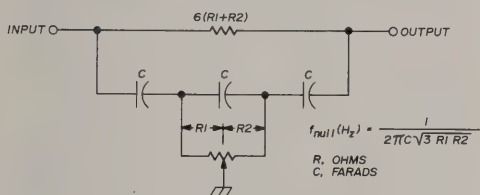


fig. 2. Basic circuit for a tunable RC notch filter which requires only one variable resistor.

## the circuit

Fig. 2 shows the basic configuration of Hall's tunable notch filter. The tuning pot is composed of R1 and R2, R1 being the resistance between one end of the pot and the wiper, and R2 the resistance between the other end of the pot and the wiper. The other resistor in the circuit must have a value equal to six times that of the pot. All three capacitors have the same value, which simpli-

fies things if you want to match them for best performance.

The null frequency equation in fig. 2 may be solved for different values of R1 and R2, and the results plotted to show how the notch frequency changes as the wiper is moved from one end of the pot to the other. Fig. 3 shows the result if the pot is assumed to be linear. When the wiper of the pot is at its mid-position (50 per cent of rotation) the notch frequency has its lowest value, and very little change in null frequency occurs in the middle section of the pot. As the wiper approaches either end of the pot, however, the null frequency begins to increase quite rapidly and would theoretically become infinite at the ends of the pot.

From the curve of fig. 3 it can be seen that, in a practical tuned notch filter, the tuning pot need only cover a relatively small percentage of the range shown. In other words, if the actual pot were used with fixed series resistors so that the pot covered only the range from 1 to 10 per cent, the relative frequency range would be from 10 to 3.3, or a 3 to 1 frequency range. Fig. 4 shows a schematic of how this would be implemented. Once the value of the pot has been selected, the values of the

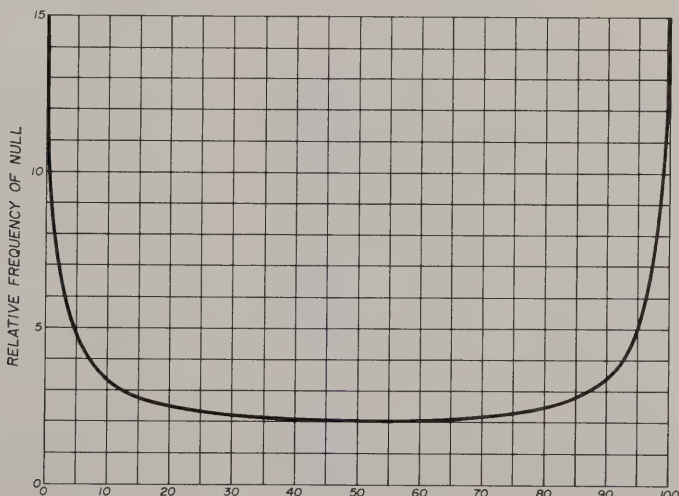


fig. 3. Relative notch frequency of the circuit shown in fig. 2 vs the rotational position of the potentiometer wiper.

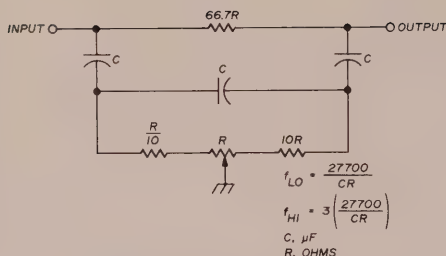


fig. 4. Relationship of resistance values for a 3:1 notch-filter tuning range.

three resistors may be calculated from the relationships shown.

It can be shown that the lowest notch frequency is given by

$$f_n = \frac{27700}{CR} \quad (1)$$

where  $f_n$  is in Hertz,  $C$  is in microfarads, and  $R$  is the resistance of the pot in ohms. The highest frequency to which the notch may be set is equal to three times the value given by eq. 1.

### practical examples

As a starting point, I had on hand a 20k pot and some 5 per cent, 2000 pF dipped-mica capacitors. These components would give a lowest notch frequency of

$$f_n = \frac{27700}{(0.002)(20 \times 10^3)} \approx 693 \text{ Hz}$$

The highest notch frequency should be three times this value or about 2079 Hz.

Using the resistor relationships of fig. 4, the circuit design was completed as

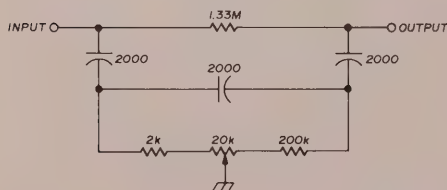


fig. 5. Notch filter which tunes from 693 to 2079 Hz. Performance of this circuit is plotted in fig. 6.

shown in fig. 5. It was necessary to connect resistors in series to arrive at some of the values shown, and the pot had a tolerance of at least  $\pm 10$  per cent. Fig. 6 shows the response of this filter with the tuning pot set at each end of its rotational range. Depth of the notch varies, but is greater than 50 dB in all cases; at 1160 Hz, the notch depth is 54 dB. Actual notch frequencies at the ends of the pot match the calculated values reasonably well, and the tuning range is slightly over 3 to 1.

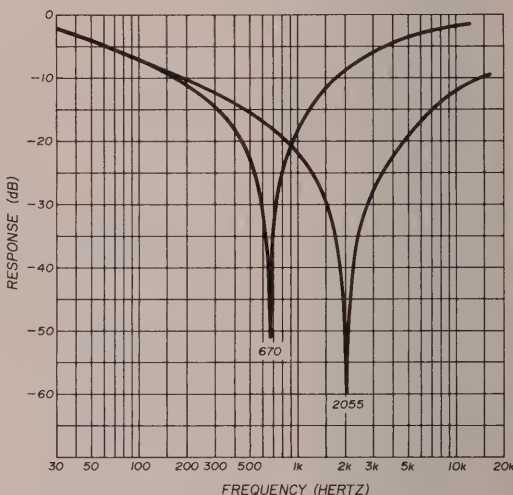


fig. 6. Frequency response of the notch filter of fig. 5 with the potentiometer set at each end.

The response curves of fig. 6 point out the value of tuning capability in notch filters. Because the notch is so sharp and narrow at the point of maximum attenuation, it is difficult to get the peak right on a particular frequency with a filter built with fixed-value components. With a tunable notch, however, it's a simple matter to set the notch right where you want it.

An example of a tunable notch filter for 60 Hz is shown in fig. 7. Such a filter can often be useful in high gain audio and sub-audio circuits to mini-



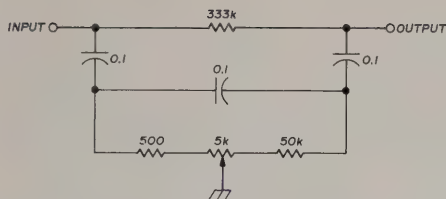


fig. 7. Tunable notch filter for 60 Hz can be used to minimize hum pickup from the ac line (circuit tunes from 40 to 120 Hz).

mize the effects of stray pickup from the ac power line. This circuit tunes from about 40 to 120 Hz.

In the examples above, the tuning ranges can be easily changed by multiplying or dividing the capacitor values by a factor. For example, doubling the capacitor values of fig. 5 would result in a tuning range of about 335 Hz to 1028 Hz, while cutting the capacitor values in half would give a tuning range of about 1340 to 4110 Hz.

## optimizing notch depth

Greatest notch depth will result when the ratios of component values approach the exact theoretical design values. In this regard, there are two requirements: the capacitors should all be exactly equal in value, and the large-value resistor connected from input to output should be exactly six times the resistance in the variable-resistance branch of the network.

Capacitors may be matched by measuring them on a capacitance bridge or a

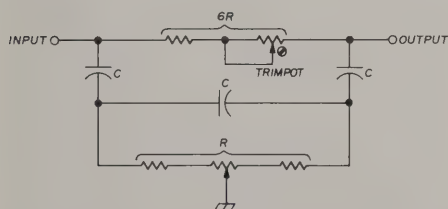


fig. 8. Notch depth may be optimized by using a trimpot to set the series resistance to exactly  $6R$ . Notch depth of the 60 Hz filter in fig. 7 was increased from 44.5 to 57 dB using this simple technique.

direct-reading capacitance meter and selecting those most nearly equal in value. An easy way to optimize the resistance ratio is to replace the resistor connected between the input and output with a trimpot and fixed resistor, or simply a trimpot, as shown in fig. 8; the trimpot can then be set for the deepest notch. Since changing this resistance also affects the notch frequency, it will be necessary to repeatedly adjust first the trimpot and then the tuning pot until the notch can no longer be improved.

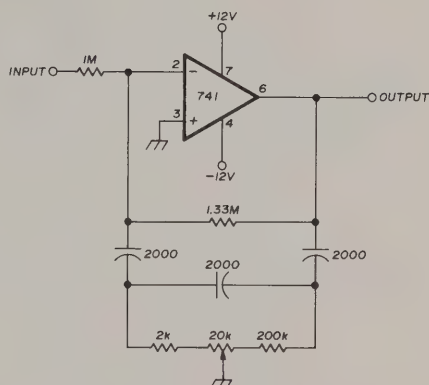


fig. 9. Tunable bandpass audio amplifier uses RC notch circuit as the feedback element. Tuning range of this circuit is 700 to 2000 Hz. Frequency response at 1000 Hz is plotted in fig. 10.

Once the trimpot has been set, however, it needs no further adjustment when the tuning pot is set to another frequency.

As an example of what this optimization can mean, the 60 Hz notch filter of fig. 7 was first built as shown with unmeasured ceramic disc capacitors and 5 per cent resistors; at 60 Hz it had a notch depth of 44.5 dB. By selecting capacitors with equal values and replacing the 333k resistor with a 500k trimpot, I was able, by careful adjustment, to increase the notch depth to 57 dB.

## tuned amplifier


The tuned notch filter can be used as

the feedback element with an op amp to produce a continuously tunable narrow-band audio amplifier. I used the circuit of **fig. 5** in conjunction with a 741 op amp to build a tunable bandpass audio amplifier which will tune from about 700 to 2000 Hz. This circuit is shown in **fig. 9**. With the tuning pot set for a center frequency of 1000 Hz, the 3 dB band-

cause the bandwidth is quite narrow as it stands.

Although I used plus and minus 12-volt power supplies for the 741 op amp, two 9-volt batteries should work okay; battery drain should be about 1 mA or less with a 2000 ohm load.

I have found that trying to increase the tuning range of this amplifier by in-

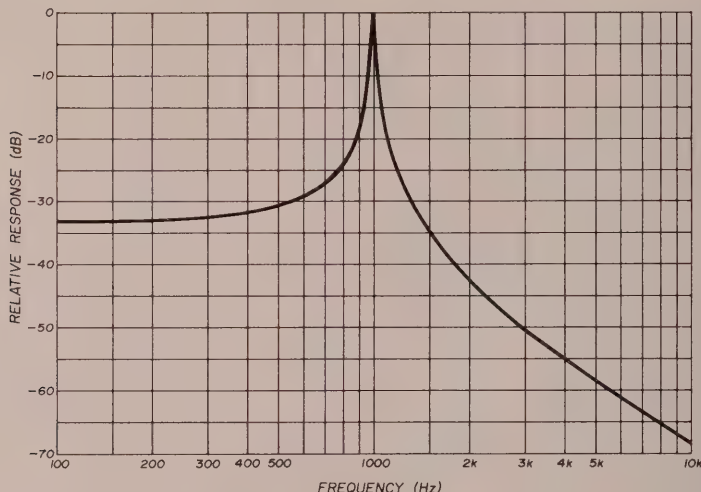

**fig. 10.** Frequency response of the tunable bandpass audio amplifier when tuned to 1000 Hz. Bandwidth at -3 dB points is 23 Hz; at -30 dB the bandwidth is approximately 773 Hz.

width is 23 Hz, the 6 dB bandwidth is 39 Hz, and the 10 dB bandwidth is 68 Hz. At 1000 Hz, the voltage gain of the circuit measured 36 dB.

**Fig. 10** shows the frequency response of this circuit when tuned to 1000 Hz. High-frequency rolloff is quite good, being about 43 dB down at 2000 Hz, so this circuit can convert a 1000 Hz square wave into a very nice sine wave. Low-frequency response flattens out, however, to a value determined by the ratio of the 1.33 megohm resistor to the 1 megohm input resistor. Some highpass filtering would improve the low-frequency skirt considerably, however. No attempt was made to optimize this notch circuit as described previously be-


creasing the value of the tuning pot and decreasing the value of the 200k resistor results in self-oscillation when the pot is set near its low frequency extremity.

This article contains everything I know at the present time about this tunable notch filter circuit and its applications. I hope I have presented enough information for those interested to make good use of this valuable but little known circuit. All data was taken using a 600-ohm audio generator and an ac vtm with an input resistance of 10 megohms. If readers have questions or can further enlighten me on these circuits, I would be pleased to hear from them.

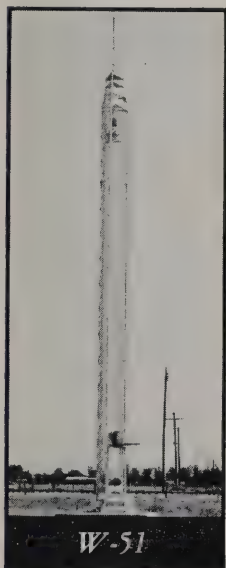
**ham radio**



**NOW.**  
*Top-of-the-Line*  
**Tri-Ex Towers**  
*for HAM operators*  
*at basic prices!*



**W-51**

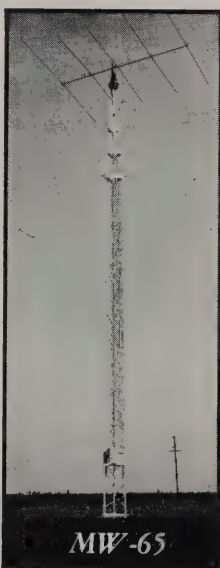


**MW-65**



**LM-470D**



**TM-370**

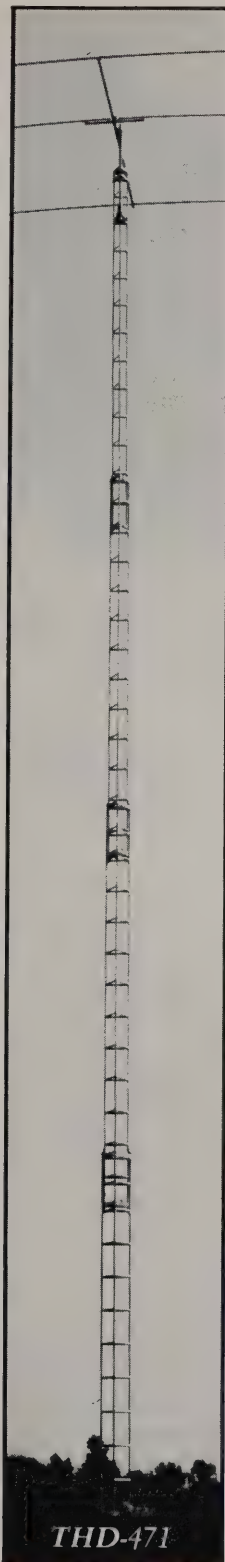

**THD-471**

Now you can afford the best! Free-standing or guyed, Tri-Ex Towers stress quality. All towers are hot dipped galvanized *after* fabrication for longer life. Each series is specifically engineered to HAM operator requirements.

### **W Series**

An aerodynamic tower designed to hold 9 square feet in a 50 mph wind. Six models at different heights.

### **MW Series**

Self-supporting when attached at first section — will hold normal Tri-Band beam. Six models.

### **LM Series**

A 'W' brace motorized tower. Holds large antenna loads up to 70 feet high. Super buy.

### **TM Series**

Features tubular construction for really big antenna loads. Up to 100 feet. Free-standing, with motors to raise and lower.

### **THD Series**

Very popular. Low Cost. Holds Tri-Band antennas. Eight models — all support 7 square feet of antenna at full height in 70 mph winds. Guyed.

Start with Top-of-the-Line Tri-Ex Towers. At basic prices. Write today, for your best buy.



**TOWER  
 CORPORATION**

7182 Rasmussen Ave.  
 Visalia, Calif. 93277

# optimization of the phase-locked RTTY terminal unit

The original design concept of the phase-locked loop RTTY terminal unit included totally automatic and universal operation requiring a minimum of adjustment. The initial design would copy any afsk shift between 150 and 100 Hz, operate at data rates up to 110 baud, and automatically track a drifting signal.<sup>1</sup> Another publication described a modified autostart system that incorporated an anti-CW feature.<sup>2</sup>

Since the original article was published there have been two distinct developments in amateur RTTY operation:

1. Wide shift (850 Hz) has almost completely disappeared from the high-frequency amateur bands with the exception of some operation on 80 meters (and, of course, wide shift is still the rule on two-meter fm).
2. The continued use of 60 wpm for 95 per cent of amateur RTTY operation, even with the availability of 75- and 100-wpm speeds.

This latter development is undoubtedly because of the vast amount of 60-wpm teleprinter machines available and the fact that most RTTY operators can't type more than 60 wpm.

With these two developments in mind, and in response to requests from readers, I've attempted to optimize the detector circuit to decrease the required minimum input-signal-to-noise ratio of 6 dB (for 99 per cent correct copy). In

consideration of users having commercially made printed-circuit boards,<sup>3</sup> one constraint was placed on the modifications: no printed-circuit changes would be necessary — only parts substitutions, deletions, and parts value modifications would be used.

## modifications

For the phase-locked loop detector (fig. 1) changes are shown circled. In the original loop, the lowpass filter capacitor, C7, was selected to give a loop bandwidth of approximately 400 Hz. This value was selected in compliance with Shannon's rule for operation at the highest data rate of 110 baud:  $110 \text{ baud} \div 2 = 55 \text{ Hz}$  signaling rate;  $55 \text{ Hz} \times 7 = 385 \text{ Hz}$ , or the required minimum loop bandwidth. But for 45-baud (60 wpm, 5 level), a 22.5-Hz signaling rate results, thus requiring a loop bandwidth of only 157.5 Hz. A 180-Hz loop bandwidth was used because 0.22  $\mu\text{F}$  was the nearest standard value capacitor to the design value for C7. To complement the preceding change, the phase-locked loop output RC ladder filter cutoff frequency was also lowered by increasing the value of C8, C9, C10 and C11 from 0.01 to 0.022  $\mu\text{F}$ .

The ssb position of the mode switch, S1, is now used for 170-Hz shift, and the vco frequency-set pot, R5, is adjusted for a natural vco frequency of 2210 Hz at TP-2 with no audio input applied to the TU. This new frequency setting allows the vco to swing symme-

P. Edward Webb, W4FQM, Digicom, 22 Hartshorn Avenue, Worcester, Massachusetts 01602



trically to either side of its natural frequency, thus reducing the probability of the loop unlocking on noise.

The *normal* position of the mode switch, S1, is used for 850-Hz shift and its pot, R6, is adjusted for a natural vco frequency of 2550 Hz at TP-2, as in the original article. Other shifts, such as 425 or 85 Hz, can be copied simply by adjusting the receiver frequency so that the shift is centered on the appropriate vco natural frequency.

In the tracking comparator, an RC network consisting of R11 and C12 is

C12 has been changed to a  $0.33 \mu\text{F}$  mylar, and R11 has been changed to 1 megohm to maintain the same time constant. To take advantage of the higher impedance presented by this RC network, U2 has been changed from a N5741T to a NE536T, an fet input op amp. The minimum detectable shift was measured at 40 Hz with an input-signal-to-noise ratio of 10 dB and a noise bandwidth of 3 kHz.

The tracking comparator output low-pass filter cutoff frequency has been decreased to 30 Hz to optimize the

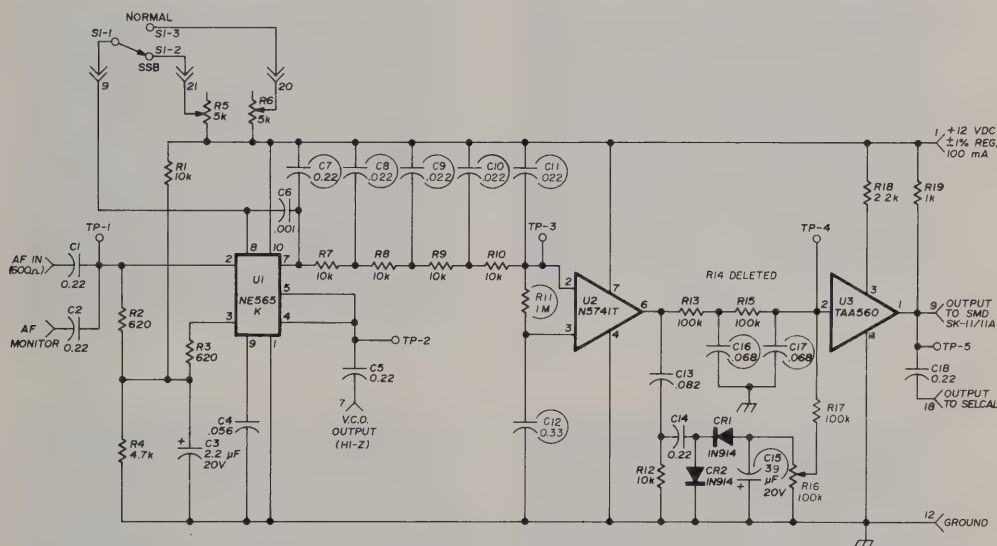


fig. 1. Circuit modifications to the phase-locked loop RTTY terminal unit for improved performance. New circuit values are circled. All resistors are 5%, 1/2 watt unless otherwise specified.

used to produce a signal-derived reference voltage for the noninverting input of U2. The RC time constant was selected to be 2.5 times that of the longest *space* condition at 60 wpm, which is the *blank* key having a *space* duration of 132 milliseconds. Accordingly R11 and C12 were selected to give a time constant of 330 milliseconds. However, the leakage path through electrolytic capacitor C12 limited the minimum detectable shift to approximately 150 Hz. Thus

section for the 22.5-Hz signaling rate used with 60 wpm, 5-level RTTY. To accomplish this frequency change, capacitors C16 and C17 were increased from 0.033 to 0.068  $\mu\text{F}$ . Also affected was resistor R14, which was deleted to produce a higher voltage to the input to the Schmitt trigger, U3, so that its operation on marginal signals would be improved. The noise rectifier in the noise squelch circuit was changed. The output filter capacitor, C15, was in-

creased from 10 to 39  $\mu\text{F}$  to provide a longer time constant, which reduced the effects of static crashes.

## experimental procedure

The phase-locked loop<sup>2</sup> TU was connected to a test setup (fig. 2). A Wavetek model 134 function generator was used to generate a 22.5-Hz square wave to simulate a 60-wpm, 5-level RTTY signal. This signal was fed through an

10, 1610, and 1960 Hz was imposed by the use of a Krohn-Hite dual electronic variable filter with both sections connected in series for highpass operation. These instrumentation methods gave simulated receiver bandpasses of 3000, 1200 and 500 Hz respectively.

All tests were started at a 10 dB s/n ratio, which was then reduced until the output of the Schmitt trigger (fig. 3, Channel 4) exhibited excessive jitter or

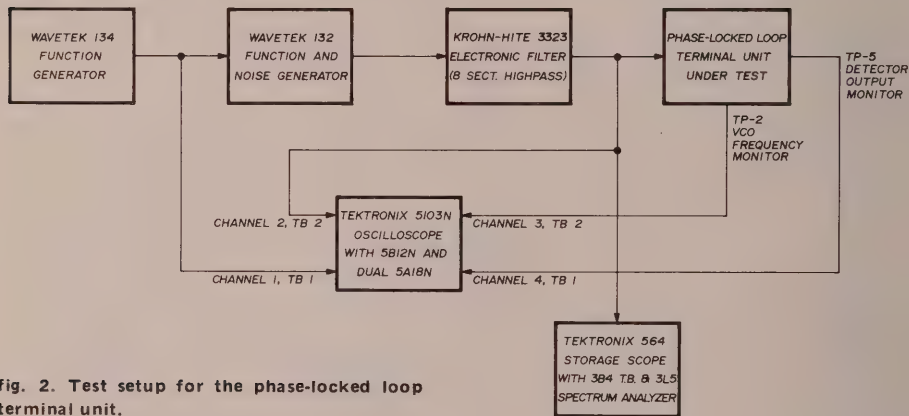


fig. 2. Test setup for the phase-locked loop terminal unit.

attenuator to the voltage-controlled generator input of a Wavetek model 132 function and noise generator. This latter instrument could simultaneously generate both a signal as well as random noise in a front-panel controlled, calibrated ratio. In these tests the signal used was an afsk sine wave shifted 170 Hz between 2125 and 2295 Hz, and a random noise sequence of  $2^{20} - 1$  was used at a maximum noise clock frequency of 48 kHz, thus ensuring that a random noise sequence could not repeat in a time period of less than 21.85 seconds.

Noise clock frequencies of 48, 45 and 39.3 kHz were used to produce upper noise bandwidths of 3, 2.81, and 2.46 kHz so that the signal-plus-noise bandwidth was always centered on 2210 Hz, which is the shift midpoint and the natural frequency of the phase-locked loop<sup>2</sup> vco. A lower bandwidth limit of



failed to follow the afsk keying signal (fig. 3, Channel 1). This s/n ratio was considered to be the minimum usable input signal for a given simulated receiver bandpass. The test results were: 0 dB minimum s/n for a simulated receiver bandpass of 3 and 1.2 kHz. For 500 Hz, it was -3 dB.
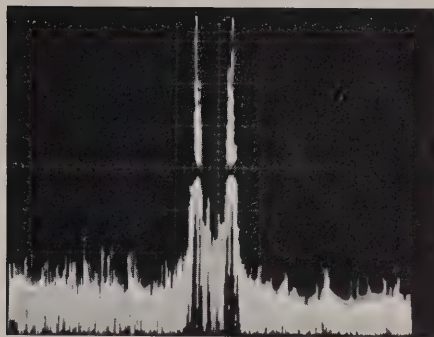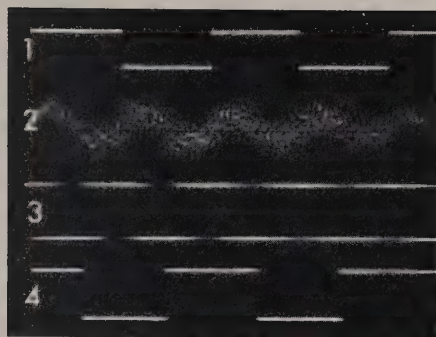
## conclusion



Figs. 3A, 3B and 3C illustrate the input and output waveforms for the test setup and TU with input s/n ratios of zero and -3 dB and simulated receiver bandpasses of 3, 1.2, and 0.5 kHz. These figures represent a 6-dB improvement for the worst case and a 9-dB improvement for the best case over the original design.

Comments, contribution of ideas, and criticism are welcome from users of phase-locked loop terminal units.







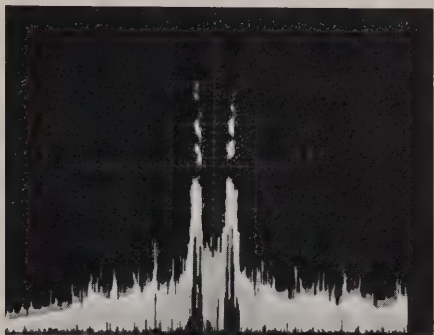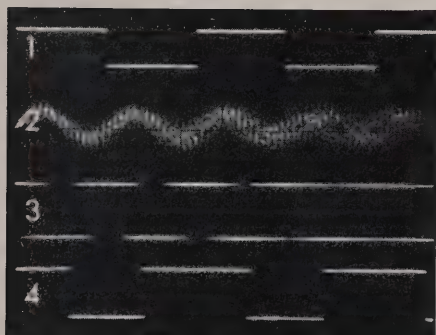A. 3-kHz noise bandwidth; signal-to-noise ratio, 0 dB.



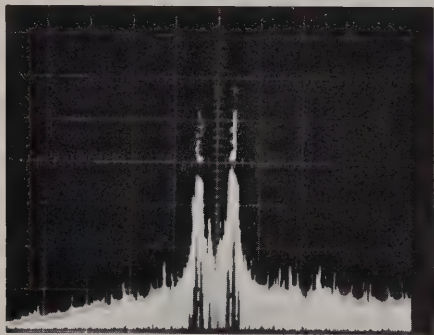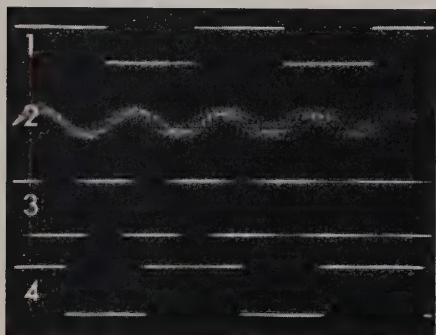B. 1.2-kHz noise bandwidth; signal-to-noise ratio, 0 dB.



C. 500-Hz noise bandwidth; signal-to-noise ratio, -3 dB.

Center frequency, 2200 Hz; dispersion, 200 Hz/cm; sweep speed, 5 sec/cm; vertical sensitivity, 200 mV/cm.

fig. 3. Input and output waveforms from test setup show improvements of 6 and 9 dB over original design for worst- and best-case conditions.

Channel 1: afsk keying voltage; horizontal, 10 ms/cm; vertical, 50 mV/cm.

Channel 2: signal + noise at 3 kHz bandwidth; horizontal, 0.2 ms/cm; vertical, 100 mV/cm.

Channel 3: PLL vco at TP-2; horizontal, 0.2 ms/cm; vertical, 10 V/cm.

Channel 4: Schmitt trigger output: horizontal, 10 ms/cm; vertical, 10 V/cm.

## acknowledgement

I'd like to express my gratitude to the Wavetek Corporation for making a Model 132 VCG/noise generator available for this and other research work in the biomedical field. The work reported here was greatly simplified by the use of this instrument.

## references

1. P. Edward Webb, W4FQM, "A Phase-Locked Loop RTTY Terminal Unit," *ham radio*, January, 1972, page 8.
2. P. Edward Webb, W4FQM, "An Anti-CW Autostart System For the PLL TU," 73, May, 1972, page 39.
3. Digital Communications Corp., 185 Devonshire, Suite 900, Boston, Massachusetts 02110.

ham radio

## toroidal coil inductance

Toroidal inductors are being used more and more in amateur communications equipment because of their small size, high Q and self shielding properties. Michael Gordon's article\* makes it relatively easy to determine the number of turns to wind a coil on a particular core. He includes numerous core constants and a helpful equation necessary to achieve a specific inductance. Fig. 1 contains much of that information in graphical form and was developed for builders who tend to shy away from using mathematical formulas. To determine the required number of turns on a particular toroid core, simply locate the

desired inductance, L, on the vertical axis, draw a horizontal line through L to where it intersects the appropriate core line, and read off the number of turns, N, on the horizontal axis, beneath the intersection point.

The graph of fig. 1 can be expanded to include more core types and a greater number of turns if desired. Fortunately, Gordon's expression  $N = K\sqrt{L}$  plots as a straight line on log-log graph paper; therefore, by using paper with more cycles, a more complete nomograph can be obtained. I constructed the original graph by rearranging the above formula into the form  $L = N^2/K^2$ , where K is one of the core constants, and then solved the equation for L when N is 20 and 100. This gives two points which can be connected by a straight line.

The dashed line shows actual measured values for an Amidon T50-2 core. Four test coils were wound using number-26 (0.4mm) enamel covered wire. A commercial Q meter was used to measure Q, and the inductance was calculated from the resonant frequency formula. The small discrepancy noted between the measured and calculated inductance values could have been due to connecting lead length and Q-meter accuracy.

Charles Miller, W3WLX

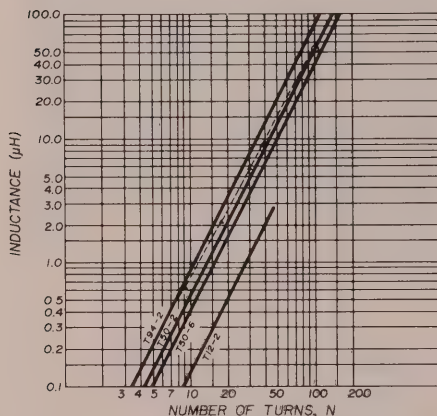


fig. 1. Inductance vs number of turns for four popular Amidon toroidal cores. Dotted line shows actual measured inductance values for a T50-2 core; discrepancy from calculated values is small.

\*Michael Gordon, WB9FHC, "Calculating the Inductance of Toroids," *ham radio*, February, 1972, page 50.



# Clegg HT-146

New Factory Direct Prices Make  
This The Best Value  
Ever In 2 Meter Hand-helds!

*Only \$197.25*  
*Shipping included*

*HT-146 Complete with  
Heliflex Antenna (BNC)*

*Mercury Battery*

*3 Pairs of Crystals*

*146.52 Simplex and any two  
pairs of your choice.*

*Add \$20.00 for Nicad Battery.*



## FOR MORE INFO

Phone toll free (800) 233-0250  
in Pa. Phone (717) 299-7221 collect

*Clegg*

208 Centerville Road

Lancaster, Pa. 17603

mastercharge

BANKAMERICARD

# single sideband speech splatter

An informative  
discussion of  
nonlinear ssb operation  
and what to do  
about it

If you've listened on the low-frequency end of the 20-meter phone band when two or three rare DX stations are coming through, you've probably noticed a steady, noise-like signal between the DX stations. Under good conditions the noise may be S2 or S3; more likely it's S9 or more. This steady noise seems to come from no particular station; in fact

it seems to emanate from all stations of the band. The noise is caused by splatter.

When only one station is causing splatter, it's a good bet the operator will be told his transmitter is at fault. Sometimes this brings an apology and an immediate resolution; often it brings a protestation of innocence based on the equipment in use: "My so-and-so off-the-shelf rig has super automatic level control; it can't be me." A cop-out response? Perhaps not. The fellow in question may not understand the causes and cure of splatter.

This article presents some hints on the causes, cure, and source of splatter interference and what can be done about it to help alleviate the noise problem in the congested amateur phone bands.

## source of splatter

Splatter comes from a single source; in fact a rather simple one. There is a relationship between the way a signal changes and the bandwidth it occupies. The relationship is easily described mathematically, but this does not lead to a good understanding of the process. For this discussion let's look at some


R. P. Haviland, W4MB, Box 45, Daytona Beach, Florida 32019

special types of signals and use these as analogies.

A simple example of a signal with a high rate of change is a pulse of width  $\Delta t$ , corresponding to a dot of a CW signal or to an ideal radar pulse. With respect to time, the signal is off for a long period, then on at constant strength for a period  $\Delta t$ , then off again for a long period. With respect to frequency, the relative strength of this signal varies with frequency; its spectrum is shown in **fig. 1**. Most of the signal energy is contained in the bandwidth defined by  $f = 1/\Delta t$ .

For example, suppose the pulse represents a dot with a width of 50 milliseconds and a dot speed of 24 words per minute. Most of the energy will be contained within a band 20-Hz wide. If the pulse is from a radar, having a width of 0.2 microsecond, most of the signal energy will be contained within a band 5-MHz wide. On a relative basis, the shape of these two signals is the same.

Both of these signals have additional peaks extending outward from this central band, as shown in **fig. 1**. These additional components are the source of key clicks on CW signals and the typical buzz of a radar signal when a receiver is tuned well away from center frequency.

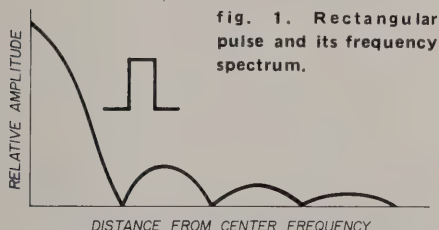


**fig. 1. Rectangular pulse and its frequency spectrum.**

The components extend far from the center frequency.

For a perfectly rectangular pulse, the magnitude of the components is defined by the relationship  $(\sin X)/X$ . This relationship is called the aperture function and is the envelope of the spectrum

amplitude for a single square pulse. The  $X$ , in this case, is  $\pi T_o f$ , where  $T_o$  is the pulse duration (seconds) and  $f$  is the frequency (Hz) at which it is desired to know how much signal amplitude exists. If the pulse duration is 0.1 second and you want to know how much splatter

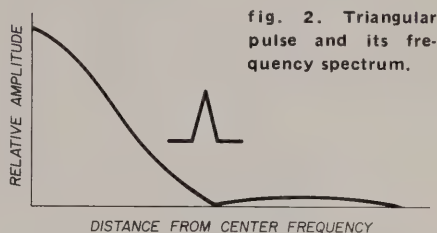

**fig. 2. Triangular pulse and its frequency spectrum.**

exists at, say, 100 Hz from center frequency, then

$$\pi(0.1)(100) = 10\pi$$

and

$$\frac{\sin 10\pi}{10\pi} = 0$$

There is no splatter at all at exactly 100 Hz from center frequency. However, if you ask about splatter 5 Hz from center frequency,

$$\pi(0.1)(5) = 0.5\pi$$

and  $(\sin \pi/2)/\pi/2 = 1/\pi/2 = 2/\pi = 0.636$ , or about two-thirds the signal you'd hear exactly on frequency.

The influence of this idealized signal extends over the entire band, from dc to infinitely high frequencies. The change in signal strength with frequency is slow. For example, if the maxima have a strength of 100 mV at 10 kHz from the center of the CW signal, they will have a strength of 50 mV at 20 kHz from the signal, 25 mV at 40 kHz, etc.

For a given pulse width and amplitude, the only way we can change the signal spectrum is to change the rate of change of the signal or rise time. This affects the strength of components far



from the center frequency of the signal without changing the main part of the signal very much. For example, suppose the pulse were changed from a perfect rectangle to the triangle of fig. 2. The energy distribution is now described by the relationship  $[(\sin X)/X]^2$ , but the

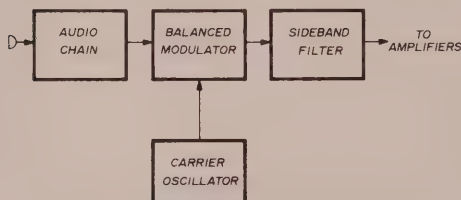


fig. 3. Block diagram of the basic filter-type ssb transmitter.

peak amplitudes far from center frequency decrease twice as fast as before. If the maxima are 100 mV at 10 Hz from center frequency, they will be 25 mV at 20 kHz; 6.25 mV at 40 kHz, etc. The energy very close to the center frequency is identical for the triangle and the rectangle. Other wave shapes can show greater reduction of the "far-out" components.<sup>1</sup>

This modification of wave shape and its effect on far-from-center frequency components is the principle of the key click filters used in CW. Note that the shaping can't stop key clicks — all it can do is reduce their strength and, in particular, reduce the strength of the components relatively far from the signal. For the 20-wpm signal, clicks beyond a few hundred Hz can be brought to the noise level or below.

The important point of this discussion is that any signal that goes on and off will spread across a band of frequencies. How far it spreads and how much energy occurs at each frequency is determined by the interval between on and off, the rate of change of the signal during the on period, and the maximum amplitude the signal reaches.

## ssb signal generation

Now let's apply these principles to ssb phone signals. We'll ignore some "fine structure," such as the effect of turning the transmitter on at the beginning and off at the end of a transmission. What we want to look at is how a signal supposedly contained within the speech bandwidth can appear many kHz from this nominal band: in other words, we want to know where splatter comes from. To do this let's look at how the signal is formed and processed.

Fig. 3 shows, in block diagram form, an elementary single-sideband transmitter. Audio and carrier are processed by the modulator to produce a double sideband suppressed-carrier signal. The modulator also produces distortion products at twice the frequency of the carrier, three times its frequency, etc. However, all of the signal outside the passband of the filter is rejected; therefore, only speech products lying between about 300 and 2400 Hz, plus the small amount of distortion that lies within this range, are passed on to the following amplifiers. At the output of

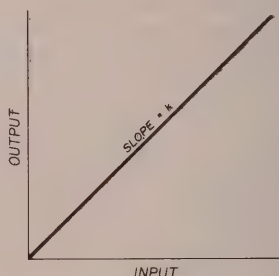


fig. 4. Ideal amplifier has linear relationship between input and output.

the filter the signal is free of widespread spurious components: it is splatter-free.

This nearly ideal signal is then amplified and finally transmitted. If the amplifiers are linear, no energy will exist outside the passband. That is, the amplifier output signals must bear a direct relation-


ship to the input signals. Each amplifier must follow the law

$$e_{out} = k(e_{in})$$

The transfer function of the amplifier must look like **fig. 4**. Unfortunately, most amplifiers don't attain this ideal relationship and this is where the trouble comes from. In looking at this, let's again remember we're not interested in "fine structure;" that is, distortion close to the transmitted signal or regeneration of the rejected sideband, or things of that kind.<sup>2</sup> We want to know the *source* of splatter.

### splatter due to flat-topping


One characteristic of practical amplifiers is that they saturate. The output reaches some maximum level then doesn't increase further. Instead of being linear they have the relationship shown in **fig. 5**. The effect on a typical signal is shown in **fig. 6**; it becomes amplitude-limited and is usually called flat-topped. The effect of flat-topping is the same as if the transmitter were putting out an ideal signal plus a

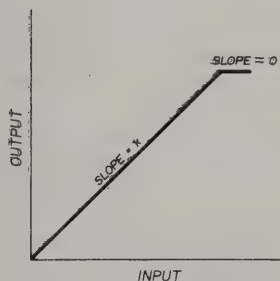

**fig. 5.** Input-output relationship of an amplifier which saturates.

negative-going pulse that cancels the top of the signal (**fig. 7**). The transmitter is now transmitting its intended signal and is also transmitting a radar-like pulse. Flat-topping generates splatter. Since speech waveforms last for relatively

short periods, and since only the tip of the wave is cut off, the radar-like pulse formed by peak clipping has a very short duration. Therefore, it spreads a long way from the desired signal and repeats at each voice peak, generating the sound amateurs call "buckshot".

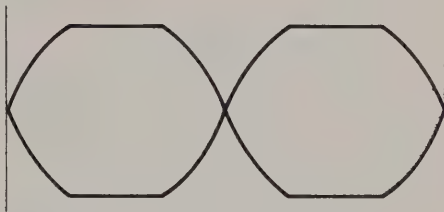

**fig. 6.** Ssb two-tone test with saturation.

Note that the signal close to the center frequency is perfectly good. Don't ask the station you are working if you are splattering; he can't tell since he hears a perfectly good signal. It's the station well removed from the center frequency who hears the splatter.

### splatter due to bias-off

Another characteristic of practical amplifiers is the tendency to ignore small signals. For a small input they show no output for a time. The transfer function tends to look as in **fig. 8**, which causes the bottom end of the signal to be clipped. Again, this is equal to a normal signal plus a distortion term. In audio amplifiers, where push-pull operation is common, this clipping is called crossover distortion. It also exists in single-ended amplifiers and is the result of improper bias adjustment — the bias is set too high — often in an attempt to reduce the tube idling current.

This form of distortion is less likely to cause trouble than that from positive peaks, since only a small part of the signal is affected. However, evidence indicates that the importance of this form of distortion has recently in-

creased as power companies lower line voltage or allow poorer line voltage regulation. These acts reduce the plate voltage (unregulated) but usually don't affect the bias voltage, since it is regulated. Effectively, the reduced line voltage increases the bias on the tube and therefore increases this type of distortion.

### splatter due to parasitics

Another characteristic of practical amplifiers is a tendency to oscillate, often at a frequency far from that at which they are designed to work. Sometimes this parasitic oscillation starts at a specific plate voltage and dies out when the voltage increases beyond this level or when it decreases below this level again. The effect on the input-output relationship can be as in fig. 9. Either of these oscillations will create splatter as the parasitic turns itself on and off. Very similar effects can appear if the

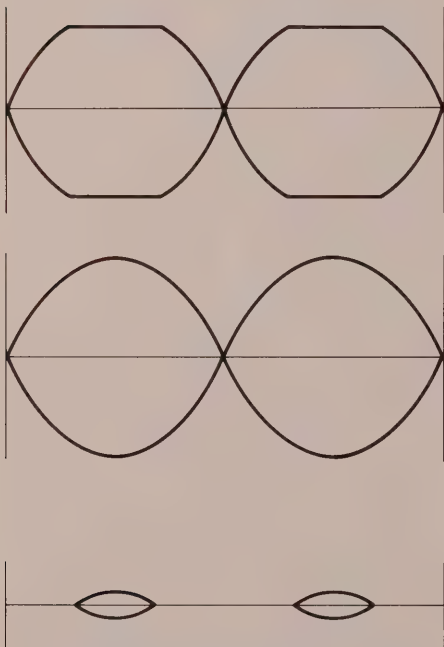


fig. 7. Flat-topping as the sum of an ideal signal plus pulses.

amplifier is merely unstable instead of oscillatory. This action causes the amplifier output to increase beyond its normal value, then level off, or perhaps even drop back to normal.

Problems of these types are very common when amplifiers are first tuned

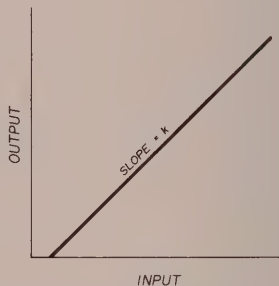


fig. 8. Input-output relationship of an amplifier with crossover distortion.

up. They may arise again because of components that become defective or change values: more commonly, they arise when an amplifier isn't adjusted properly or if it's operated with voltages appreciably different than those for which it was adjusted. It's likely that the really bad cases of splatter are due to such parasitic oscillations or instability.

### splatter due to level control

Let's go back to the flat-topping situation, which is the most common problem. A number of automatic means of preventing flat-topping have been developed. Most work by detecting a particular level of signal at the final amplifier and feeding the signal back to an earlier amplifier to reduce the gain. This scheme is called automatic level control, ALC, or overdrive detection. The intent of these systems is to reduce the value of  $k$  in the linear input-output relationship,  $e_{out} = k(e_{in})$ , to the point where linear operation is maintained — by keeping all peaks below the overload point.



Unfortunately there can be some problems with these automatic circuits. It takes a finite time for the overload signal to be detected, fed back, and for it to reduce the gain of the earlier stage. This time delay can also introduce a problem, as shown in **fig. 10**. The relatively sudden decrease from the initial value of  $k$  to a second value is just as effective in producing splatter as any other change of equal rate and magnitude. An associated splatter source may be the click of the vox relay pulling in: it's gone before the ALC circuits can act, but it can still produce splatter.

Some transmitters incorporate circuits to prevent these sudden changes from occurring. There may be several gain-controlled stages, or several control sources, with different time constants. These complex circuits definitely help prevent the rapid changes shown in **fig. 10**; however, even they can't cope with the results of a wide-open gain control. The transmitter struggles zealously but just can't prevent splatter from occurring.


### splatter due to the receiver

To be complete, we should note that receivers also include some linear stages, and can have almost identical problems. Problems arise if these stages are overloaded, unstable, or if the automatic gain control circuit time constants don't match the rate of change of a particular signal being received. Splatter reports can be generated in the receiver, so that a false report is perfectly possible. If you're told you're splattering, it's in order to ask about the precautions against receiver overload, assuming your transmitter is operating linearly.

### detecting your own splatter

Many stations are equipped with an oscilloscope or monitor. This is by far the best way to operate, but it's necessary to be cautious. A scope won't show all splatter problems. Example: suppose

two transmitters are operating. One is an ssb transmitter with two-tone modulation. The second is an a-m transmitter 100 percent modulated by the unfiltered output of a full-wave rectifier. As seen on a monitor scope, what is the difference between these two signals?

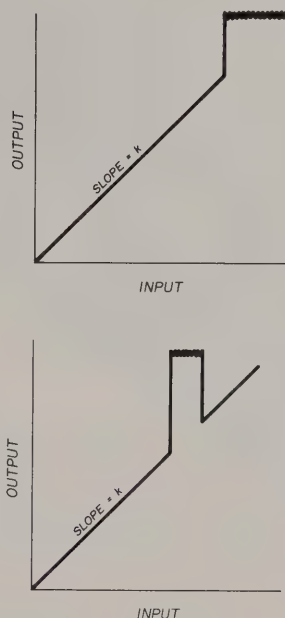

**fig. 9.** Input-output relationships of an amplifier with parasitic oscillations.

The answer is that, to casual inspection, there is absolutely no difference. Both look like the ideal signal of **fig. 7**. Even detailed inspection of the envelope will not show any difference. The only way a scope can detect the difference is to look at the rf waveform. When this is done, a phase reversal will be found at each zero crossing of the envelope for the two-tone test: the rf wave of the a-m signal doesn't show this reversal. This very small difference won't show up on any of the usual types of signal monitor; yet the difference as seen by outside receivers is enormous. The two-tone ssb signal is clean while the recti-

fier-output modulated a-m signal spreads to many, many times the frequency of the modulating sine wave.

Fortunately this situation is artificial but it does show that casual observation of the scope is not enough; some attention to detail is necessary. The first

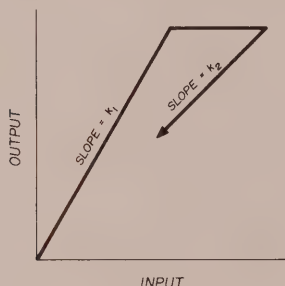


fig. 10. Input-output relationship of an amplifier with poor automatic leveling control.

point to watch for is flat-topping, usually the only item observed. Sharp peaks of the voice signal are a good indication that splatter is not occurring from flat-topping. However, splatter due to parasitics or to instability can cause a pattern that resembles, very closely, the sharp peaks of a voice pattern. It takes careful examination of the signal, and, in particular, examination of the *rate of rise* around the midpoints of the signal, to detect splatter-producing parasitics. The type of splatter that arises from sharp changes at the lower signal levels is also detectable on the scope, but also only by careful observation. The rule should be, inspect the *entire* signal, not just peaks.

Many operators with stations using transmitters incorporating automatic level control (ALC) eliminate the scope and place their dependence on the automatic circuits. As long as the circuits are working properly and the transmitter is adjusted properly, this is satisfactory. The circuits do work if given half a chance; however, the practice of turning


the gain fully open is responsible for much splatter. The gain control should be set to give ALC action as recommended by the instruction book.

Stations using transmitters without ALC and no scope have a special problem. It's almost impossible to detect splatter generation by reading the meters on the transmitter. About the only automatic way of preventing splatter is to choose an exciter that can't overdrive the amplifier. In most cases, this means limiting the exciter power to about one-tenth to one-twentieth the power of the final amplifier. If the final is to run 1000 watts input, the exciter should run no more than 50-100 watts input.

#### references

1. *Reference Data for Radio Engineers*, Fifth Edition, "Fourier Waveform Analysis," page 42-1.
2. Marv Gonsior, W6VFR, "Intermodulation Distortion Measurements on SSB Transmitters," *ham radio*, September, 1974, page 34.

ham radio

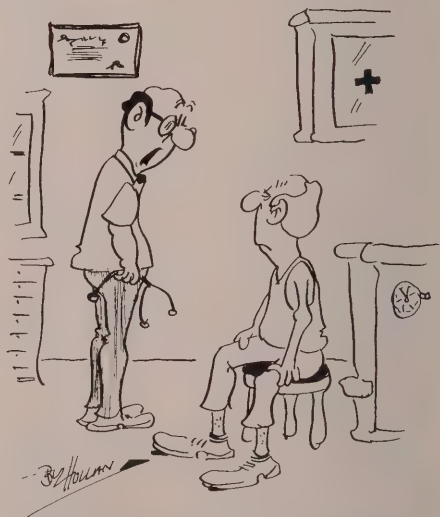

"Let me put it this way. If you asked me your QSA, I'd give you about a 2-3-1."

**YAESU****DIGITAL RECEIVER****FR-101**

14313.2

**MHZ****KHZ**

# Amateur radio's new look.

The new look in amateur radio is digital readout. And in the FR-101 digital receiver from Yaesu, you can check frequency with just a glance. If you're searching for a whisper of a QSL from across the world, you can be sure you're on the right wave-length every time.


The FR-101 digital receiver is accurate to an incredible 100 Hz. And there's a provision for up to four crystal-controlled channels in each of eight band segments. Added options allow up to twenty-one 500 KHz frequency ranges from 1.8 MHz all the way up to 148 MHz with reception of SSB, CW, AM, RTTY and FM modes.

Whether you're interested in two-way communications or listening in on the world, hear it all with the receiver that sports amateur radio's new look — the FR-101 digital receiver. Backed by a solid warranty, a strong dealer and service network — from the world's leading manufacturer of amateur radio gear, Yaesu. See the FR-101 digital receiver at your nearest Yaesu dealer or write for our catalog. Yaesu Musen USA Inc., 7625 E. Rosecrans Blvd., No. 29, Paramount, California 90723.



**YAESU**  
***The radio.***



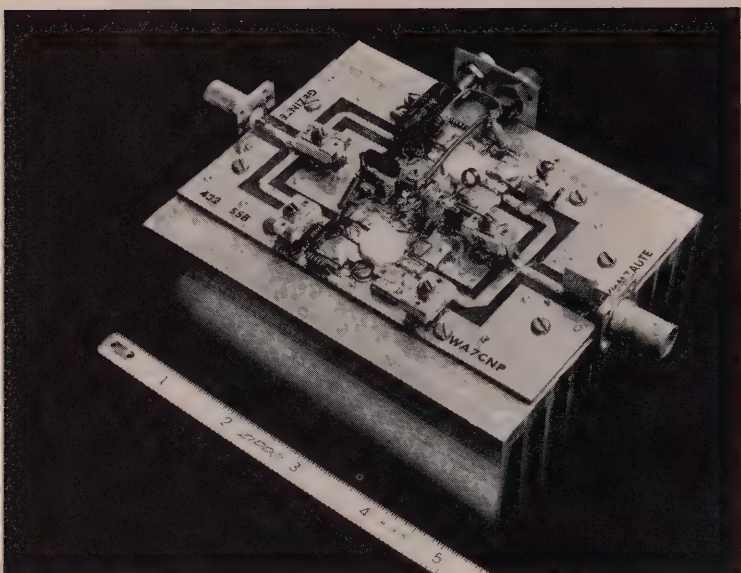

# 100-watt solid-state power amplifier for 432 MHz

Design and construction  
of a 100-watt  
solid-state  
power amplifier  
for linear, CW,  
or fm service

R. Keith Olsen, WA7CNP\*

There has been a tremendous increase in ssb activity on 432 MHz since the launch of Oscar 7 in late 1974. However, many amateurs who are communicating through Oscar's 432-to-144-MHz translator are using only 5 to 15 watts ssb output on 432 MHz so they must use complex, high-gain antennas to hold a good signal through the satellite. Few 432-MHz power amplifier designs have appeared in print, and because of mechanical considerations, vacuum-tube amplifiers are difficult to build at this frequency. This article describes a two-transistor, 100-watt PEP, solid-state linear amplifier which solves many of these problems. The components used in the amplifier, for the most part, are readily available.

\*RF Power Circuits Engineering, Motorola Semiconductor Products Division, 5005 East McDowell Road, Phoenix, Arizona.

The transistors used in this power amplifier are the new high reliability Motorola MRF306s. The MRF306 is a 28 volt, 60 watt, 225 to 400 MHz power transistor and is unique in that it is internally matched for broadband use. Internal matching is nothing more than extending the matching network to the actual chip inside the package. This is accomplished by incorporating the bond wires and additional MOS capacitors as tuning elements between the base lead and the transistor die (fig. 1). The ladder network transforms the input impedance of the device in a controlled manner so it represents a low loaded Q at the frequency of use, hence the name, "Controlled Q Transistor."

Gold metalization is used inside the MRF306 to provide high reliability, ruggedness, and long life. The device can withstand a load vswr of 30:1 at all phase angles at 60 watts CW output. This kind of ruggedness offers burnout protection against hazards such as a forgotten antenna connector or even a mislaid screwdriver!

## theory of operation

The power amplifier described here is essentially a narrowband, parallel amplifier that can be tuned from 420 to 450 MHz. For conventional ssb use, a push-pull configuration should be employed; in this case, however, both transistors are being driven at less than what they are capable, and operate in the class AB linear mode. Fig. 2 is a spectrum display of a two-tone test I ran on the amplifier. The center frequency is 432 MHz, the two tones are spaced 500 kHz apart, and power output is 100 watts PEP. The drive level is approximately 10 watts PEP.

As you can see, the 3rd and 5th order intermodulation products are down 28 dB. IMD responses greater than -30 dB can be attained by running the amplifier at lower power levels (see fig. 3), but since 100 watts is intended to be the "worst-case" condition, I chose

to demonstrate its response there. I might add that you should always pay very close attention to the linearity of any amplifier, especially when operating in crowded bands or when using one of the OSCAR satellites. When you operate an amplifier too close to the saturation point of the curve, you not only increase the incidence of spurious emission, your ssb signal also becomes mushy and distorted.

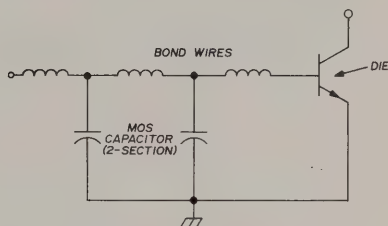


fig. 1. The MRF 306 power transistors used in this amplifier use a ladder network between the base lead and the transistor die to transform the input impedance of the device so it represents a low Q at the frequency of use.

This power amplifier can also be used on CW and fm. When I first built the amplifier I biased it into class C, and was able to drive and sustain 140 watts of output power for more than 30 minutes (I cheated a bit by using a fan because the ambient temperature of the heatsink can rise above 80°C). If you wish to use the amplifier for either CW or fm, and not on ssb or a-m, you can replace the class AB bias circuit with a ferrite bead and a four-turn inductor from the base of each device to ground as shown in fig. 5A. The devices can be driven further into class C by placing a 2.7 ohm, ¼ watt resistor between the inductor and ground (fig. 5B). This resistor is required only if you desire greater efficiency or have a greater drive level capability.

## construction

The amplifier is built on 1/16 inch (1.5mm) thick double-clad G10 epoxy-

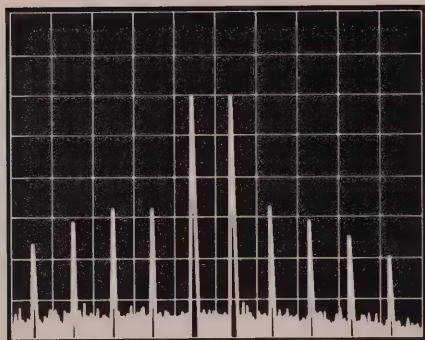


fig. 2. Spectrum display of 100-watt amplifier at 432 MHz shows 3rd and 5th intermodulation distortion products are down 28 dB referenced to 100-watt output (each vertical division = 10 dB).

glass printed-circuit board. I normally design with 1/16 inch (1.5mm) thick glass-teflon board, but at \$135 a sheet it's a bit expensive for amateur radio projects. Epoxy-glass circuit board is somewhat lossy at 432 MHz, but is still quite acceptable for amateur use considering the cost differential.

However, it is imperative that you use double-sided board. It is also important that the ground on the bottom side be tied closely to the ground pads on the top side. This is accomplished by using either eyelets or plated-through holes from one side to the next. If you don't have eyelets you can do it by drilling holes through the board with a number-50 (1.8mm) drill; you then place number-18 or -20 (1.0 or 0.8mm) wire through the holes, solder both ends, and trim them off flush with the circuit board. I recommend that you make such a connection under each Unelco capacitor. As for the holes for the transistor flanges, a good drill, a file, patience, and a little elbow grease are all that is necessary.

The Unelco metal-clad mica capacitors have a dual purpose. Not only are they important to the input and output networks, they also serve as supports for the transistor leads. The Unelco capacitors are a bit expensive, but at these frequencies they cannot be replaced by

anything other than porcelain chip capacitors such as those manufactured by ATC.

The transistors should *always* be screwed down to the heatsink (thermal compound underneath) *before* soldering the leads as it is possible to crack or break off the ceramic cap of the device. (The clearance holes in the flange are made for 4-40 [M3] screws.) Once this is done, the base and collector leads can be connected to the microstrip with 2 to 5 mil (0.05 to 0.10mm) thick copper or brass strap. Be sure that the width of the strap does not exceed the width of the microstrip.

The Arco variable mica trimmers work surprisingly well at uhf. Piston variables are better suited for uhf work, but here again the price tag is prohibitive. When you look at the bottom of the Arco variables you will notice that there are two small grounding tabs on each side. These tabs must be soldered to the ground plane to reduce the amount of lead inductance inherent in the capacitor. Be careful, when installing the capacitor, to make sure it doesn't short out the microstrip.

The collector and base biasing circuits are best placed between the two devices in the center of the board (see fig. 6). The 580 pF feedthrough capacitor, C12, is mounted on a piece of 0.7x0.4 inch (18x10mm) copper strap.


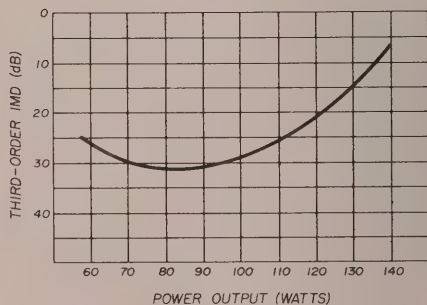


fig. 3. IMD performance of the 100-watt 432-MHz power amplifier vs output power ( $V_{CC} = 28$  Vdc, quiescent collector current = 100 mA).

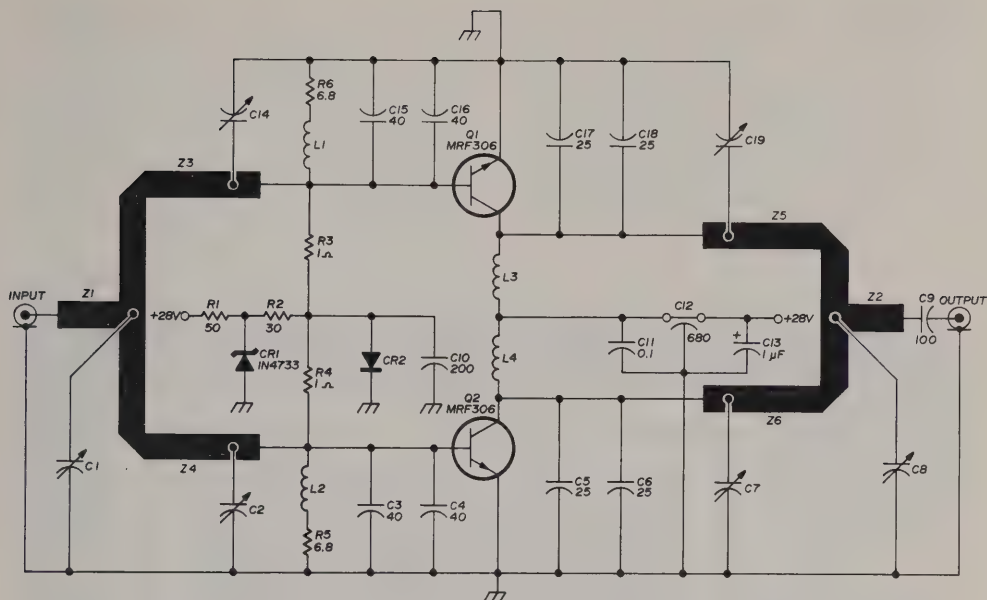



- |             |  |          |  |
|-------------|--|----------|--|
| C1, C2, C14 | 20 pF mica trimmer (Arco 402)                | C17, C18 | 25 pF metal-clad mica capacitor (Underwood)                            |
| C3, C4      | 40 pF metal-clad mica capacitor (Underwood)  | CR2      | 1 amp silicon diode with 0.6 volt forward drop (Motorola MR501)        |
| C5, C6      | 25 pF metal-clad mica capacitor (Underwood)  | L1-L4    | 4 turns no. 22 (0.6mm) enameled wire, closewound on 1/8" (3mm) mandrel |
| C7, C8      | 40 pF mica trimmer (Arco 403)                | R1       | 50 ohm, 5 watt   |
| C9          | 100 pF metal-clad mica capacitor (Underwood) | R2       | 30 ohm, 1 watt   |
| C10         | 200 pF metal-clad mica capacitor (Underwood) | R3, R4   | 1 ohm wirewound, 1/4 watt  |
| C11         | 0.01 $\mu$ F disc ceramic, 100 V             | R5, R6   | 6.8 ohm, 1/4 watt  |
| C12         | 680 pF Allen Bradley feedthrough capacitor   | Z1       | Microstrip 0.11" (3mm) wide, 0.75" (19mm) long                         |
| C13         | 1 $\mu$ F tantalum, 50 V                     | Z2       | Microstrip 0.11" (3mm) wide, 1.3" (33mm) long                          |
| C15, C16    | 40 pF metal-clad mica capacitor (Underwood)  | Z3, Z4   | Microstrip 0.11" (3mm) wide, 2.3" (58.5mm) long                        |
|             |  | Z5, Z6   | Microstrip 0.16" (3mm) wide, 1.7" (43mm) long                          |

fig. 4. Schematic diagram of the solid-state 100-watt linear amplifier for 432 MHz. This amplifier may also be used on fm or CW by replacing the class AB bias circuit with a ferrite bead and inductor as shown in fig. 5.

A 0.192 inch (5mm) hole is drilled through the strap for insertion of the capacitor and a small right-angle bend is placed in the strap so it can be soldered upright on the board.

The 1  $\mu$ F tantalum capacitor, C13, is connected on the side which is elec-

trically closest to the power supply. The 0.1  $\mu$ F disc capacitor, C11, is connected on the other side of the feedthrough. The collector chokes L3 and L4 come straight off the feedthrough to a point on the collector leads as close as possible to the cap of the devices.

## bias circuit

As you may or may not know, the  $h_{FE}$  (dc current gain) of transistors will vary from device to device but will always stay within a prescribed tolerance. As a result of some laborious experimentation, I have determined that the

biasing scheme used in this amplifier will keep the MRF306s biased between 20 and 50 milliamps of quiescent collector current. This variation in quiescent current has little or no effect in IMD performance but does have a small effect on gain.

The placement of the 1-ohm wirewound resistors, R3 and R4, is not as critical as that of the collector chokes; it is still advisable, however, to have the bias brought in as close to the transistor package as possible. Remember, too, that the 1-ohm wirewound resistor acts as an rf choke. Carbon varieties will not work in this application.

It is necessary to use approximately 100 nH of inductance in series with the 6.8 ohm resistors, R5 and R6, as they are carbon-composition resistors. The junction point of diode CR2, resistors R2, R3 and R4, and capacitor C10 use the isolated tab of the Unelco capacitor as a standoff. The anode lead of the zener diode, CR1, may be soldered directly to the circuit board. The cathode lead then serves as a tie point for

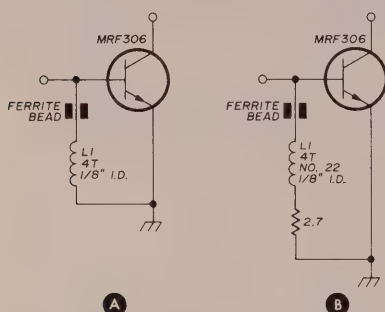


fig. 5. Power amplifier can be operated in class C for fm and CW by connecting a ferrite bead and inductor from the base of each device to ground as shown in (A). The devices can be driven further into class C by adding the 2.7 ohm series resistor as in (B). Inductor L1 is 4 turns no. 22, 1/8" (3mm) inside diameter.

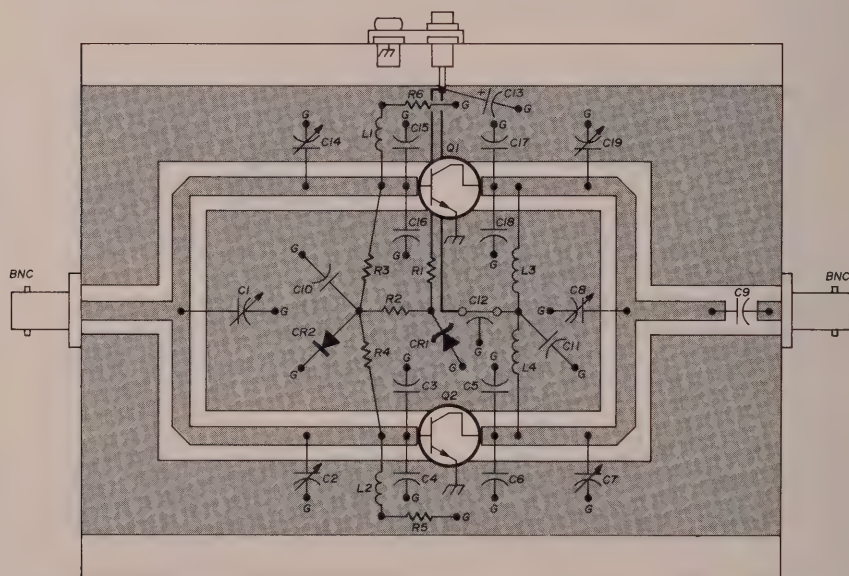


fig. 6. Component placement for the 432-MHz power amplifier. Full-sized printed-circuit board is shown in fig. 7.

resistors R1 and R2. The other end of resistor R1 is connected directly to +28 volts.

Finally, the 100 pF series capacitor in the output, C9, is mounted by placing it on its side on the microstrip with its isolated tab connected to the BNC output connector. This capacitor pre-

vents and sufficient voltage regulation to prevent gross  $V_{cc}$  fluctuations during load and no-load conditions, as encountered during modulation. Fig. 8 is a basic block diagram of a simple power supply that meets these requirements for this amplifier.

The transformer should provide from

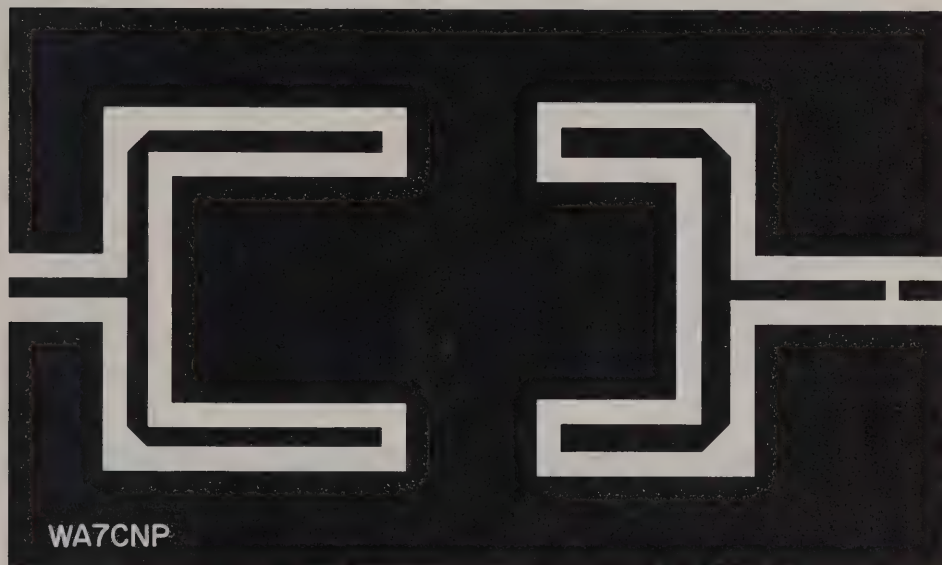


fig. 7. Full-sized printed-circuit layout for the 100-watt linear power amplifier. Component placement is shown in fig. 6.

sents only a small impedance bump in the collector load circuit. Its main purpose is to prevent shorting the dc power supply to ground when using a dc grounded antenna such as a Yagi.

### power supply

Let's digress for a moment and give consideration to a subject that is often neglected in articles such as these: A good power supply. Good IMD response is not only dependent upon bias, a good linear device, and proper collector loading, but also on a power supply that is capable of following the load changes presented by ssb operation. The power supply should have enough current capacity to handle peak current require-

ments and sufficient voltage regulation to prevent gross  $V_{cc}$  fluctuations during load and no-load conditions, as encountered during modulation. Fig. 8 is a basic block diagram of a simple power supply that meets these requirements for this amplifier.

Tune-up of the amplifier is not as tricky as it may seem, although it will require a little caution at first. It is advisable, if you have a means of varying the drive level, that you begin by applying only 3 to 5 watts to the input. It is very important that you get the



collectors loaded to a "ball park" point before you start pouring on the coal.

When you first begin tune-up, adjust the input trimmers until you see a small deflection of output power. Then immediately adjust the output trimmers for peak output, ignoring the input match for the moment. The best way to adjust the output is to adjust C8 for a peak before adjusting C7 and C19. Capacitors C7 and C19 should be adjusted so that both Q1 and Q2 are equally sharing the load. Once you have a reasonably good collector load established, you can go ahead and do the same to the input match.

You will notice that, as output power increases, the output circuit will require small amounts of adjustment. This is because the required collector load impedance changes slightly as power increases. A small decrease in


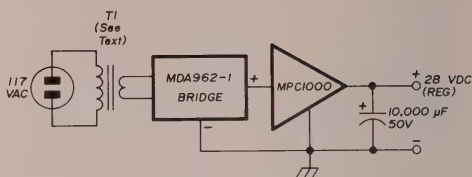


fig. 8. Basic block diagram of a regulated 28-volt supply for the 100-watt solid-state power amplifier. The Motorola MPC1000 is a positive voltage regulator designed to deliver up to 10 amps dc.

capacitance will probably be required on all the output trimmers as output power comes up. Alternately adjust the input and output circuits until you have reached your desired operating point (around 100 watts output).

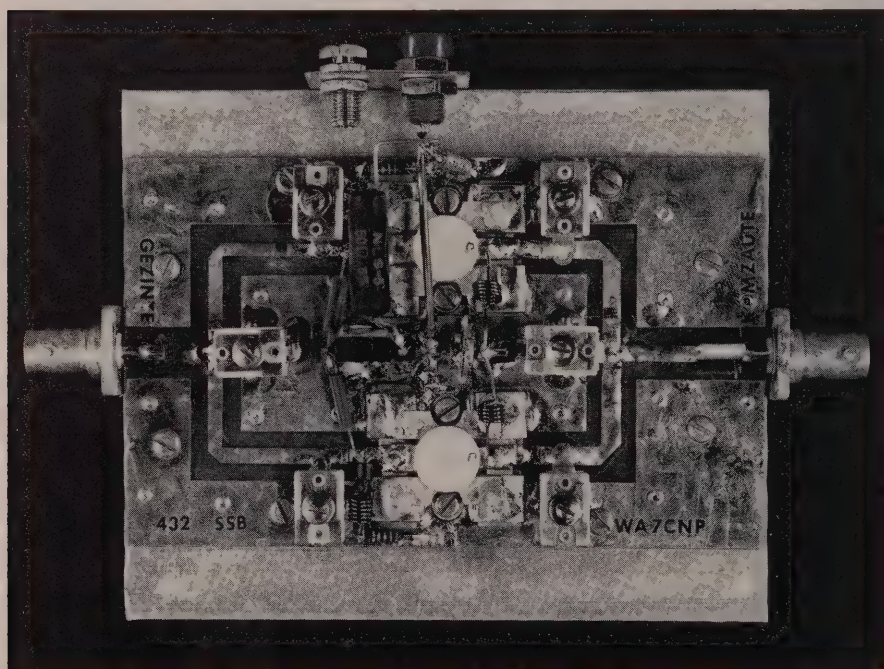The collector current should be between 6 and 8 amps depending upon the operating frequency. Capacitor C8



Top view of the solid-state 100-watt 432-MHz power amplifier, showing placement of the various components. Component designations can be easily correlated with the printed-circuit layout diagram in fig. 6. Input is at the left.

may be adjusted for slightly better efficiency but be careful not to drive the amplifier above 100 watts PEP output as severe flattopping will occur in the output waveform.

I hope you find this amplifier to be a useful tool in extending the capabilities of your 432 MHz station. There are many ways that this amplifier can be made to work even better, but it was my desire to make it as simple and in-

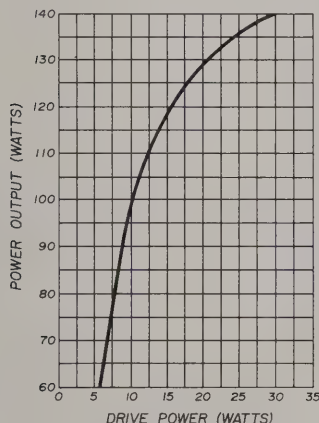



fig. 9. Plot of drive vs output power for the 100-watt 432-MHz power amplifier operating in class AB ( $V_{CC} = 28$  Vdc). Note that the knee of the curve is just above 100 watts output; this corresponds to the rolloff in IMD performance shown in fig. 3.

expensive as possible without seriously degrading performance.

A lot of the technology employed in solid-state power devices and amplifier design is new to amateur radio (and to industry as well) but as soon as technical publications and education programs can get geared up to this new technology, this type of work will become more and more commonplace. It should be the job of amateurs who are familiar with this technology to show the rest how it is done, and also to be the first ones to improve its implementation.

ham radio

## NEW FROM MFJ

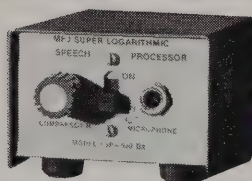

### SUPER LOGARITHMIC SPEECH PROCESSOR MODEL LSP-520BX

**400% MORE RF POWER** is yours with this plug-in unit. Simply plug **LSP-520BX** into the circuit between the microphone and transmitter and your voice suddenly is transformed from a whisper to a **DYNAMIC OUTPUT!**

Look what happens to the RF Power Output on our NCX-3. It was tuned for normal SSB operation and then left untouched for these "before" and "after" oscillograms.



Fig. 1 SSB signal **before** processing. See the high peaks and the low valleys. Our NCX-3 is putting out only 25 watts average power.

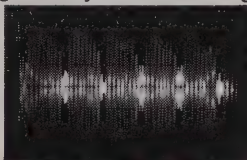


Fig. 2 SSB signal **after** processing with LSP-520BX. The once weak valleys are now strong peaks. Our NCX-3 now puts out 100 watts of average power.


Three active filters concentrate power on those frequencies that yield maximum intelligibility. Adds strength in weak valleys of normal speech patterns. This is accomplished through use of an IC logarithmic amplifier with a dynamic range of 30dB for clean audio with minimum distortion.

This unit is practically distortion-free even at 30dB compression! The input to the LSP-520BX is completely filtered and shielded for RF protection.

Size is a mere 2 3/16H x 3 1/2W x 4D. Money back if not delighted and **ONE YEAR UNCONDITIONAL GUARANTEE.**

Order now or write for **FREE** brochure.

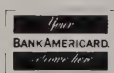**LSP-520BX** ..... **\$49.95**  
ADD \$1.50 SHIPPING & HANDLING




DEALER INQUIRIES  
INVITED  
**601-323-5869**



## MFJ ENTERPRISES

P. O. BOX 494(H)  
MISS. STATE, MS 39762

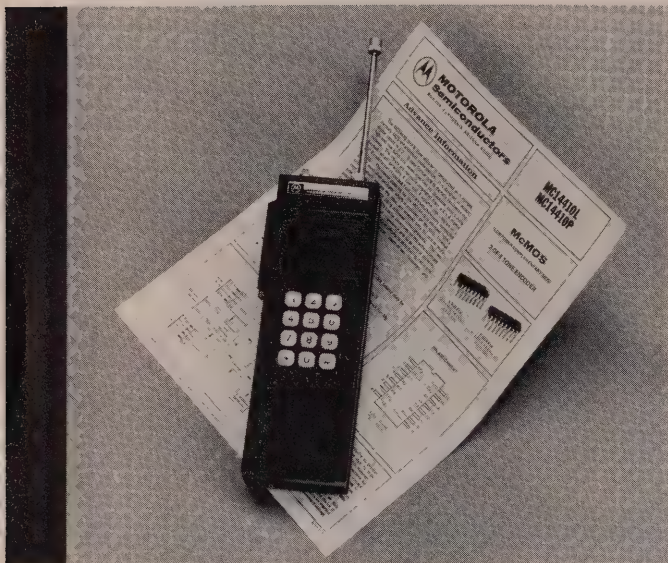

## hand-held touch-tone

New Motorola  
tone-encoder IC  
is the basis for  
this miniature  
Touch-Tone encoder  
for use in  
hand-held fm  
transceivers

Al Lowenstein, K7YAM, Motorola Semiconductor

The continuing increase in the popularity of autopatches, on both two meters and 450 MHz, coupled with the large number of hand-held fm transceivers now available, has generated the need for a truly compact tone encoder. With the introduction of a single-chip IC for this purpose, the handie-talkie Touch-Tone is now a practical achievement and for less than \$35 you can enjoy all the benefits of your autopatch while operating portable with a handie-talkie.

The Motorola MC14410 is a complementary mos IC and is functionally a 2-of-8 tone encoder or Touch-Tone.<sup>1</sup> It is available in both plastic and ceramic packages, but for amateur purposes there is no reason to pay the premium for the ceramic package. Designed for 4.4 to 6 volts, it will withstand moder-



Unlike many other hybrids available today, the MC14410 is not susceptible to rf interference, so close proximity to the transmitter is no problem. The board shown here was designed to slide into the PL area of an Omni-housing Motorola HT220 radio. Fortunately, it is small enough to be tucked away in some corner of almost any fm transceiver. The crystal can be remoted on pigtails, and does not have to be mounted on the printed-circuit board, but can be located wherever space is available.

Any good PC board material can be used for the circuit board. Since the solder pads are small, a board with good adhering foil is necessary; the phenolic materials seem to lack this attribute. Use a number-64 (0.9mm) drill and a high-speed drill motor to avoid tearing the pads. The IC should be soldered in last to avoid any possible static build-up

on the MOS devices. Use a soldering *iron*, not a gun. Pins 1 and 7 are clipped off as they are not used.

board first; Teflon insulated wire is easier to work with because the insulation doesn't melt at soldering temperatures. The double pad on pin 11 of the IC is for the fourth column tone if you have a 4x4 keyboard — it was not needed here.

CHOMERICS  
ER-21623  
TOUGH-TONE PAD

Y1  
1 MHz 0.1%

R1  
5M-15M

U1  
MC14410

R2-56k

R3  
56k

R4  
20-50k

C1-1 μF

CR1 (SEE TEXT)

OUTPUT

ON

1 μF

1 μF

\* ALTERNATE FOR C1

tor, C1, must be a nonpolarized unit. An alternative is to use two 1- $\mu$ F electrolytics in parallel with reversed polarity. Since the output is approximately 25 kilohms to ground, the capacitor can be tied directly into the audio line.

A zener diode, CR1, is used to limit the voltage to the IC at high battery

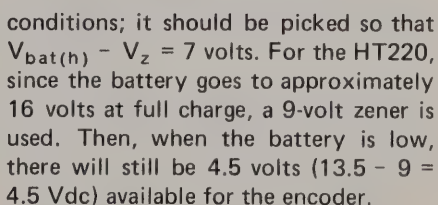




fig. 3. Full-size printed-circuit board for the miniature tone encoder.

The Chomerics ER-21623 pad pins must be clipped to approximately 1/8 inch (3mm) so they will clear the components of the HT220. Remove the fuse in the HT220 front cover from its clip while cutting the slots for the pins. An Xacto saw works well after pilot holes have been drilled; a Dremel Mototool could also be used. Extreme neatness isn't necessary as the Chomerics pad will completely cover the slots after it is epoxied into place.

The four plastic pins at the corners of the pad should be cut off and filed flush with the case. Fit thin pieces of cardboard around the pin areas to support the pad (see fig. 4). The pad is then epoxied to the front of the radio. Be sure to roughen the plastic of the radio with fine sandpaper to insure a good bond. Also, be careful to only epoxy the four edge rails of the pad. A little goes a long way, and epoxy can seep around the inside edges of the pad and make it inoperative.

After the epoxy has hardened, you are ready to put it all together. The pins of the pad should be tinned using a good clean hot iron. Do not overheat the pins as they will come free internally from the pad, resulting in erratic or no operation. The eight wires from the circuit board can then be soldered

to the keyboard. The B+ supply, ground and audio are picked up as shown in the photograph. The difficult part is stuffing in all those wires in. A gentle loop between the front cover and main circuit board will suffice, and there don't appear to be any detrimental effects from having the eight wires right next to the radio circuitry.



Interconnect points for the Touch-Tone encoder installed in a Motorola HT-220.

The output potentiometer, R4, should be adjusted to produce a 4 to 5 kHz final frequency deviation when one key is depressed. This assumes, of course, that the radio's modulation causes a similar deviation during normal voice operation. Note that the microphone is live, so use precautions while dialing.

#### reference

1. Jon DeLaune, W7FBB, "Digital Touch-Tone Encoder for VHF FM," *ham radio*, April, 1975, page 28.

ham radio

CHOMERICS  
ER-21623



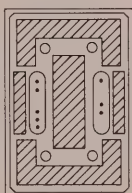


fig. 4. Cardboard inserts (hatched areas) are used to support the Chomerics Touch-Tone pad (see text).
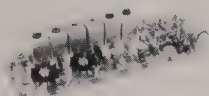
# The world's most complete line of VHF - FM kits and equipment





|                  |                                   |       |
|------------------|-----------------------------------|-------|
| TX144B Kit . . . | exciter — 1 watt — 2 meters . . . | 29.95 |
| TX144B W/T . . . | factory wired . . .               | 49.95 |
| TX220B Kit . . . | exciter — 1 watt — 220 MHz . . .  | 29.95 |
| TX432B Kit . . . | exciter — NEW — 432 MHz . . .     | 39.95 |

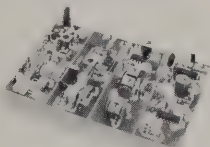


|                  |   |        |
|------------------|---|--------|
| RX50C Kit . . .  | 30-60 MHz rcvr w/2 pole 10.7<br>xtal filter . . .     | 59.95  |
| RX144C Kit . . . | 140-170 MHz rcvr w/2 pole<br>10.7 xtal filter . . .   | 69.95  |
| RX144C W/T . . . | factory wired / mounted . . .                         | 114.95 |
| RX220C . . .     | 210-240 MHz rcvr w/2 pole xtal<br>10.7 filter . . .   | 69.95  |
| RX432C Kit . . . | NEW — 432 MHz receiver . . .                          | 79.95  |
| RXFL . . . . .   | 70DB filter option for all RX-Recv<br>(w/exch.) . . . | 9.50   |
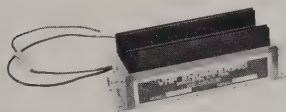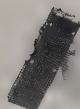
## HT144B Kit . . .


2 meter — 2w — 4 channel —  
hand held xcvr . . . . . 129.95



|                    |   |        |
|--------------------|---|--------|
| PA2501H Kit . . .  | similar to above — 25w . . . . .                                  | 59.95  |
| PA2501H W/T . . .  | factory wired . . . . .   | 74.95  |
| PA4010H Kit . . .  | 10w in — 40w out — relay<br>switching . . . . .                   | 59.95  |
| PA4010H W/T . . .  | factory wired . . . . .   | 74.95  |
| PA144/15 Kit . . . | similar to PA1501H less case,<br>connectors & switching . . . . . | 39.95  |
| PA144/25 Kit . . . | similar to above — 25w . . . . .                                  | 49.95  |
| PA220/15 Kit . . . | similar to PA144/15 for 220<br>MHz . . . . .                      | 39.95  |
| PA432/10 Kit . . . | NEW — similar to PA144/15 ex-<br>cept 10w and 432 MHz . . . . .   | 39.95  |
| PA140/10 . . . .   | NEW — 10w in — 140w out<br>2 meter amp — factory wired . . .      | 179.95 |
| PA140/30 . . . .   | NEW — 30w in — 140w out<br>2 meter amp — factory wired . . .      | 159.95 |

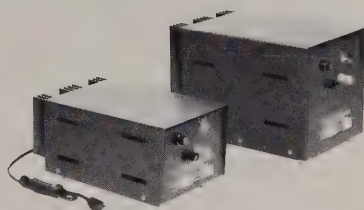

|                   |   |        |
|-------------------|---|--------|
| PS3 Kit . . . . . | power supply regulator card . . .                           | 8.95   |
| PS12C Kit . . . . | 12 amp — 12 volt regulated<br>power supply w/case . . . . . | 69.95  |
| PS12C W/T . . . . | factory wired . . . . .                                     | 85.95  |
| PS24C Kit . . . . | 24 amp — 12 volt regulated<br>power supply w/case . . . . . | 99.95  |
| PS24C W/T . . . . | factory wired . . . . .                                     | 114.95 |

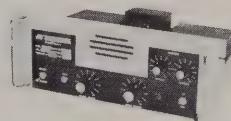

|                    |   |        |
|--------------------|---|--------|
| RPT144 Kit . . . . | 2 meter — 15w — complete . . .                                | 364.95 |
| RPT220 Kit . . . . | 220 MHz — 15w — complete . . .                                | 364.95 |
| RPT432 Kit . . . . | NEW — 10 watt — 432 MHz<br>repeater . . . . .                 | 399.95 |
| RPT144 . . . . .   | NEW — 15 watt 2 meter<br>repeater — factory wired . . . . .   | 595.95 |
| RPT220 . . . . .   | NEW — 15 watt — 220 MHz<br>repeater — factory wired . . . . . | 595.95 |
| RPT432 . . . . .   | NEW — 10 watt — 432 MHz<br>repeater — factory wired . . . . . | 649.95 |

## OTHER PRODUCTS BY VHF ENGINEERING

|                    |  |         |
|--------------------|--|---------|
| CD1 Kit . . . . .  | 10 channel receive xtal deck<br>w/diode switching . . . . .            | \$ 6.95 |
| CD2 Kit . . . . .  | 10 channel xmit deck w/switch<br>and trimmers . . . . .                | 14.95   |
| COR2 Kit . . . . . | complete COR with 3 second and<br>3 minute timers . . . . .            | 19.95   |
| CWID-1 Kit . . . . | NEW — code identifier — 160 bits,<br>field programmable diode matrix . | 39.95   |
| SC2 Kit . . . . .  | 10 channel auto-scan adapter<br>for RX . . . . .                       | 19.95   |
| Crystals . . . . . | we stock most repeater & simplex<br>pairs for 146.0-147.0 . . . . .    | 5.00    |
| *DPLX-144 . . . .  | 2 meter, 6 cavity, close spaced<br>duplexer — tuned to frequency . .   | 399.95  |
| *DPLX-220 . . . .  | 220 MHz, 6 cavity duplexer<br>tuned to frequency . . . . .             | 399.95  |

**SHIPPING INFORMATION:** All shipments are F.O.B. Binghamton, N.Y. 13902. Shipments will be made by the most convenient method. Please include sufficient funds to cover shipping and handling. Figure shipping charges on a minimum weight of 2 pounds per unit with the exception of the following: PS 12C — 13 lbs., PS 24C — 25 lbs., Repeaters — 25 lbs.

# Vhf engineering

320 Water St. • PO Box 1921-H • BINGHAMTON, NY 13902 • 607-723-9574

DIVISION OF BROWNIAN ELECTRONICS CORP.





# how to use milliammeters

A discussion of  
meter shunts  
and other techniques  
to adapt surplus  
panel meters to the  
operating requirements  
of your own circuits

Quite often neither your junkbox nor the local surplus outlet has the meter you need for some new piece of equipment. It is very easy to substitute low-range microammeters or milliammeters where higher range milliammeters are wanted, or voltmeters in some cases. Meters have a generally-unknown internal resistance and a shunt resistor will divide the total circuit current flow between the meter and the shunt according to Ohm's law.

Guy Black, W4PSJ, 12317 Hanger Road, Fairfax, Virginia 22030

It is not necessary to determine the meter resistance to apply this ancient trick, although that is not particularly difficult, and meter shunts can be satisfactorily made with readily-available materials. For example, on a recent rig I shunted a 60 mA meter to read 600 mA, a 200  $\mu$ A meter to read 20 mA and a 100  $\mu$ A meter to read 10 mA. The basic test setup for current-meter shunting is a variable current source and a calibrated meter, either a small battery, with a series variable resistor, or an adjustable current-limiting power supply such as the Heath HP-28 which can be set at the desired full-scale current.

For milliammeters, shunt resistances are often very small: a 10 mA meter, for example, is likely to have about 2.5 ohms internal resistance and a 200 mA meter, about half an ohm. In the resistance ranges desired, copper wire makes quite satisfactory shunts.

## meter shunt theory

For full-scale meter readings there will be an IR drop across the meter. If it is desired that the meter read full scale when the total circuit current is higher, the shunt must have whatever resistance

will pass all the additional current at the same IR drop. For example, a 10 mA meter with 2.5 ohms internal resistance will have an IR drop of  $(0.01 \times 2.5 = 0.025 \text{ volt})$ . If you wish the meter to read full scale when the circuit current is actually 100 mA, the shunt must pass 90 mA at 0.025 volt, which calls for a 0.278 ohm shunt  $(0.025V \div 0.09 \text{ mA} = 0.278 \text{ ohm})$ . A standard-value 0.27 ohm resistor will do the trick.

It is not difficult, however, to zero in on the right shunt value without knowing the internal resistance by taking a random length of small copper wire, placing it in series with the constant-current source, connecting the meter to one end and tapping it (with a needle-tipped probe) along the shunt wire until the meter reads full scale. Number-30 enamel wire, for example, has about 0.1 ohm per foot (3.28 ohm per meter) and the resistance and current-carrying capacity of other wire sizes appear in the ARRL Handbook. Thus, 2.8 feet (85.3cm) of number-30 wire wound in a small coil would make a suitable shunt for the previous example.

A lot of trial and error can be saved, however, by some simple calculations. Start by making a trial shunt, erring on the low resistance side if you have limited control over your constant-current source. Here is how it went shunting a 60 mA meter to 600 mA. With about 3 inches (76mm) of resistance wire, 60 mA in the circuit produced a meter reading of 15 mA, meaning that 45 mA was being passed by the shunt. As the IR drop across the meter and the parallel shunt is the same, two Ohm's law expressions can be stated in terms of three unknowns: the meter resistance,  $R_m$ , the test shunt resistance,  $R_s$ , and the common voltage across the meter and shunt,  $E$ ,

$$\begin{aligned} E &= 0.045 R_s \\ E &= 0.015 R_m \\ R_s &= 0.333 R_m \end{aligned}$$

When this meter is used in the 600 mA circuit the required current division between the meter and the shunt is 60 mA through the meter and 540 mA through the shunt. Using the same set of equations, the relationship of the meter resistance to the desired shunt resistance,  $R'_s$  is calculated as follows:

$$\begin{aligned} E &= 0.540 R'_s \\ E &= 0.060 R_m \\ R'_s &= 0.111 R_m \end{aligned}$$

Since the meter resistance,  $R_m$ , is an unchanging value, the *desired* shunt resistance,  $R'_s$ , compared to the *test* shunt resistance,  $R_s$ , is:

$$\frac{R'_s}{R_s} = \frac{0.111 R_m}{0.333 R_m} = 0.333$$

This is the same as saying that the wire in the desired shunt should be exactly one-third the length of the wire in the test shunt. The unknowns are still unknowns, but the desired result has been achieved.

When shunting sensitive milliammeters or microammeters, a low-range resistance decade is nearly essential because the resistance values are too high for lengths of copper wire. Alternatively, a small-value potentiometer can be used as a variable shunt, the value set for full-scale reading at the desired circuit current and then measured with an ohmmeter.

The approximate shunt values can be estimated by noting that 1 mA meters typically have about 30 ohms resistance; 500  $\mu A$  instruments, about 90 ohms; 100  $\mu A$ , 500 ohms; and 50  $\mu A$ , about 2500 ohms. (If a decade resistance box is used, be sure it has shorting contacts or the full circuit current will instantaneously go through the movement during switching!) With this technique, the actual value of the desired shunt is determined and it is possible to select series or parallel combinations of stan-

dard-value resistors that will closely approximate the desired shunt value.

Note that decade resistance boxes can be constructed with only four resistances by using the Mallory type 154L switch, which automatically arranges a 1-ohm, two 2-ohm and a 5-ohm resistor so as to provide the entire decade range. In the one-tenth to one ohm range switch contact resistance is not likely to be serious. Such a decade will be very convenient if you plan to design shunts for very many meters.

There is less chance of blowing out meters accidentally in test set-ups if you wire the shunt in series with the current source and tap the meter around the shunt, rather than the other way round.

You will probably find that resistance wire is a bit hard to come by, and generally bare wire intended for heating elements is all that can be found. Standard Scientific Supply\* carries Chrome-A resistance wire (80 percent nickel and 20 percent chromium) which has the best temperature/resistance relationship. Its resistance characteristics are listed in table 1.

### critical damping resistance

If a meter is heavily shunted, the movement will be severely damped by self-induced current, and this may be undesirable in applications such as measuring the plate current of a linear, or VU instruments. The amount of damping can be reduced by putting a small resistor in series with the movement and shunting the combination of that resistor with the movement

An interesting experiment with a sensitive high-quality meter is to vary the shunt resistor with a potentiometer and observe how the needle oscillates before finally coming to rest. The largest resistance for which the needle approaches the final setting without overswing is

called the critical damping condition. With more resistance there will be a slight overswing, and with less resistance the final setting will be approached more slowly.

In amateur applications there is no particular need to achieve critical damp-

table 1. Resistance characteristics of Chrome-A nickel-chromium resistance wire.

| B&S<br>gauge | diameter         | resistance<br>per foot<br>(ohms) | resistance<br>per meter<br>(ohms) |
|--------------|------------------|----------------------------------|-----------------------------------|
| 18           | 0.0400" (1.02mm) | 0.406                            | 1.332                             |
| 20           | 0.0320" (0.81mm) | 0.635                            | 2.083                             |
| 22           | 0.0253" (0.64mm) | 1.017                            | 3.337                             |
| 24           | 0.0201" (0.51mm) | 1.610                            | 5.282                             |
| 26           | 0.0159" (0.40mm) | 2.570                            | 8.432                             |
| 28           | 0.0126" (0.32mm) | 4.100                            | 13.451                            |
| 30           | 0.0100" (0.25mm) | 6.500                            | 21.325                            |

ing, but it can easily be approximated by making the series combination of the shunt and resistance in series with the coil equal to the critical damping resistance.

### meter multipliers

Voltmeters can also be multiplied using additional series resistors, and low-current milliammeters or microammeters can be easily converted to voltmeter use. In this use, it is well to operate far below the wattage rating of the shunts because the temperature coefficient of standard carbon resistors is not the best. In addition, the maximum voltage across any one resistor should be kept below about 400 volts.

One of the best uses for shunts is for multi-circuit metering of equipment where different current or voltage ranges are desired for each circuit. In such configurations it is very useful to mount the shunts on the switch — generally a non-shorting type. You must watch the voltages on the various circuits, and on the meter as well. Current production panel meters from Weston and other firms built to government

\*Standard Scientific Supply Corp., 808 Broadway, New York, New York 10003.




specifications are tested at 3000 volts (actually 2600 volts rms) between the movement and the case, but very old meters with metal zero-adjust screws should be used in high-voltage circuits only with great caution.

If a multiplier resistor is used to expand the range of a voltmeter which is switched off the multiplier, leaving the multiplier resistor floating, it will assume the full voltage potential which may be more than the switch insulation can stand. A better approach is to run the multiplier to ground, taking the voltage off a tap on the multiplier resistor. With this arrangement, the voltage across the switch contacts will be far less.

## ayrton shunt

You can easily convert a sensitive meter into a multirange milliammeter with a few standard-value resistances and a switch using the configuration known as the Ayrton shunt shown in **fig. 1**. The values given will yield full-scale readings of 10, 100 and 1000 milliamperes within a few percent from a 1 mA meter with 50 ohms internal resistance. If your meter has less internal resistance, add enough resistance in series to bring it up to that value. A

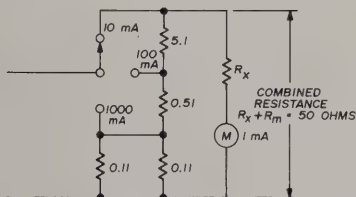


**fig. 1.** Using the simple Ayrton shunt circuit shown here, a 1 mA meter with 50 ohms resistance can be used to measure 10, 100, and 1000 mA.

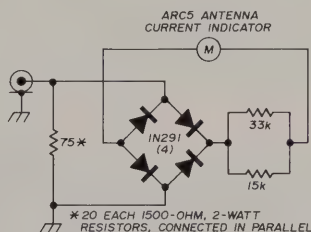rough way to measure internal meter resistance is to adjust a constant-current source through a resistor to bring the meter to full scale, and then add enough resistance in parallel to bring the meter

to half scale. The *added* resistance then equals the meter resistance.

Meters are sometimes found with non-linear movements, and they can be particularly useful in some applications (and of course internal resistance cannot be found in the manner just described).



| CALIBRATION |        |
|-------------|--------|
| SCALE       | POWER  |
| 1           | 40 mW  |
| 2           | 150 mW |
| 3           | 330 mW |
| 4           | 610 mW |
| 5           | 1.65 W |
| 6           | 2.70 W |
| 7           | 5.00 W |
| 8           | 8.60 W |
| 9           | 16.9 W |
| 10          | ≈ 45W  |

**fig. 2.** This wide range rf wattmeter uses surplus non-linear "antenna current indicator" meter used in Command Set transmitters.

Many amateurs have such meters in their junkboxes which were salvaged from war surplus Command Sets, a 2½-inch (64mm) meter with a zero-to-ten indication labelled, "antenna current indicator." Half-scale of this meter is about 5 milliamperes, but it is very sensitive at the low range and very insensitive at the high range. Built into the rf wattmeter shown in **fig. 2**, a scale reading of 1 corresponds to 40 milliwatts on my instrument, 5 corresponds to 1.6 watts, and 9 corresponds to 17 watts. This wattmeter is for 75-ohm systems but a similar arrangement could be built for 50 ohms (I often use 75-ohm coax, as low-loss 75-ohm CATV cable is often available on the surplus market).

If you cannot find a non-linear meter you can achieve the same result by shunting any meter with diodes and add-

ing enough series resistance to the movement to bring the combined IR drop to about the contact potential of the diode. Table 2 gives the full-scale IR drop of a common (and typical) series of panel micro/milliammeters. Since silicon diodes start to conduct at about 0.6 volt, nonlinearity is achieved by adding enough series resistance to the movement at  $R_V$  in fig. 3 so that the combined IR drop is in this general range.

If too large a resistance is added the meter will not reach full scale; if just enough resistance is added so that full scale can be achieved the reading will be very nonlinear, and by adding less the linearity is improved. In fact, merely adding a protective diode alone will produce some degree of non-linearity, although it is not likely to be noticeable except in microammeters.

Parenthetically, meters are protected only up to the point where the shunting diode blows out, and with high-current

curves of current versus needle deflection can be obtained by various combinations of zeners and shunt diodes. All of these effects, of course, ruin the original scale calibration.

Zener diodes in series with milliammeters result in expanded-range volt-

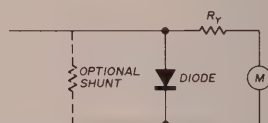


fig. 3. Simple circuit for non-linearizing meter movements uses semiconductor diode (see text).

table 2. Internal resistance of Simpson type 1212C panel milliammeters (typical of quality panel instruments).

| full-scale reading | internal resistance (ohms) | full-scale IR drop (volts) |
|--------------------|----------------------------|----------------------------|
| 50 $\mu$ A         | 5000                       | 0.250                      |
| 100 $\mu$ A        | 2000                       | 0.200                      |
| 200 $\mu$ A        | 1000                       | 0.200                      |
| 500 $\mu$ A        | 200                        | 0.100                      |
| 1 mA               | 46                         | 0.046                      |
| 5 mA               | 23                         | 0.115                      |
| 25 mA              | 3                          | 0.075                      |
| 50 mA              | 1.5                        | 0.075                      |
| 100 mA             | 0.75                       | 0.075                      |
| 200 mA             | 0.6                        | 0.120                      |
| 1 amp              | 0.05                       | 0.050                      |

diodes available so inexpensively on the surplus markets, it makes sense to use a 10-ampere diode in any setup (such as an experimental bench supply) where short circuits are occasionally possible. These diodes need not be heatsinked.

Nonlinearity of the opposite sort can be achieved by putting zener diodes in series with meters, and some very odd

meters. For example, a 150 volt, 10 watt zener such as the 1N3011, in series with a 1N4007 and 100-ohm resistor, spreads out 100 to 130 volts over the entire scale of a 50 mA meter. The amount of resistance determines the amount of compression. Lower voltage zeners — typically just above the target voltage — are very useful for expanded scale monitors of battery packs and transmitter filament voltages. The additional series diode is only necessary when monitoring ac.

## summary

Liberal use of meters can be one of the design features where the home builder can outshine the commercial source. Good quality panel meters are still in abundant supply in surplus and at flea markets, often at very low prices. Changing scales and ranges is not very difficult for many types, though it is not possible to open up the newer hermetically sealed-instruments. The more odd-ball the scale, of course, the lower the selling price.

## bibliography


1. Ernest Frank, *Electrical Measurement Analysis*, McGraw-Hill, New York, 1959.

ham radio

Our new priority crystal processing, using a mark sensing order system, is designed to expedite orders for International Crystals and EX Kits. It's another effort to improve our order processing and make a proven reliable system even better. Your order in the future will be processed by using mark sensing order cards and prepunched name and address cards. Complete and return the coupon and we will mail you a special kit containing instructions, order cards and a prepunched name and address card. This is the first step in our new "no delay" order processing.

For International Crystals, EX Oscillators and Amplifiers

SPEEDS AND SIMPLIFIES ORDERS...

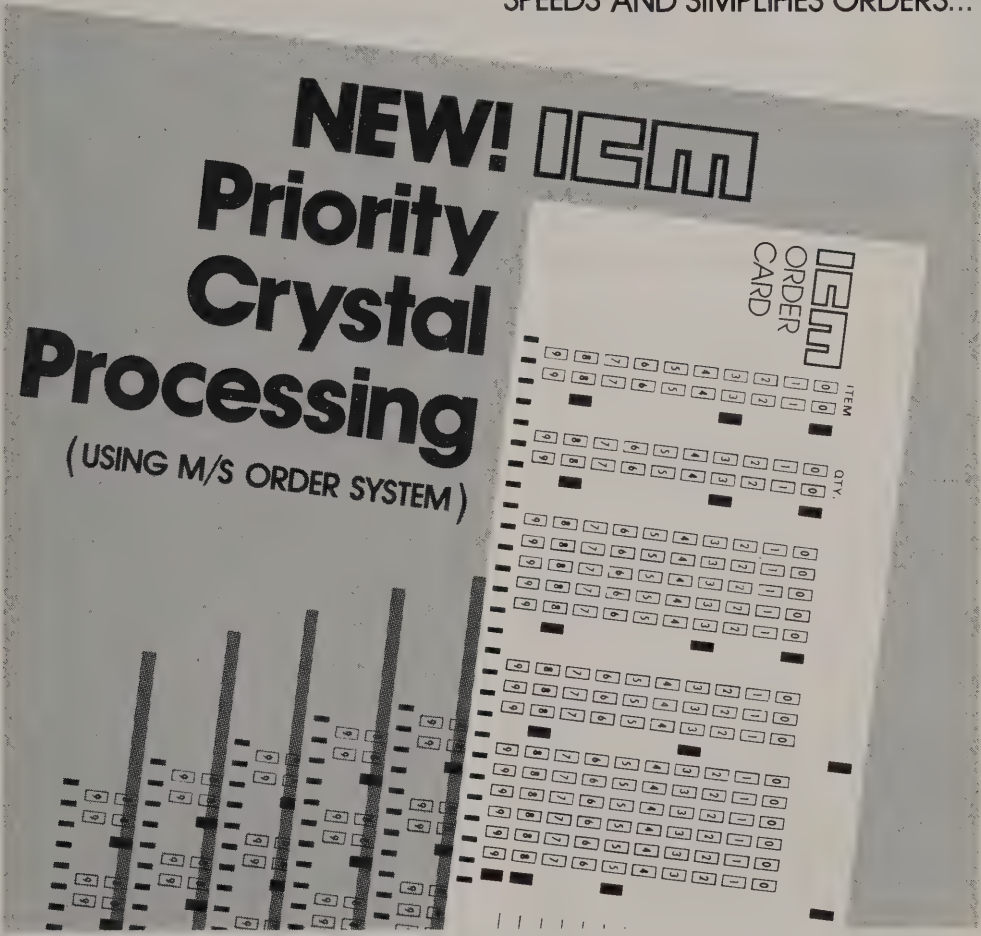

INTERNATIONAL CRYSTAL MFG. CO., INC.  
EX Dept, P.O. Box 32497, Oklahoma City, Ok. 73132

Send Special Kit to . . .

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_



# magnet-mount mobile antenna

This simple,  
magnet-mount  
vhf antenna is useful  
for temporary  
mobile operation  
where a permanently  
mounted antenna  
is not available

A magnet-mount antenna is an indispensable item for anyone currently working vhf fm on 144, 220, or 450 MHz. When used in conjunction with a cigarette lighter adapter to provide 12 Vdc for the fm rig, it permits mobile operation from almost any vehicle at a moment's notice. Thus, from an emergency standpoint, you are not restricted to a vehicle already equipped with a vhf antenna. In addition, the magnet mount is useful for those who do not wish to cut a hole in their car to operate mobile.

Unfortunately, commercially available magnet-mount antennas are expen-

sive, and up to now it has been difficult to obtain magnets with the right surface area, the right holding power, and the right price. This article describes a very simple quarter-wave magnet-mount antenna which can be built in about a half hour for any of the three vhf bands mentioned. The total cost of the antenna, not including coaxial cable, is less than \$6.00. All parts are readily available, and the magnets can be obtained locally.\*

The magnet-mount antenna is really too simple for words; **fig. 1** shows a drawing of the antenna. It simply consists of a good quality magnet, a 1½-inch (38mm) long 6-32 or 8-32 (M3.5 or M4) flat-head screw, three nuts, a lock washer, coax connectors, and a cable clamp.

## construction

To build the antenna, connect a female uhf chassis connector to the magnet as shown in **fig. 1**. Run the coax under the cable clamp (or tape the coax to the screw if you don't have the clamp), and connect the inner conductor to the center of the coax connector and the shield to the flange. Take a piece of brazing rod of the proper length (see **fig. 1**), and solder it to the male uhf connector. Use some silicone

\*If you can't find a local source, the 1½ inch diameter magnets are available for \$3.95 plus postage from George Allen Engineering, 80 Farmstead Lane, Windsor, Connecticut 06095. Connecticut residents add 6% sales tax.

George Allen, W1HCL, 80 Farmstead Lane, Windsor, Connecticut 06095

bathtub caulking such as that made by GE to fill up the male connector to provide a good seal. The brazing rod can be obtained from any welding supply house.

In regard to the magnet, use round button or shallow pot Alnico magnets or equivalent of 1¼ or 1½ inches (32 to 48mm) diameter. Magnets of this size provide enough holding power, while smaller magnets won't hold well and will blow off your car at high speeds. Note that when your antenna is not being used, make sure that the "keeper," the small metal piece provided with the magnet, is placed across the poles of the magnet. The use of the keeper prevents loss of magnet power.

## tuning

Although this simple magnet-mount antenna will give you good results, it is not quite as efficient as a quarter-wave antenna permanently mounted on your car. In most cases, however, you probably couldn't see the difference between the magnet-mount antenna and one that is permanently mounted. In regard to feedline matching, it is difficult with

this type of antenna to get the swr down to 1:1. However, this really doesn't matter since your feedline is very short and the overall losses will be small.

To tune the antenna, place the antenna on the center of the car roof or trunk and connect an swr bridge in the line between the transmitter and the antenna. Start snipping off pieces of brazing rod by 1/8 inch (3mm) at a time until the swr falls between 1.5:1 and 2:1. At this point the antenna is tuned, and the only remaining thing to do is to put some silicone seal or tape on the end of the antenna to protect against injury. Note that the swr may vary when the antenna is used with different cars.

## performance

I have been doing quite a bit of traveling in the last six months and have been taking this antenna with me. It is convenient to use, works well, and has yet to come off a car roof at speeds up to 80 mph. I have been using the antenna on all sorts of rental cars and have had no problems except where the car has a vinyl roof. In those cases I place the antenna on the trunk. The magnet won't hold well through the thickness of the vinyl.

In practice, I place the antenna on the center of the roof or trunk and run the coax through a window, leaving the window slightly open so as not to damage the cable. I connect the coax to my rig and I'm on the air! It does not appear to be necessary to protect the car paint from the magnet. I have been using these mounts for four years and have yet to scratch the paint with a bare magnet.

I hope that this short article gives you the incentive to build this simple antenna; it's handy either for daily use or to keep in the closet for use in that emergency when you can't use your own car.

ham radio


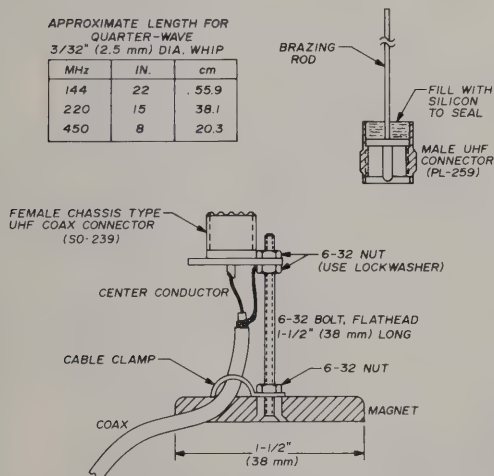


fig. 1. Construction details of the simple magnet-mount mobile antenna. Dimensions are given for quarter-wave operation on 144, 220 and 450 MHz.


# DENTRON — for QUALITY

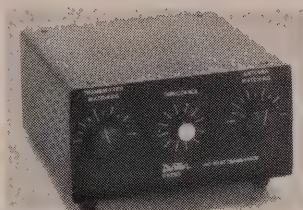

## 160-10AT SUPERTUNER™

Want an antenna tuner to match everything between 160 and 10 through balanced line, coax line and random line, pump out the full legal limit and look and sound good doing it? Supertuner™ is the one for you at just


**\$119.50**

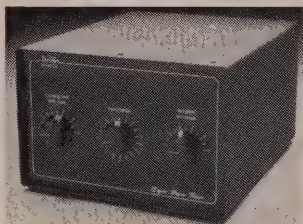

## 160-10AT-3K SUPER SUPERTUNER™

Designed and engineered to be compatible with the full-power highly efficient modern amplifiers now available to the amateur. In our opinion the finest tuner on the market today.

**\$229.50**

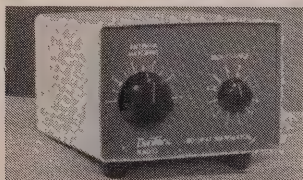

## 80-10AT SKYMATCHER™

Here's an antenna tuner for 80 through 10 meters, handles full legal power and matches your 52 ohm transceiver to a random wire antenna. 80-10AT is yours for only

**\$59.50**



## 160AT SKYMATCHER™

160 meters is a blast! This antenna tuner brings the fun of 160 to you while handling full legal power. Matches your 52 ohm transceiver to your present antenna or any random length antenna ranging from a short whip to an extra long wire. Only

**\$59.50**



## 160XV TOP BANDER™

160 meters is only a step away from 80 with this remarkable Dentron 160 meter transverter. Specifically designed to bring simple low cost 160 meter capability to any amateur station currently equipped for 80 meter CW, SSB, or AM operation. No modification of your existing equipment is required. Just "plug in and play" and you're on 160 meters with 100 watts transmit power and a super sensitive receiver. Just

**\$199.50**

2 MHz MARS Unit

**\$229.50**

## COMING ATTRACTIONS FROM DENTRON

- 160 meter solid state receiving converter
- "Dual-meter" in line wattmeter
- Audio Rectification Filters for RFI problems in HiFi, tape recorders, organs, intercoms, etc.

Write for full details



# TY and PERFORMANCE

## SKYMASTER™

A fully developed and tested 27 foot vertical antenna covers entire 10, 15, 20, and 40 meter bands using only one cleverly applied wave trap. A full  $\frac{1}{4}$  wave antenna on 20 meters. Constructed of heavy seamless aluminum with a factory tuned and sealed HQ Trap, SKYMASTER™ is weatherproof and withstands winds up to 80 mph. Handles 2 KW power level and is for ground, roof or tower mounting. Radials included in our low price of **\$84.50**

## SKYCLAW™

A tunable monoband high performance vertical antenna, designed for 40, 80, 160 meter operation. SKYCLAW™ gives you the following spectrum coverage:

| BAND<br>(Meters) | BANDWIDTH<br>(kHz) |
|------------------|--------------------|
| 160              | 50                 |
| 80               | 200                |
| 40               | entire band        |

Tuning is easy and reliable. Rugged construction assures that this self-supporting unit is weatherproof and survives nicely in 100 mph winds. Handles full legal power limit. All this coverage for **\$79.50**

## 160 METER MOBILE TOP BANDER™

Now you can operate on 160 meters in your car, boat, plane or RV. Covers 10 kHz bandwidth without adjustment and entire 160 meter band with adjustment. It's streamlined 10½ ft. length includes a slim lightweight, factory sealed loading coil. Handles 500 watts. Standard  $\frac{3}{8}$ "-24 ball mount thread. Now **\$59.50**

## ALL BAND DOUBLET

This All Band Doublet or Inverted Type Antenna covers 160 through 10 meters. Has total length of 130 feet (14 ga. stranded copper) although it may be made shorter if necessary. This tuned Doublet is center fed through 100 feet of 450 ohm open balanced transmission line. The assembly is complete. Add rope to the ends and pull up into position. Tune with the Dentron Super Tuner and you're on 10 through 160 meters with one antenna! Now just **\$24.50** for the Dentron All Band Doublet.

NOTE: All prices are postpaid in U.S.A.


Phone: 216-425-8073



"MAKING AMATEUR RADIO MORE FUN!"
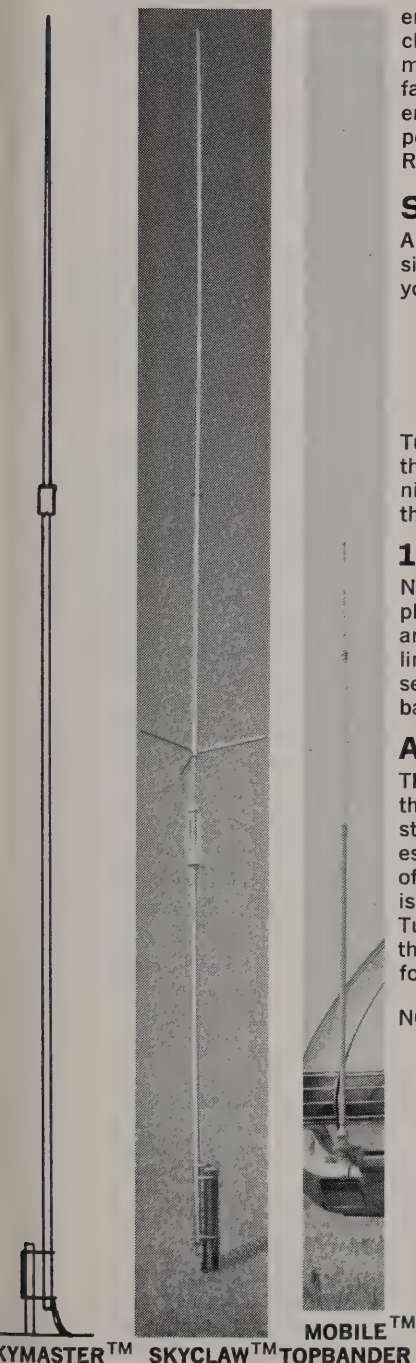
# Dentron

RADIO CO., INC.  
2100 Enterprise Avenue  
Twinsburg, Ohio 44087



SKYMASTER™ SKYCLAW™ MOBILE™ TOP BANDER™

# 300-Hz crystal filter for Collins receivers

Recently a number of 455-kHz Collins crystal filters with a 6-dB bandwidth of 300 Hz have become available on the surplus market.\* These filters, which were built to military specifications, have a 60-dB bandwidth of 1200 Hz and maximum insertion loss of 5 dB, are designed for a source and load impedance of 2000 ohms, and do not require any resonating capacitors† (mechanical filters for Collins receivers are designed for terminations of 50 kilohms or greater and require external capacitance to resonate the transducer coils). If the crystal filter is not terminated with 2000 ohms, passband ripple will be on the order of 6 dB or more and spurious response will seriously degrade skirt selectivity.

Since the filters in Collins receivers are isolated by dc blocking capacitors, the required terminations for the crystal filter are most easily provided by simply connecting 2200-ohm resistors across the input and output terminals. Be sure to remove the 100 pF resonating capacitors from the circuit, however, as they will cause excessive passband ripple and unwanted spurious response. When terminated with 2200-ohm resistors passband ripple is nil and the skirts roll off smoothly to 80 dB or more.

Unfortunately, however, this simple resistive loading results in a serious impedance mismatch which manifests itself as 10 to 12 dB of additional circuit loss. Increasing the terminating resistors to 3900 ohms will reduce the loss about 3 dB, but passband ripple starts to suffer. A better solution is to drive the

crystal filter with the simple emitter follower circuit shown in fig. 1. This circuit, which requires only 10 mA of current, reduces circuit loss to 3 dB or less and provides the filter with the required source impedance.

The emitter follower can be built on a small section of perforated circuit board which is supported by the input and output wiring. Power is derived from the screen circuit of the mixer tube. Make sure that the emitter follower is properly isolated with dc blocking capacitors as any dc voltage on the filter transducers will damage them (the filter switch has shorting contacts, so any voltage on the switch may damage adjacent filters as well). However, if you follow the circuit shown in fig. 1, which is completely isolated, you will have no difficulties.

Installation of the filter in 75S3B and later model S-line receivers requires only a length of number-20 (0.8mm) tinned bus wire, a lockwasher, and a 4-40 nut. The filter is installed below the chassis, on one side of the filter shield compartment, as shown in fig. 2

\*The Collins 300-Hz crystal filters, X455KF300, with data sheets, are available from Gary Fertik, W1EBC, 40 Pilgrim Trail, Woodbury, Connecticut 06798. Price is \$49.95, postpaid.

†XF455KF300 filters, Collins part number 526-7073-010. Other Collins crystal filters with the same generic nomenclature but with different part numbers are designed for 20k terminations; some require external capacitors. Although the filter described here is the most common, check the data sheet which comes with your filter.

Jim Fisk, W1DTY, Ham Radio Magazine, Greenville, New Hampshire 03048


(installation suggested by WA8OBG). Three holes are required: two for the electrical terminals and one for the mounting screw. Since these holes are below the chassis the filter installation does not deface the receiver.\* The filter is symmetrical so either end may be used for the input or output.

## Collins 75A4

Owners of Collins 75A4 receivers should be particularly interested in the 300-Hz crystal filter as the narrowest bandwidth filter designed specifically for this receiver has a 3-dB bandwidth of 500 Hz, and these filters are very difficult to find on the open market. Although there are two methods of installing the 300-Hz crystal filter in the 75A4, the installation shown in the photograph is recommended because it provides maximum isolation between the input and output (this same method is also recommended for Collins type-FA mechanical filters).

Turn the 75A4 upside down on your bench (front panel forward) and remove the bottom cover. The three filter sockets are in the front right-hand corner next to the selectivity switch. The crystal filter is installed in the shield which crosses the three filter sockets. Two 1-inch (25mm) deep slots must be cut in the shield as shown in **fig. 3**. Use *sharp* tin snips and place rags underneath the work area on both sides

of the shield to catch any debris. After cutting the slots, bend the tab toward the rear of the receiver so it forms a 90-degree angle with the shield. A hole for the filter mounting screw is drilled in the center of the tab, 1/4 inch (6mm)

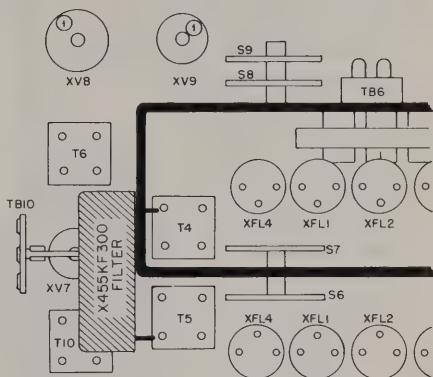


**fig. 2.** Installation of the Collins X455KF300 crystal filter in S-line receivers.

from the end (the threaded stud on the other end of the filter is not used).

After the tab is finished, temporarily set the filter in place to check for clearance between the top of the filter and the bottom cover of the receiver (if you follow the dimensions shown in **fig. 3**, the top of the filter should be approximately flush with the top of the shield).

Locate the input and output wires to filter socket A (underneath switch S2) and their respective connection points on the switch wafers (note that one of the wires is grounded). Remove the two 100-pF resonating capacitors. Install the emitter follower circuit shown in **fig. 1** between switch S2 and the crystal filter. The emitter follower common is con-

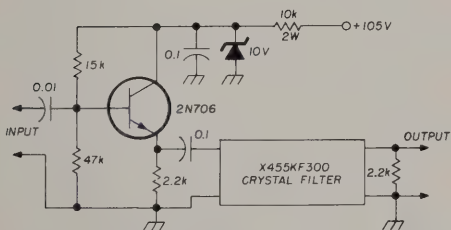

**fig. 1.** Emitter-follower circuit which provides correct source impedance for the crystal filter and minimizes circuit loss. Most general-purpose npn transistors may be substituted in the circuit.

\*In some Collins 75S3B receivers there is sufficient clearance under the filter shield on the top of the chassis that the crystal filter can be installed in the existing crystal-filter sockets. Although the terminals of the X455KF300 will not fit the sockets, short lengths of no. 20 (0.8mm) wire can be soldered to the filter terminals and plugged into the sockets.



nected to the grounded terminal on the rear wafer of S2; the input coupling capacitor, C1, is connected to the other switch terminal which goes to filter socket A. Install two short lengths of number 20 (0.8mm) bus wire to each of the connection points on the front wafer of switch S2. (If you don't want to include the emitter follower, connect bus wires to the rear wafer as well.)

Connect a 2200-ohm resistor across the output terminals of the crystal filter and install the filter on the mounting tab using a lockwasher and 4-40 nut. Wire in the emitter follower and solder the two bus wires to the output terminals. Total installation time should be two hours or less.

Since you have the bottom of the receiver open, this is a good time to apply some contact cleaner (such as GC Electronics *Tunerlube*) to each of the switch contacts. It's also a good idea to dab some silicone grease on the switch detent mechanisms. If your 75A4 is like most, the only lubrication the receiver has ever seen was applied at the factory, and that's pretty well dried up. A little switch care now may save an expensive replacement problem later.

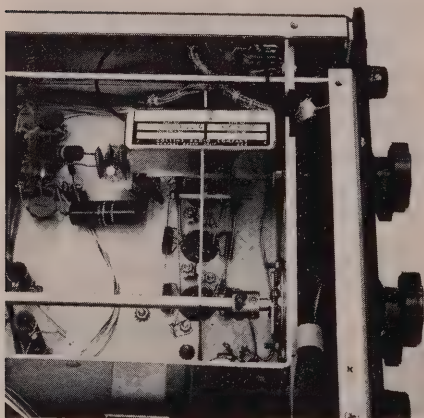


fig. 4. Crystal filter installation in the Collins 75A4 receiver. The emitter follower is on the small circuit board to the left.

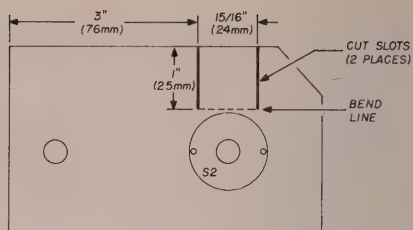


fig. 3. Collins 75A4 filter shield, showing modifications required for installing the crystal filter. Completed installation is shown in the photograph.

An alternative method is to mount the crystal filter on a small L-shaped bracket which is attached to the chassis with the screw which holds the left-hand end of the filter shield (next to the i-f gain control). In this case the filter connections are made to filter socket C. However, this method is not recommended because the connecting wires are quite long and lowered input-output isolation degrades the high skirt selectivity of which the filter is capable.

## operation

If another mechanical filter is installed in filter socket A, it must be moved to socket B or C. Operation of the 75A4 with the sharp 300-Hz filter requires some practice to gain full advantage of its high skirt selectivity. The setting of the *passband tuning* control is quite critical and for best results should be set so that CW signals peak at a pitch of about 700 Hz. When you tune in a signal with a broader filter, set the main tuning for a 700-Hz note before switching the sharper 300-Hz filter into operation. If the signal is tuned for a higher or lower note (assuming the passband tuner is set for 700 Hz), the receiver must be retuned slightly to find the signal. With a little practice, you'll find that the narrow bandwidth and high skirt selectivity of this filter do an excellent job of cutting interference or digging into the noise for weak signals.

ham radio

# Wilson Electronics Corp.

FACTORY DIRECT

**SPECIAL SEPTEMBER SALE**

## 1402 SM - 2.5 Watt Hand Held FM Transceiver

### SPECIAL INCLUDES:

- Rubber Flex Antenna
- Complete Set Nicad Batteries
- Leather Case
- 52-52 Crystal
- Your Choice of 2 Pair of Common Frequencies Only

Extra Xtals, \$4.50 ea.

**\$320 VALUE**  
**\$199.95**

### FEATURES

- 6 Channel Operation.
- Individual Trimmers on all TX and RX Xtals.
- All Xtals plug in.
- S Meter/Battery Indicator.
- 10.7 IF and 455 KC IF.
- 12 KHz Ceramic Filter.
- .3 Microvolt Sensitivity for 20 db Quieting.
- Microswitch Mike Button.
- Size 8 7/8 x 1 7/8 x 2 7/8 in.
- Weight 1 lb. 4 oz., Less Battery.
- Current Drain RX 14 MA TX 450 MA.
- 2.5 Watts Minimum Output - 12 VDC.

### ACCESSORIES

|       |   |          |
|-------|---|----------|
| SM1   | Speaker Mike                                    | \$ 29.95 |
| BC1   | Battery Charger                                 | \$ 36.95 |
| XF-1  | 10.7 Monolithic IF Xtal Filter (Installed)      | \$ 10.00 |
| TE-1  | Continuous Sub-Audible Tone Encoder (Installed) | \$ 39.95 |
| 1410A | 12 Watt Amplifier (Mobile)                      | \$109.00 |

## 1405 SM - 5 Watt Hand Held FM Transceiver

### SPECIAL INCLUDES:

- Rubber Flex Antenna
- Complete Set Nicad Batteries
- Leather Case
- 52-52 Crystal
- Your Choice of 2 Pair of Common Frequencies Only

Extra Xtals, \$4.50 ea.

**\$400 VALUE**  
**\$279.95**

### FEATURES

- 6 Channel Operation.
- Individual Trimmers on all TX and RX Xtals.
- All Xtals plug in.
- S Meter/Battery Indicator.
- 10.7 IF and 455 KC IF.
- 12 KHz Ceramic Filter.
- .3 Microvolt Sensitivity for 20 db Quieting.
- Microswitch Mike Button.
- Size 8 7/8 x 1 3/4 x 2 7/8 in.
- Weight 1 lb. 4 oz., Less Battery.
- Current Drain RX 14 MA TX 800 MA.
- Switchable 1 & 5 Watts Minimum Output - 12 VDC.
- High Impact Lexan® Case.

### ACCESSORIES

|      |   |          |
|------|---|----------|
| SM2  | Speaker Mike                                    | \$ 29.95 |
| BC2  | Battery Charger                                 | \$ 36.95 |
| XF-1 | 10.7 Monolithic IF Xtal Filter (Installed)      | \$ 10.00 |
| TE-1 | Continuous Sub-Audible Tone Encoder (Installed) | \$ 39.95 |

TO: WILSON ELECTRONICS CORP., 4288 S. POLARIS AVE., LAS VEGAS, NEVADA 89103  
(702) 739-1931

SHIP ME \_\_\_\_\_ 1402 SM \_\_\_\_\_ 1405 SM \_\_\_\_\_ SEPTEMBER SPECIALS

PLUS ☐ SM1 ☐ BC1 ☐ SM2 ☐ BC2 ☐ XF-1 ☐ TE1 ☐ 1410A

ENCLOSED IS \_\_\_\_\_ ☐ CHECK ☐ MONEY ORDER ☐ MC ☐ BAC

CARD # \_\_\_\_\_ EXPIRATION DATE \_\_\_\_\_


XTALS \_\_\_\_\_

NAME \_\_\_\_\_ ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

SIGNATURE \_\_\_\_\_

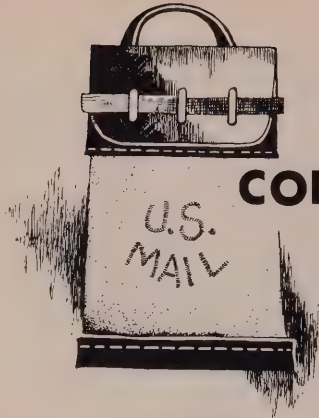Enclose additional \$4.50 for prepaid shipping & handling. Nevada residents add sales tax.  
Sale ends September 30, 1975.



## comments

### touch-tone decoder circuit boards

Dear HR:

Due to the rather large response to my article on Touch-Tone decoders which appeared in the December, 1974, issue of *ham radio*, I have decided to offer printed-circuit boards for sale to those individuals who might want them. I am also putting together some kits for those builders who have a hard time finding all the necessary components. All the parts and materials are top quality, commercial grade and ICs will be pre-tested to ensure performance. A set of boards is \$12.95, and a kit, including boards and toroids, is \$37.50.

John F. Connors, W6AYZ

Electromedics

3295 Brookdale Drive

Santa Clara, California 95051

### ssb transceiver

Dear HR:

A small number of the transceivers built from the ssb transceiver article in the August, 1974, issue of *ham radio* suffer from apparent agc instability. The symptoms are generally motor-boating at certain signal levels.

The problem is not, in fact, due to the agc but to instability caused by i-f feedback through the unused transmitter section of the circuit. It may easily be cured by connecting a single 0.1- $\mu$ F capacitor with low rf resistance between the transmitter section power

supply line and ground (as near as possible to the SL610C amplifier). Installing this capacitor does not remove the necessity of grounding the transmitter power line during reception and vice versa.

I apologize to anyone who has been inconvenienced by this fault, but the majority of these transceivers are not affected and the problem has only recently been brought to my attention.

Brian D. Comer, G3ZVC  
Plessey Semiconductors

### quadrature-phased local oscillator

Dear HR:

I have been following the articles concerning direct-conversion receivers and find the communication between Madey and Shubert regarding the Phase II receiver in the June, 1974 *comments*

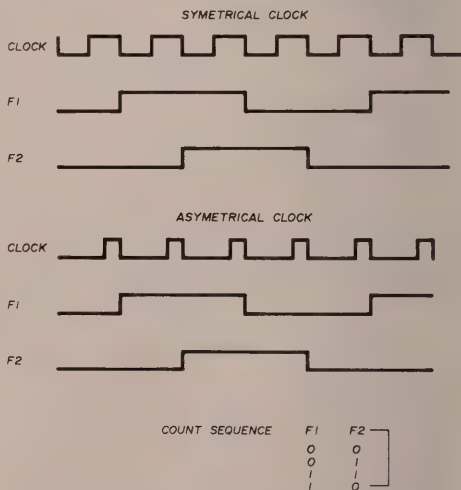


fig. 1. Waveform of the quadrature-phased local oscillator, showing independence of local-oscillator quadrature on clock-period asymmetry. Asymmetry of negative-going transitions would imply gross frequency instability.



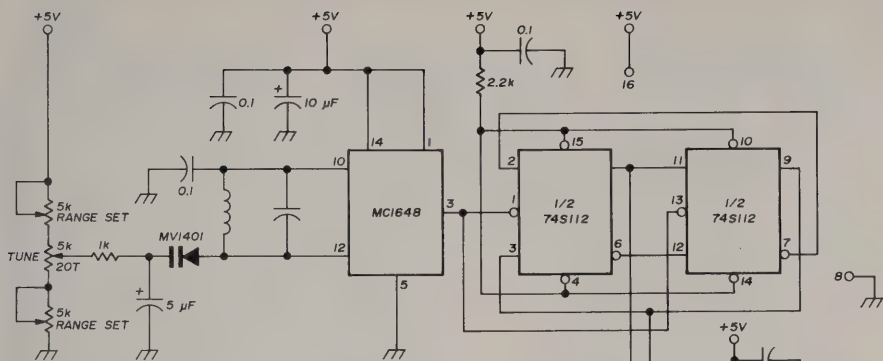


fig. 2. Schematic of a direct-phasing quadrature local oscillator designed for a direct-conversion 80-meter receiver. Timing sequence is shown in fig. 2.

section most interesting. The diagram of a quadrature-phased local oscillator I have been working on for use in a 3.5- to 4-MHz receiver is shown in fig. 2. As the timing diagram (fig. 1) demonstrates, the design is free of asymmetry errors since it is responsive to the negative-going transition of the clock waveform, and the clock may exhibit any periodicity it wishes, within device limitations. The circuit was intended for use with MC1496-type product detectors and has provision for switching the phase of the local oscillator to effect sideband reversal rather than performing the task at audio and having to accept a compromise in unwanted sideband rejection.

Douglas K. Beck, K6ZX  
Sunnyvale, California 94086

## Collins 75A4 mods

Dear HR:

Recently, when the avc failed in my Collins 75A4, the usual changing of tubes had no effect. Actually, a small amount of avc action remained — the S-meter needle rose slightly off zero with very strong signals. The trouble proved to be R86, a 39k resistor. Both R86 and R87 had suffered severe overheating — R86 had changed in value

from 39k to approximately 3k, causing overheating of R87 and eventual failure of the avc.

My 75A4 manual lists R86 as a half-watt resistor. However, a friend has a later 75A4 manual, and it shows a rating of one watt (the serial number of my receiver is in the 2500 series). If you experience avc failure in your 75A4, first check R86 and, if you're working on the receiver anyway, make sure that R86 is a one-watt resistor.

Incidentally, I cannot recommend too highly the 75A4 mixer mods described by W6ZO in *ham notebook*. I installed them over a year ago and have been extremely pleased with the results. I also changed the first rf amplifier from a 6DC6 to a 6GM6 as recommended by W2VCZ, and recommend that, too, as it increases gain and sensitivity. However, I would not plug in the 6GM6 without first installing the W6ZO mixer modifications.

Bob Locher, W9KNI  
Deerfield, Illinois 60015

## Heath HM-2102 wattmeter mods

Dear HR:

With reference to the item on the Heath HM-2102 wattmeter by VE6RF,\* the following additional information might also be of some interest. It was interesting to read how one amateur solved the problem of calibrating his Heath HM-2102 below an swr of 1.5:1. In my case the problem was solved in a slightly different manner.

In my initial calibration, using a Bird Termaline wattmeter, the minimum swr null was about 1.3:1. This was within the specified limits called for in the Heath instruction manual and, for all practical purposes, should have sufficed. However, in actual tests erroneous readings were obtained, often below the 1.3:1 reference level. An inspection of the schematic shows that C3 in series with C4 (the trimmer) will produce a capacitance of 1.99 to 5.56 pF. The total capacitance would then have to be changed to either a value lower than 1.99 pF, or higher than 5.56 pF. A 2 pF capacitor placed across C3 showed that the null could not be brought down to less than 2:1. Obviously the total capacitance of C3 and C4 had to be decreased instead of increased.

Cutting the long lead from C3 to the circuit board and inserting several values of capacitance in series with C3 showed an immediate improvement in the null. In my case a 10 pF capacitor brought the null down to a 1:1 swr. The total range of all three capacitors in series is now 1.66 to 3.57 pF. Replacing C3 with a capacitor of about 4 pF would probably have produced the same results. Since the capacitors in this circuit form an ac voltage-divider network, changes in this circuit will also affect the wattmeter reading so the wattmeter will also have to be recalibrated.

\*R. Fransen, VE6RF, "Better Balancing of the Heath HM-2102 Wattmeter," *ham radio*, January, 1975, page 56.

In my case no thought was given to changing capacitor C16 since this appears to be a bypass for frequencies outside the desired range of 50 to 160 MHz. Changes here could influence the sensitivity of the bridge and may even bypass energy at the wanted frequencies.

In addition to the above, I found two other slight modifications to be useful. The first concerns wattmeter calibration. According to the instruction manual, power calibration is performed with the wattmeter in the 25-watt range; no provision is made for calibrating in the 250 watt range. However, after calibrating the wattmeter on the low range using 20 watts of power, switching to the high range showed a meter reading of about 16 watts. An examination of the schematic shows that if R8, a 68k resistor, is replaced by a fixed resistor and potentiometer in series, a second calibration can be made on the 250-watt range which is quite accurate. In my case R8 was replaced by a 51k, 1/4-watt fixed resistor in series with a small 25k potentiometer.

The last modification was for convenience more than anything else. In order to locate the remote chassis closer to the coax feedline, the short piece of five-conductor cable supplied with the kit was replaced with similar cable about 6-feet (1.8m) long. One end of the cable was connected inside the cabinet in accordance with the instructions, but the other end was terminated in a small five-pin plug instead of being connected directly to the remote chassis. A matching five-pin socket was mounted on the chassis off to one side of coax connector A. Short leads were then run from the circuit board to the five-pin socket. To prevent rf from reaching the indicator unit through the cable, the ferrite beads supplied with the kit were mounted at the socket instead of on the circuit board. Now the indicator unit and remote chassis can be easily separated.

B. T. Ring, K3VNR  
Riverdale, Maryland

# NEW NEW NEW!!

## TOUCH TONE ENCODERS

### SOLID STATE CRYSTAL CONTROL TONE ENCODERS

- 12 or 16 Touch Tone digits
- Ideal for hand held units
- Choice of 4 keyboard styles
- RF proof
- Temperature, -20° to 150°F
- CMOS IC Encoder

- Bell System Compatibility
- Easy Installation
- Sub-miniature size
- Crystal Controlled
- Single Tone capability
- Low cost



Style A



Style B



Style C



Style D

### SELF-CONTAINED KEYBOARD ENCODERS

Complete 12 or 16 digit Touch Tone keyboard encoders for mounting directly to side of hand-held transceivers. All electronics included WITHIN keyboard, nothing to add inside of transceiver. Only 1/4" thick. Ready for easy installation, just add three connections to unit. RF proof. Select keyboard style when ordering.

DTM

\$49.50

### SUB-MINIATURE TOUCH TONE ENCODER AND KEYBOARD

Touch-Tone encoder for mounting INSIDE hand-held transceiver, keyboard mounts on side of transceiver. P.C. board only 0.8" x 1.2". RF proofed. Assembled and ready for easy installation. Select keyboard style when ordering.

SME

\$29.50

### DO IT YOURSELF ENCODERS

Now, buy all the major parts — "ala-carte" and build your own Touch Tone Encoder. All you need is a Keyboard, Digital Touch Tone Encoder, a 1-MHz crystal, and P.C. board. Parts come with complete set of application notes, schematics and instructions.

|  |         |
|--|---------|
| Keyboard, your choice of keyboard style            | \$8.50  |
| Digital T. T. Encoder with 1-MHz HC-6 Crystal      | \$12.50 |
| Digital T. T. Encoder with 1-MHz Slim HC-5 Crystal | \$13.50 |
| P.C. board 0.8" x 1.2"                             | \$2.50  |
| All resistors, capacitors, and P.C. board          | FREE    |

(With purchase of keyboard, encoder and crystal)

### AUTOMATIC TOUCH TONE DIALER

Automatic mobile telephone dialing is now available. By the push of a single button you can automatically dial up to six separate 7-digit numbers. All solid-state micro-power COS-MOS design. Automatic PTT operation. Programmable to send telephone number only, access code plus telephone number or telephone number plus an identification number. Low profile dash mount, easy installation. Compatible with most radio equipment. Available with keyboard for manual dialing of numbers. Manual operation provides automatic PTT operation with 1 1/2 second transmitter hold.

AD-6

Without keyboard 99.50

AMD-6

With keyboard 119.50

Factory programming of numbers \$7.50.



ORDER TODAY — SEND FOR FREE NEW CATALOG

## DATA SIGNAL, INC.


Successor to Data Engineering, Inc.

2212 PALMYRA ROAD, ALBANY, GA. 31701

912-435-1764





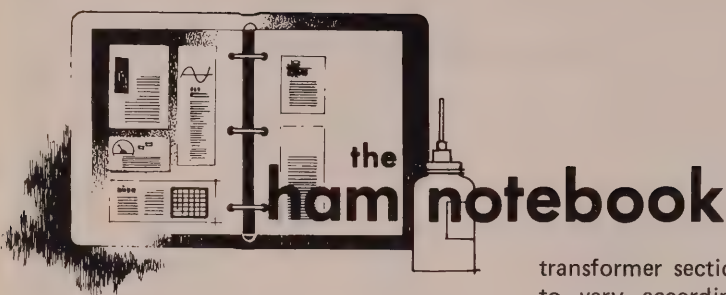

## non-synchronous impedance transformer

In matching one impedance level to another, as in antenna work, the usual device is a quarter-wavelength transformer section whose characteristic impedance is the geometric mean of the two impedances to be matched (fig. 1). When it is necessary to match one transmission line to another, and particularly in coaxial line applications, obtaining a length of line of the proper intermediate characteristic impedance may present a major problem.

The non-synchronous transformer shown in fig. 2 offers a way out of this dilemma. It is composed of two abbreviated lengths of transmission line of the same characteristic impedance as the impedances being matched. The procurement problem is therefore greatly simplified. As indicated in fig. 2, the

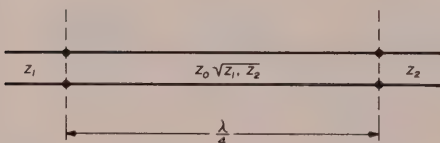


fig. 1. Characteristic impedance of the quarter-wavelength transformer is equal to the geometric mean of the impedances being matched.

transformer section length can be seen to vary according to the impedance ratio. For example, if a 2:1 impedance transformation ratio is required, each section of the transformer would be  $28^{\circ} 8'$ , making the total length about  $56\frac{1}{4}$  degrees, or in terms of wavelength,  $0.156 \lambda$ .

It must be pointed out that the non-synchronous transformer is not al-

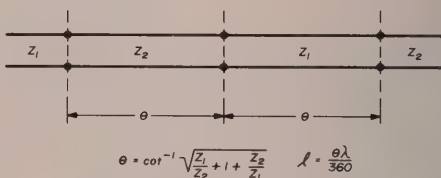


fig. 2. The non-synchronous transformer consists of two lengths of transmission line of the same characteristic impedance as the impedances being matched, with length varying according to the impedance ratio.

ways interchangeable with the quarter-wavelength version. The quarter-wavelength transformer will match an infinite number of impedance pairs, as long as their geometric mean is equal to the characteristic impedance of the transformer. The non-synchronous transformer, on the other hand, will match only the impedance pair for which it was designed. Within these limits, however, the non-synchronous transformer compares very favorably in

bandwidth as well as impedance-matching characteristics, and should find ready application in coaxial impedance-matching networks.

Henry Keen, W5TRS

## drilling aluminum

The following hint for working with aluminum, which may not be common knowledge, was given to me by ham friends in Portugal: apply a drop or two of alcohol when drilling aluminum. It not only makes the work easier but results in a much cleaner cut.

Ralph Cabanillas, Jr., W6IL

## metric conversions for screw and wire sizes

Here's a conversion chart you can use for plugging in metric values for machine screws and wire sizes. *Ham radio* articles have been including metric equivalents for dimensions of physical quantities such as area, length, mass, temperature, and volume. We have wanted to include metric equivalents for machine screws and wire but have only recently been able to obtain equivalent data for this hardware from the International Standards Organization (ISO). The ISO standard has not yet been adopted by all countries, but these

table 2. Wire-size conversion, American (AWG) to metric.

| American standard (AWG) | nearest metric standard (mm) |
|-------------------------|------------------------------|
| 2                       | 6.5                          |
| 4                       | 5.2                          |
| 6                       | 4.1                          |
| 8                       | 3.3                          |
| 10                      | 2.6                          |
| 12                      | 2.1                          |
| 14                      | 1.6                          |
| 16                      | 1.3                          |
| 18                      | 1.0                          |
| 20                      | 0.8                          |
| 22                      | 0.6                          |
| 24                      | 0.5                          |
| 26                      | 0.4                          |
| 28                      | 0.3                          |
| 30                      | 0.25                         |
| 32                      | 0.2                          |

tables will at least give overseas readers an idea of what size the author specified in the nearest metric standard.


Jim Fisk, W1DTY

## short circuit

In DJ2LR's excellent article on crystal oscillators in the June, 1975, issue of *ham radio*, there was an error in fig. 5 (10k pot incorrectly shown). The correct schematic is presented below.


table 1. Thread conversion, American to metric.

| American standard | nearest metric standard |
|-------------------|-------------------------|
| 0-80              | M1.6                    |
| 1-64              | M1.8                    |
| 2-56              | M2                      |
| 3-48 or 3-56      | M2.5                    |
| 4-40              | M3                      |
| 6-32              | M3.5                    |
| 8-32              | M4                      |
| 10-24 or 10-32    | M5                      |
| 12-24 or 12-28    | M6                      |
| 1/4-20            | M7                      |
| 3/8-16            | M10                     |
| 7/16-14           | M12                     |
| 1/2-12            | M12                     |

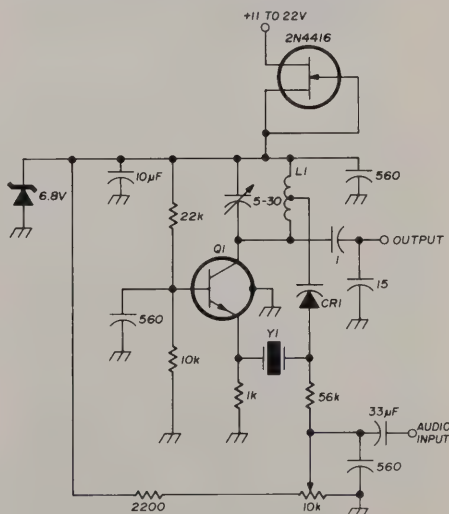

# new products
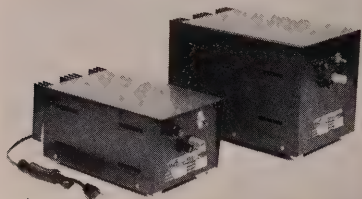
## low-voltage, high-current power supplies



High-current power supplies are an absolute requirement in commercial two-way radio shops and are now on the verge of becoming a requirement in the ham shack. Most of the new solid-state equipment being released for the amateur market is designed for 12-volt operation, either mobile or from a fixed station 12 Vdc supply. The 12-volt ac supply has been a problem in the past because well-regulated, high-current supplies tend to be complex and expensive to build while commercially available supplies are even more expensive and are frequently in short supply. VHF Engineering has recently announced two

inexpensive solid-state 12 Vdc power supply kits which are simple to build and can be used in either commercial or amateur applications. Two models are available, the PS12C for 12 amps, and the PS24C for 24 amps.

The circuit for both power supplies consists of a full-wave dc current source feeding a capacitive filter network and an IC voltage regulator. The IC regulator controls a set of pass transistors and keeps the output voltage consistent to within 2% over a load range of from zero to 20 amps (zero to 10 amps in the PS12). Large heat sinks are provided to dissipate the heat produced by the pass transistors. The 12-amp supply is rated at 10 amps continuous or 12 amps for 50% intermittent duty. The 24-amp supply is rated at 20 amps continuous or 24 amps for 50% intermittent duty. Current limiting prevents damage to the supply in the case of an accidental short circuit. The output voltage of both supplies may be adjusted over a nominal range from 12 to 15 volts. The supplies may be used as general purpose, variable voltage supplies by replacing the voltage controlling resistor with a 10k potentiometer.

The VHF Engineering high-current power supply kits are complete with all parts, computer grade capacitor, epoxy glass circuit boards, styled case, and complete instructions. Average construction time is one evening or less. The 12-amp supply kit, model PS12C, is priced at \$69.95 (\$85.95 wired and tested). The 24-amp supply kit, model PS24C, is \$99.95 (\$114.95 wired and tested). For more information, write to VHF Engineering, 320 Water Street, Binghamton, New York, 13902, or use *check-off* on page 110.




## scientific calculator



The new six-ounce HP-21 from Hewlett-Packard is the smallest and lowest priced model in HP's line, and is designed primarily for scientists, engineers and students. The HP-21 has all of the trigonometric and logarithmic functions of the HP-35. In addition, the user can calculate in either degrees or radians; convert from polar to rectangular coordinates and vice versa; format and round the display in either fixed or scientific notation; and perform register arithmetic (+, -, X, ÷) with the contents of the HP-21's single addressable memory.

The new calculator has five fewer keys (30) than other HP pocket models, but since several keys serve dual functions, the HP-21 is able to perform more functions and operations than the HP-35. Like other HP pocket calculators, the HP-21 features the company's RPN logic system with a four-memory stack that holds intermediate answers and automatically brings them back when needed in a calculation.

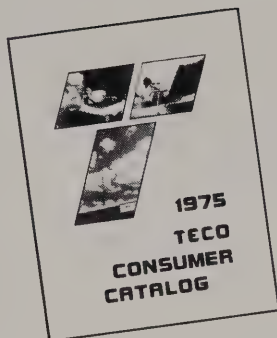The HP-21 comes with an owner's handbook, soft carrying case and an ac adapter/recharger that allows the calculator to be operated on ac while its batteries are recharging. Optional accessories include a security cradle and a reserve power pack (with batteries). The HP-21 will be sold through leading col-



send  
for  
your  
**FREE**  
copy  
now!!!

In it you'll find hundreds of quality consumer electronic products. Amateur radios, CB radios, scanners, antennas, masts, towers, rotors, tools, components, electronic kits, technical books, test gear, digital watches, calculators, portable radios, televisions, microphones, speakers, audio equipment, high fidelity, stereo systems, tape recorders, and much, much more. If it's electronic and it's quality, TECO has it.

WRITE FOR YOUR FREE COPY  
TODAY.



P. O. Box 1050 • Garland, Texas 75040

**USED HAM EQUIPMENT FOR SALE**  
**GOOD SELECTION AVAILABLE**  
**REASONABLE PRICES**

**Walt Van Arsdale, K5SXO**  
**(214) 348-1560**



P O Box 1050 • Garland, Texas 75040



## You're Ahead when mobile with a Larsen Kūlrod® Gain Antenna

- TOPS IN PERFORMANCE ■
- LOW SILHOUETTE GOOD LOOKS ■
- V.S.W.R. LESS THAN 1.3 TO 1 ■
- HANDLES FULL 200 WATTS ■

Larsen Kūlrod VHF Antennas are the result of over 25 years of practical experience in the two-way radio field. They are rugged, reliable and built with infinite care to assure top performance. Models available to fit all standard mounts and for all popular amateur VHF frequencies. Each is equipped with the exclusive Larsen Kūlrod, your assurance of maximum efficiency and no loss of RF through heat. Comes complete with all instructions. Models for 2 meters deliver a full 3 db gain over 1/4 wave whips . . . the 420-440 MHz and 440-460 MHz collinears . . . 5 db gain and full 100 watts capability.

Sold with a full money back guarantee . . . the most liberal in the mobile antenna field. Whether you work via repeater or simplex you deserve to have a Larsen Kūlrod. Get full fact sheet and prices, today.



©Kūlrod . . .  
a trademark of Larsen Electronics

### Larsen Antennas

11611 N.E. 50th Ave. P.O. Box 1686  
Vancouver, WA 98663  
Phone 206/573-2722

lege bookstores and department stores, by direct mail and through HP's calculator sales force. For more information, use *check-off* on page 110.

## 525-MHz uhf prescaler

The new Pagel model 525 uhf prescaler divides frequency by ten to extend the range of any 50 MHz or higher counter to the vhf and uhf bands. The unit also contains a 20 dB preamp for the unscaled 1 MHz to 50 MHz range to improve frequency counter sensitivity to 5 millivolts rms or better. Sensitivity is 50 mV rms at 500 MHz, and 30 mV rms below 400 MHz. A through-line feature with an internal signal sampler can be used with transmitters up to 100 watts (requires an external 50-ohm dummy load). This feature can be used to perform simultaneous power and frequency measurements and is a great time saver.

The model 525 operates from the 117 Vac line or battery power (8 to 15 volts) and may be used for portable or mobile use. Price is \$159. For more information, write to Pagel Electronics, 6742-C Tampa Avenue, Reseda, California 91335, or use *check-off* on page 110.

## envelope detector


The *Modset* recently introduced by David R. Corbin Manufacturing is an envelope detector which can be used with an oscilloscope to provide a clear, hum-free display of the transmitted audio waveform from ssb and a-m transmitters. The *Modset* is built into a rugged, machined aluminum box, and includes input and output impedance matching and an overload protection circuit.

The *Modset* accepts any input signal from a few milliwatts to 25 watts peak power and operates over the frequency

range from 200 kHz to 30 MHz; to 50 MHz with slight reduction in output level. Higher power levels can be monitored by using a short whip antenna or probe instead of the 50-ohm direct coupling. Output level is 0.1 to 10 volts (relative to input power), dc reference plus recovered audio to 10 kHz. The unit is priced at \$29.50.

For more information, write to David R. Corbin Manufacturing, Post Office Box 44, North Bend, Oregon 97459, or use *check-off* on page 110.

## keyer chip adds dash memory

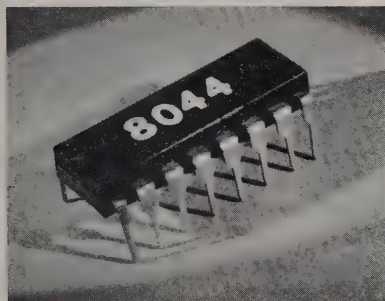


A companion to the 8043 keyer-on-a-chip has been announced by Curtis Electro Devices. Called the 8044, this new cmos IC offers dash memory in addition to the features found on the 8043. These are dot memory, dot, dash and space completion, instant start, key debouncing filters, iambic operation, internal sidetone, weight control and practically zero power dissipation.

An exact pin-for-pin equivalent to the 8043, the 8044 yields a top performance one-IC electronic keyer capable of running on 5 to 12 volt supplies. Usual power supply is a 9-volt transistor radio battery. The 8044 may be plugged into any keyer designed around the 8043 such as that described in the April, 1975, issue of *ham radio*.

The keyer kits are offered. The 8044-1 contains the 8044, a printed-

## LOW COST DIGITAL KITS
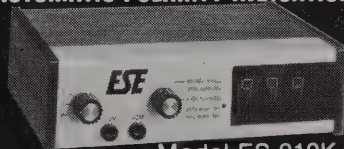
### NEW BIPOLAR MULTIMETER: AUTOMATIC POLARITY INDICATION



Model ES 210K

Displays Ohms, Volts or Amps in 5 ranges • Voltage from 100 Microvolts to 500 V • Resistance from 100 Milliohms to 1 Megohm • Current from 100 Nano Amps to 1 Amp... \$80.00 Case included. (Optional probe \$5.00).

### 40 MHz DIGITAL FREQUENCY COUNTER:

- Will not be damaged by high power transmission levels.
- Simple, 1 cable connection to transmitter's output.



ES 220K — Line frequency time base.

1 KHz resolution . . . 5 digit: \$79.50. Case extra: \$10.00

ES 221K — Crystal time base.

100 Hz resolution . . . 6 digit: \$109.50. Case extra: \$10.00

### DIGITAL CLOCK:



ES 112K/124K • 12 hour or 24 hour clock: \$46.95.

Case extra: Metal \$7.50

### CRYSTAL TIME BASE:

ES 201K — Opt. addition to ES 112K, 124K or 500K


Mounts on board. Accurate to .002% . . . \$25.00

### I.D. REMINDER:

ES 200K — Reminds operator that 9 minutes and 45 seconds have passed. Mounts on ES 112 or 124 board. Silent LED flash: \$10.95. Optional audio alarm \$4 extra.

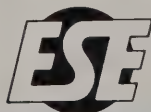**SPECIAL OFFER:** Ask about our unique Clock Kit Special. Prices as low as **\$20.00!**

Each kit contains complete parts list with all parts, schematic illustrations and easy to follow, step by step instructions. No special tools required.




**ORDER YOURS TODAY:**  
Use your Mastercharge or  
BankAmericard  
Money Back Guarantee

505½ Centinela • Inglewood, Ca. 90302 • (213) 674-3021



# NEW! NEW! NEW! DELUXE P.C. KEYS

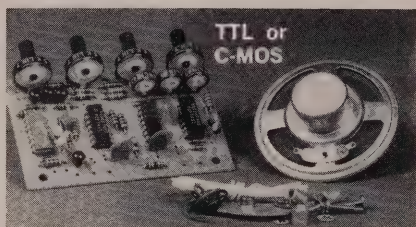

*The keyer you can't afford  
not to buy!*

In either a 5 volt TTL or a 9 volt C-MOS version this new module type IC keyer can be easily adapted to your own custom package or equipment.

Versatile controls allow wide character weight variation, speeds from 5 to 50 w.p.m. plus volume and tone control.

Solid-state output switching saves power, eliminates all those annoying relay problems and is compatible with both grid block and solid-state circuitry.

With its side-tone monitor and 90 day warranty the Data Signal PC Keyer is the one for you.

TTL Keyer Wired \$19.95  
Kit \$14.95

C-MOS Keyer Wired \$24.95  
Kit \$19.95

## DELUXE RECEIVER PREAMPS

Specially made for both OLD and NEW receivers. The smallest and most powerful single and dual stage preamps available. Bring in the weakest signals with a Data Preamp.

| FREQ.<br>(MHz) | USE           | STAGES | DELUXE PREAMPLIFIER |     |         |         |
|----------------|---------------|--------|---------------------|-----|---------|---------|
|                |               |        | GAIN                | dB  | KIT     | WIRED   |
| 14, 21 or 28   | HIGH FREQ.    | SINGLE | 25                  | 2   | \$10.50 | \$13.50 |
|                |               | DOUBLE | 48                  | 2   | \$20.50 | \$26.50 |
| 28 to 30       | OSCAR SPECIAL | SINGLE | 25                  | 2   | \$12.50 | \$15.50 |
|                |               | DOUBLE | 48                  | 2   | \$24.50 | \$30.50 |
| 50 to 54       | 6 METER       | SINGLE | 25                  | 2   | \$10.50 | \$13.50 |
|                |               | DOUBLE | 48                  | 2   | \$20.50 | \$26.50 |
| 108 to 144     | VHF AIRCRAFT  | SINGLE | 20                  | 2.5 | \$ 9.50 | \$12.50 |
|                |               | DOUBLE | 40                  | 2.5 | \$18.50 | \$24.50 |
| 135 to 139     | SATELLITE     | SINGLE | 20                  | 2.5 | \$ 9.50 | \$12.50 |
|                |               | DOUBLE | 40                  | 2.5 | \$18.50 | \$24.50 |
| 144 to 148     | 2 METER       | SINGLE | 20                  | 2.5 | \$ 9.50 | \$12.50 |
|                |               | DOUBLE | 40                  | 2.5 | \$18.50 | \$24.50 |
| 146 to 174     | HIGH BAND     | SINGLE | 20                  | 2.5 | \$ 9.50 | \$12.50 |
|                |               | DOUBLE | 40                  | 2.5 | \$18.50 | \$24.50 |
| 220 to 225     | 1 1/4 METER   | SINGLE | 18                  | 2.5 | \$ 9.50 | \$12.50 |
|                |               | DOUBLE | 35                  | 2.5 | \$18.50 | \$24.50 |
| 225 to 300     | UHF AIRCRAFT  | SINGLE | 15                  | 2.5 | \$ 9.50 | \$12.50 |
|                |               | DOUBLE | 30                  | 2.5 | \$18.50 | \$24.50 |
| 1 thru 30      | HF BROADBAND  | 19-36  | 3                   | —   | —       | \$17.95 |

Write today for complete details

## Data Signal, Inc.

Successor to Data Engineering, Inc.

2212 PALMYRA ROAD, ALBANY, GA. 31701

912-435-1764

circuit card, a socket and instruction manual. The 8044-2 kit contains the foregoing plus the parts necessary to complete a deluxe keyer exclusive of chassis, jacks, switches, speaker and knobs. This keyer will key  $\pm 300$  volts at 200 mA. The 8044 is priced at \$24.95, the 8044-1 kit at \$32.95 and the 8044-2 is \$57.95. Like the 8043, the 8044 carries a lifetime guarantee.

For further information, contact Curtis Electro Devices, Box 4090, Mountain View, California 94040, or use *check-off* on page 110.

## essential formulae for electronic and electrical engineers

This new book by Noel M. Morris provides all of the essential electrical and electronic formulas required by students, technicians and professional engineers. The rapid growth of electronics technology has made it practically impossible to memorize all the formulas which are required. This book contains all the basic equations in the fields of electronics, electrical engineering, control systems, measurements, logic, telecommunications and mathematics. Sections include electrostatics and electromagnetism, complex numbers, ac and dc circuits, transients, amplifiers and oscillators, modulation and transmission lines. The SI system of units is used throughout.

This book assumes that the reader is familiar with each of the formulas, so it does not provide any typical examples or information describing how to use them. However, for the serious worker who frequently needs this information, this valuable book provides it all in one place. 26 pages, softbound, 8 1/4 x 11 1/2 inches, \$2.95 from Halstead Press, a Division of John Wiley & Sons, 605 Third Avenue, New York, New York 10016.


## tracking voltage regulators

Three new dual tracking voltage regulator ICs are now available from National Semiconductor. Called the LM125, LM126 and LM127 (LM325, LM326 and LM327 for commercial temperature range), the regulators are designed to provide balanced positive and negative output voltages at currents up to 100 milliamps. Input voltage can be as high as  $\pm 30$  volts, and there is a provision for external adjustable current limiting.

The LM125 provides tracking outputs of  $\pm 15$  volts making it ideal for op amp power supplies. It features output voltages balanced to within 1% and line and load regulation of 0.06%. The LM126 provides  $\pm 12$  volt outputs balanced to within 1% and features line and load regulation of 0.08%, while the LM127 has +5 and -12 volt outputs which are compatible with most mos circuits.

For more information, contact National Semiconductor Corporation, 2900 Semiconductor Drive, Santa Clara, California 95051, or use *check-off* on page 110.

## stepped drill bit

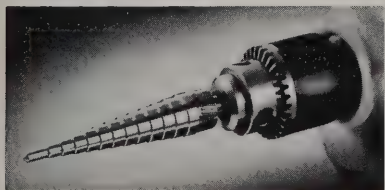

The Unibit,<sup>®</sup> a versatile single flute step drill that does the work of thirteen conventional twist drill bits, is now available. The first Unibit model, designed to fit any three-jawed  $\frac{1}{4}$ " (6.5mm) chuck, is intended primarily for use with hand-held electric drills. It has a starting diameter of  $\frac{1}{8}$ " (3mm)



**The  
"STANDARD"  
by Heights**

Light,  
permanently  
beautiful  
**ALUMINUM**  
towers

**THE MOST  
IMPORTANT  
FEATURE OF  
YOUR ANTENNA  
IS PUTTING  
IT UP WHERE  
IT CAN DO  
WHAT YOU  
EXPECT.  
RELIABLE DX —  
SIGNALS EARLIEST IN  
AND LAST OUT.**

**ALUMINUM**  
Self-Supporting  
Easy to Assemble  
and Erect  
All towers mounted  
on hinged bases  
Complete Telescoping  
and Fold-Over  
Series available

And now, with motorized options, you can crank it up or down, or fold it over, from the operating position in the house.


Write for 12 page brochure giving dozens of combinations of height, weight and wind load.

**ALSO TOWERS FOR WINDMILLS**

**HEIGHTS  
MANUFACTURING CO.**

In Almont Heights Industrial Park  
Almont, Michigan 48003
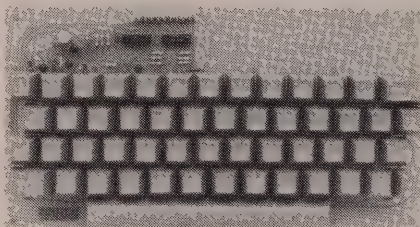
# NEW ★ **SWT2** KEYBOARD and ENCODER KIT



- \* 53 Keys
- \* One Chip MOS Encoder
- \* Upper and Lower Case
- \* Standard ASCII Output
- \* Two Key Lockout

We are happy to announce a new addition to our keyboard and encoder line. Our new KBD-3 uses a one chip MOS encoder system to give you maximum possible features with a minimum number of parts.

This keyboard produces a standard ASCII coded output that is compatible with TTL, DTL, RTL and MOS logic systems. You have the option of wiring the kit for normal typewriter style output in both upper and lower case letter, or all upper case format. All common machine control commands such as "line feed", "return", "control", etc. are provided on the keyboard. Four uncommitted or extra keys are available for your specific use requirements. Two of these have isolated output lines to the connector for special functions such as "here is".

Keyswitches are standard, full travel style with gold plated contacts for long troublefree service. Requires +5 Volts and -12 Volts.

**KBD-3 Keyboard and Encoder Kit \$49.50 ppd**

**SOUTHWEST TECHNICAL  
PRODUCTS CORP.**

219 W. Rhapsody Dept. HR  
San Antonio, Texas 78216

and each of twelve succeeding steps removes material in 1/32" (0.8mm) increments up to 1/2" (12.5mm) diameter. Each step penetrates material up to 1/8" (3mm) thick.

The Unibit is made of industrial grade high-speed steel, heat treated and tempered to assure maximum strength for long wearing, rugged use. It exhibits superior characteristics when drilling thinner gauges of sheet metals such as steel, copper, brass and aluminum as well as most plastics and wood. Starting a hole with the Unibit is a snap because its single flute design eliminates skidding and the need for center punching. Chatter and vibration are also kept to a minimum. Its design geometry also helps prevent the Unibit from penetrating softer material too fast and "hogging-in."

Many other operations, considered difficult with conventional twist drills, can be conveniently accomplished using the Unibit. Its unique cutting edge angle automatically de-burrs a hole, eliminating a time consuming countersink tool change. The Unibit allows for sizing or aligning and reaming operations, drilling intersecting holes as well as enlarging a slot or a square into a round hole. In addition, the Unibit is available with a special non-slip key on its shank that prevents it from spinning in the chuck.

The newest Unibit drill, Model II, enables the drilling of eight round holes, sizes 9/16-inch (14.5mm) to one-inch (25.5mm), with a single bit. The Unibit II requires a starting diameter of 1/2-inch (12.5mm) or larger and removes material in 1/16-inch (1.5mm) increments in eight steps.

Designed for use with any 1/2-inch drill chuck, Unibit II works equally well with hand-held electric drills as well as drill press equipment. The Unibit II is made of industrial grade, high speed steel, heat treated and tempered to assure maximum strength for long wearing use. It's patented design features a single flute to assure smooth penetra-



tion of materials and, unlike conventional twist drills, it is easily sharpened without special tools. Unibit II is extremely versatile and allows the user to perform many operations including intersecting holes, making round holes from slots, hole de-burring and a "hole-opening" reamer.

Unibit literature, information and prices are available by contacting the Unibit Corporation, Box 331, Department 2, Wyoming, New York 14591, or by using *check-off* on page 110.

## how to use ic logic elements

Just released and completely illustrated, this new book by Jack Streater is designed to help the engineer or technician who has not previously used or designed digital logic circuits meet the challenge of digital ICs in electronics. The practical problems and limitations of connecting IC logic elements into logic systems to accomplish the required result are thoroughly covered.


The first two chapters cover binary, BCD, and decimal number systems and Boolean algebra with its applications to simple switching circuits. The next two chapters discuss gates and gate combinations, and the following chapter explains bistable elements and their uses. Then the logic families (RTL, DTL, TTL, ECL, CTL or CML, MOS and diode logics) are discussed and compared.

Another chapter is devoted to off-the-shelf logic elements — breadboarding, testing, troubleshooting and locating sources of data on integrated circuits. The final chapter includes experiments to aid in understanding the operation of logic circuits. A glossary of digital terms has been included as an appendix.

Soft cover, 160 pages, \$4.50 from HR Books, Greenville, New Hampshire 03048.

# NEW! HR-440

## 12 Channel 440 MHz FM Transceiver

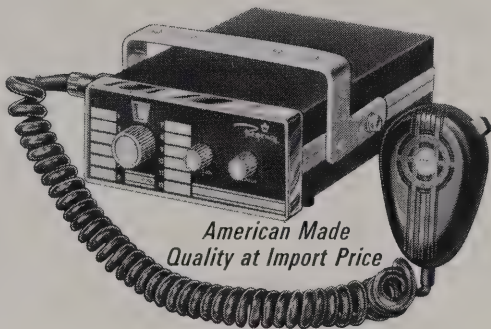

### Delivers 10 Watts of Power and 12 Channel Capability

You'll like the crystal clear transmit and receive performance of this compact 440 MHz unit . . . and so will those listening.

Solid state design brings you the best in American Made circuitry. Features include Automatic Frequency Control and UHF power module. Frequency range is 420-450 MHz, with 0.5  $\mu$ v tune-up sensitivity and 3 watts audio output. No need to worry about current drain, either. And all of this for the low, low price of only

**\$349<sup>00</sup>**

*Regency* **ELECTRONICS, INC.**

7707 RECORDS STREET  
INDIANAPOLIS, INDIANA 46226

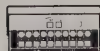
### An FM Model For Every Purpose . . . Every Purse



**HR-6**  
12 Channel-25 Watts  
6 Meter FM Transceiver



**HRT-2**  
5 Channel Hand-Held  
2 Meter FM Transceiver



**ACT 10H/L/U**  
3 Band-10 Channel  
FM Scanner Receiver

# Heathkit "104"...



## ...new performance standard for SSB transceivers

A revolutionary "new generation" transceiver. It's completely solid-state and totally broadbanded to eliminate preselector tuning. And the output can be instantly switched from 100 watts to 1 watt. The true digital readout offers resolution down to 100 Hz and outstanding tuning accuracy. Receiver intermodulation distortion has been minimized and there are very few active devices ahead of the highly selective crystal filter. Adjacent channel overload is negligible, yet sensitivity is better than 1  $\mu$ V (.6  $\mu$ V typical) and front-end overload is dramatically reduced. The "104" is 12 VDC-powered for mobility and the optional HP-1144 fixed station supply fits inside the SB-604 speaker cabinet. An optional noise blanker can be installed in the "104" and an optional 400 Hz crystal filter improves CW selectivity.

Kit SB-104, 31 lbs., mailable .....669.95\*  
 Kit SBA-104-3, 400 Hz CW crystal filter, 1 lb., mailable .....36.95\*  
 Kit SBA-104-1, Noise blanker, 1 lb., mailable ....26.95\*  
 Kit SBA-104-2, Mobile mount, 6 lbs., mailable ....36.95\*  
 Kit HP-1144, Fixed station power supply, 28 lbs., mailable .....89.95\*

### SB-230 — the lowest-cost conduction-cooled linear around

The SB-104's "silent partner." 1200 watts PEP or 1000 watts CW from less than 100 watts drive. It's rated at 400 watts input for slow-scan TV and RTTY. The high-efficiency Eimac 8873 triode is double-shielded to reduce stray RF and a massive heat sink replaces noisy fans and blowers. The "230" assembles in just 15 to 20 hours with no alignment.

Kit SB-230, 40 lbs., mailable .....319.95\*

### SB-634 station console combines 5 convenient accessories

The "634" performs 5 important functions—a 10-minute digital ID timer with visual or visual and audible indicators an RF wattmeter that reads 0-200- or 0-2000 watts with  $\pm 10\%$  accuracy, an SWR bridge, a hybrid phone patch that can be used manually or with VOX control, and a 24-hour digital clock that runs independently of all other functions. It's a must for every well equipped station.

Kit SB-634, 14 lbs., mailable .....179.95\*

### SB-614 station monitor shows you how clean your signal is

Highly visible 1½ x 2" CRT detects problems that can reduce the effectiveness of your signal — non-linearity, insufficient or excessive drive, poor carrier or sideband suppression, regeneration, parasitics and CW key clicks. It monitors SSB, CW and AM signals from 80 to 6 meters. Push-pull drive for keystone free trace; automatic sync sweep generator with 3 ranges from 10 Hz to 10 kHz. Can be used as an ordinary oscilloscope from 10 Hz to 50 kHz.

Kit SB-614, 17 lbs., mailable .....139.95\*

### SB-644 remote VFO

Designed exclusively for the SB-104. It provides split transmit and receive control and you aren't frequency-limited in any way—transmit at one end of the band, receive at the other. The "644" even has two crystal positions for fixed-frequency control. The "644" has a linear dial, but the exact frequency is displayed on the "104's" digital readout. The display automatically changes when switching from transmit to receive.

Kit SB-644, 10 lbs., mailable .....119.95\*

### SB-604 station speaker — response-tailored to SSB

Designed to match the SB-104 in styling and performance. The "604" uses a 5 x 7", 3.2-ohm speaker. And there's room inside for the HP-1144 power supply. With connector cable and plug.

Kit SB-604, 8 lbs., mailable .....29.95\*



# Heathkit "202"...



## ...top value standard for 2-M transceivers

The HW-202 puts you on "two" at a price you want to pay, with the features you need. It operates on any 2 MHz segment from 143.9 to 148.3 with independent selection of 6 transmit and 6 receive channels, and all 12 can be netted. A solid 10 watts min. transmitter output, a hot 0.5  $\mu$ V receiver sensitivity. Dual-gate MOSFET front end... IC IF...dual conversion...10.7 MHz crystal filter...built-in hash filter/voltage regulator...crystals for 146.94 MHz...push-to-talk mike...quick-connect cable for 12 V hookup...antenna coax jack...quick-release gimbal mount...complete alignment procedures using the front panel meter...and a complete line of accessories to put you on "two" with maximum versatility and low cost.

Kit HW-202, 11 lbs., mailable .....179.95\*

### Crystal Certificates.

Order from Heath, mail certificates to crystal mfr., get the crystals you specify, postpaid.

HWA-202-6, one Transmit Crystal certificate .....5.95\*

HWA-202-7, one Receive Crystal certificate .....5.95\*

### Tone Burst Encoder.

Put this in your "202" so you don't have to whistle while you work repeaters. 4 tone buttons can be preset to any tone between 1800 and 2500 Hz. Burst duration is adjustable. Stability is  $\pm 1\%$  from  $-30^\circ$  to  $+50^\circ$ C. Mounts behind removable front panel bezel of your "202".

HWA-202-2, 1 lb., mailable .....26.95\*

### AC Supply.

To work your "202" as a fixed station. Delivers 13.8 VDC @ 2.2A. with better than 1% regulation.

Circuit breaker protected. Wire it for 120 or 240 VAC. Includes 3-wire line cord and transceiver cables.

HWA-202-1, 7 lbs., mailable .....32.95\*

### 40-watt 2-M Amplifier.

Hauls up fringe repeaters by putting out a minimum 40 W from 10 W input. Only 7A battery drain, and so compact (3 x 4 1/4 x 5 1/2) that it fits anywhere. Internal antenna changeover relay and sensing circuitry for automatic T/R switching. Tuned input/output circuits for low spurs and coverage of any 1.5 MHz portion of 143-149 MHz.

Kit HA-202, 4 lbs., mailable .....59.95\*

**Mobile 2-M antenna;** 5/8-wave whip w. rear deck clip mount has 3.4 dB gain over 1/4-wave. Inc. 17' coax.

HWA-202-3, 2 lbs., mailable .....19.95\*

**Fixed 2-M antenna;** 5/8-wave vertical w. radials has 3.4 dB gain over 1/4-wave; for mast mt.; less coax.

HWA-202-4, 4 lbs., mailable .....17.95\*

**New mobile 2-M colinear;** 1/4 & 5/8-wave phased radiators; 5.2 dB gain; swivel trunk lip mt. 17' coax.

HWA-202-9, 3 lbs., mailable .....37.95\*

**New fixed 2-M colinear;** two 5/8-wave phased radiators; 6 dB gain; for mast mt. Heavy duty. Less coax.

HWA-202-10, 8 lbs., mailable .....47.95\*

## Send for FREE Catalog

Heathkit

|   |   |           |
|---|---|-----------|
| HEATH<br>Schlumberger   | Heath Company,<br>Dept. 122-09<br>Benton Harbor, MI 49022 |           |
| <input type="checkbox"/> Please send free catalog<br><input type="checkbox"/> Enclosed is _____, please send models _____ |   |           |
| NAME _____  |   |           |
| ADDRESS _____   |   |           |
| CITY _____  | STATE _____   | ZIP _____ |
| *MAIL ORDER PRICES; F.O.B. FACTORY.<br>PRICES & SPECIFICATIONS SUBJECT TO CHANGE WITHOUT NOTICE.                          |   | AM-313B   |





**\*Special Requested Items\***

[illegible]

# CAPACITOR CORNER

50 VOLT CERAMIC DISC CAPACITORS

|     |      |        |  |     |      |    |        |   |       |
|-----|------|--------|--|-----|------|----|--------|---|-------|
| .05 | 1049 | 50 100 |  | .05 | 0001 | .1 | 35V 28 | 1 | 47 50 |
| .1  | 04   |        |  | .1  | 0002 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0003 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0004 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0005 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0006 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0007 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0008 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0009 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0010 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0011 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0012 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0013 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0014 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0015 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0016 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0017 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0018 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0019 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0020 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0021 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0022 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0023 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0024 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0025 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0026 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0027 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0028 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0029 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0030 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0031 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0032 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0033 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0034 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0035 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0036 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0037 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0038 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0039 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0040 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0041 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0042 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0043 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0044 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0045 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0046 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0047 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0048 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0049 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0050 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0051 | .1 | 35V 28 | 1 | 50    |
| .1  | 04   |        |  | .1  | 0052 | .1 | 35V 28 | 1 | 50    |

## 20% DIPPED TANTALUM SOLID CAPACITORS

|    |        |   |            |    |    |    |    |    |    |
|----|--------|---|------------|----|----|----|----|----|----|
| .1 | 35V 28 | 1 | 25 28V 31  | 21 | 21 | 21 | 21 | 21 | 21 |
| .1 | 35V 28 | 1 | .25 28V 31 | 21 | 21 | 21 | 21 | 21 | 21 |
| .1 | 35V 28 | 1 | .25 28V 31 | 21 | 21 | 21 | 21 | 21 | 21 |
| .1 | 35V 28 | 1 | .25 28V 31 | 21 | 21 | 21 | 21 | 21 | 21 |
| .1 | 35V 28 | 1 | .25 28V 31 | 21 | 21 | 21 | 21 | 21 | 21 |
| .1 | 35V 28 | 1 | .25 28V 31 | 21 | 21 | 21 | 21 | 21 | 2  |

[illegible]

|                          |  |  |  |
|--------------------------|--|--|--|
| ASS'T 1                  | 28 OHM 50 OHM 35 OHM 50 OHM 150 OHM 100 OHM 100 OHM 150 OHM 150 OHM  | 1/4 WATT 5% - 50 PCS.  | 1/4 WATT 5% - 50 PCS.                      |
| ASS'T 2                  | 430 OHM 560 OHM 460 OHM 270 OHM 270 OHM 270 OHM 270 OHM 270 OHM  | 1/4 WATT 5% - 50 PCS.  | 1/4 WATT 5% - 50 PCS.                      |
| ASS'T 3                  | 1.2K 1.5K 1.8K 2.2K 2.7K 3.3K 3.9K 4.7K  | 1/4 WATT 5% - 50 PCS.  | 1/4 WATT 5% - 50 PCS.                      |
| ASS'T 4                  | 3.3K 3.9K 4.7K 5.6K 6.8K 8.2K 10K 12K  | 1/4 WATT 5% - 50 PCS.  | 1/4 WATT 5% - 50 PCS.                      |
| ASS'T 5                  | 22K 27K 33K 39K 47K 56K 68K 82K  | 1/4 WATT 5% - 50 PCS.  | 1/4 WATT 5% - 50 PCS.                      |
| ASS'T 6                  | 150K 180K 220K 270K 330K 390K 470K 560K  | 1/4 WATT 5% - 50 PCS.  | 1/4 WATT 5% - 50 PCS.                      |
| ASS'T 7                  | 1M 1.2M 1.5M 1.8M 2.2M 2.7M 3.3M 3.9M  | 1/4 WATT 5% - 50 PCS.  | 1/4 WATT 5% - 50 PCS.                      |
| PRIME INTEGRATED CIRCUIT | SN7400 7401 7402 7403 7404 SN7410 7411 7412 7413 7414 SN7447 7490 7491 74100 74121 SN74145 74175 74180 74193 74203 74210 74211 74212 74213 74214 74215 74216 74217 74218 74219 74220 74221 74222 74223 74224 74225 74226 74227 74228 74229 74230 74231 74232 74233 74234 74235 74236 74237 74238 74239 74240 74241 74242 74243 74244 74245 74246 74247 74248 74249 74250 74251 74252 74253 74254 74255 74256 74257 74258 74259 74260 74261 74262 74263 74264 74265 74266 74267 74268 74269 74270 74271 74272 74273 74274 74275 74276 74277 74278 74279 74280 74281 74282 74283 74284 74285 74286 74287 74288 74289 74290 74291 74292 74293 74294 74295 74296 74297 74298 74299 74300 74301 74302 74303 74304 74305 74306 74307 74308 74309 74310 74311 74312 74313 74314 74315 74316 74317 74318 74319 74320 74321 74322 74323 74324 74325 74326 74327 74328 74329 74330 74331 74332 74333 74334 74335 74336 74337 74338 74339 74340 74341 74342 74343 74344 74345 74346 74347 74348 74349 74350 74351 74352 74353 74354 74355 74356 74357 74358 74359 74360 74361 74362 74363 74364 74365 74366 74367 74368 74369 74370 74371 74372 74373 74374 74375 74376 74377 74378 74379 74380 74381 74382 74383 74384 74385 74386 74387 74388 74389 74390 74391 74392 74393 74394 74395 74396 74397 74398 74399 74400 74401 74402 74403 74404 74405 74406 74407 74408 74409 74410 74411 74412 74413 74414 74415 74416 74417 74418 74419 74420 74421 74422 74423 74424 74425 74426 74427 74428 74429 74430 74431 74432 74433 74434 74435 74436 74437 74438 74439 74440 74441 74442 74443 74444 74445 74446 74447 74448 74449 74450 74451 74452 74453 74454 74455 74456 74457 74458 74459 74460 74461 74462 74463 74464 74465 74466 74467 74468 74469 74470 74471 74472 74473 74474 74475 74476 74477 74478 74479 74480 74481 74482 74483 74484 74485 74486 74487 74488 74489 74490 74491 74492 74493 74494 74495 74496 74497 74498 74499 74500 74501 74502 74503 74504 74505 74506 74507 74508 74509 74510 74511 74512 | \$5.95 ASST<br>\$5.95 ASST<br>\$3.95 ASST<br>\$3.95 ASST<br>\$10.95 ASST | 50 TPL<br>MSI TPL<br>CROS<br>LINEAR<br>JAN |

Satisfaction Guaranteed. \$5.00 Min. Order. U.S. Funds.  
California Residents: Add 6% Sales Tax.  
Write for FREE 1975 Data Sheets .25¢ each


JAMES

P.O. BOX 822, BELMONT, CA. 94002

PHONE ORDERS - (415) 592-8097

[illegible][illegible]

# five new breadboard testers from

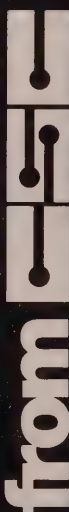

Continental Specialties Corp. offers a total line of breadboard test devices ... everything from inexpensive kits to high-power professional units and logic monitors too. Each high quality, compact unit comes with a guarantee of complete satisfaction or your money back within 10 days. Here are but five of the "hottest" items we make.



## Power for the Professional!

New Proto Boards  
PB-203 and PB-203A  
with built-in  
regulated  
short-proof  
power supplies!

Ready-to-use. Just plug in and start building! 2 extra floating 5-way binding posts for external signals (PB-203 only). Completely self-contained with power switch, indicator lamp and power fuse. 24 14-pin DIP capacity. All metal construction ... no chipping or cracking as with plastic cases. Two-tone quality case makes both PB-203 and PB-203A aesthetically, as well as technically attractive.



## PROTO BOARD 100

A complete mini-  
breadboard budget  
kit with full IC capacity

PB-100  
Complete Kit ...

**19<sup>95</sup>**

Add \$1.50  
shipping/handling

The PB-100 is a low cost, big 10 IC capacity breadboard kit, complete down to the last nut, bolt and screw. Includes 2 QT-35S Sockets; 1 QT-35B Bus Strip; 2 5-way binding posts; 4 rubber feet; screws and easy assembly instructions. 4.50" (114.3mm) wide x 6.00" (152.4mm) long x 1.35" (34.3mm) high. Order your PB-100 kit! Start building and testing now!



## PB-203

- 3 QT-59S Sockets
- 4 QT-59B Bus Strips
- 1 QT-47B Bus Strip
- Fuse • Power Switch
- Power-On Light
- 9.75" L x 6.6" W x 3.25" H
- Weight: 5 lbs.
- 5V, 1 AMP regulated power supply

# 75.

Add \$2.50 shipping/handling

### OUTPUT SPECIFICATIONS

**Output Voltage** 5V  $\pm$  1/4V  
**Ripple & Noise** @ 1/2 AMP  
 10 millivolts  
**Load Regulation** Better than 1%

## PB-203A

- 3 QT-59S Sockets
- 4 QT-59B Bus Strips
- 1 QT-47B Bus Strip
- Fuse • Power Switch
- Power-On Light
- 9.75" L x 6.6" W x 3.25" H
- Weight: 5 lbs.
- 5V, 1 AMP regulated power supply (same as PB-203)
- +15V, 1/2 AMP regulated power supply
- -15V, 1/2 AMP regulated power supply

# 120.

Add \$2.50 shipping/handling

### OUTPUT SPECIFICATIONS

**Output Voltage** 15V, internally adjustable  
**Ripple & Noise** @ 1/4 AMP,  
 10 millivolts  
**Load Regulation** Better than 1%

## PROTO-CLIP offers power-on... hands-off signal tracing ... under \$5!

Trace signals or troubleshoot fast. Inject signals or wire unused circuits into existing boards. Flexible plastic web\* construction eliminates springs and pivots. Plus, the narrow throat is perfect for high density pc boards.

Order now!

PC-14 14-pin Proto-Clip: \$4.50 ea.

PC-16 16-pin Proto-Clip: \$4.75 ea.

Add \$1.00 shipping and handling

**Scope probes, test leads lock onto unique toothed grips**

©COPYRIGHT CONTINENTAL SPECIALTIES CORPORATION 1975

All Continental Specialties breadboard test devices are made in the USA, and are available off-the-shelf from your local distributor or CSC. Direct purchases may be charged on BankAmericard, Master Charge or American Express. You get a FREE English/Metric conversion slide rule with each order. Foreign orders please add 10% for shipping/handling. Prices are subject to change. Write or phone for complete illustrated catalog, plus the name and address of the CSC dealer nearest you.

\*Patents Pending



## CONTINENTAL SPECIALTIES CORP.

44 Kendall St., Box 1942, New Haven, CT 06509 • 203/824-3103

West Coast Office: Box 7808, San Francisco, CA 94119 • 415/383-4207

CANADA: Available thru Len Finkler Ltd., Ontario

## Continental

## Specialties Corp.


## LOGIC MONITOR


brings ICs to life faster than a scope ... safer than a voltmeter

LM-1 **84.95 each**

Add \$2.50 shipping/handling

Self-contained, pocket size. No adjustments or calibrations needed. Puts life into digital designs. Just clip to any DIP IC up to 16 pins. NO POWER SUPPLY NEEDED! Simultaneously displays static and dynamic logic states of DTL, TTL, HTL or CMOS on 16 large high intensity LEDs. Watch signals work through counters, shift registers, timers, adders, flip flops, decoders, entire systems. Concentrate on signal flow and input/output truth tables. Forget probe grounds, pin counting or sync polarity. Precision plastic guides and flexible plastic web\* insure positive connections. Versatile. Fast. Accurate. Indispensable. Order yours today!

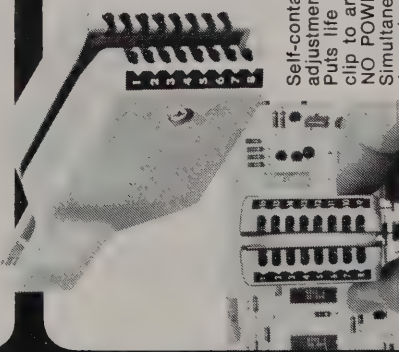

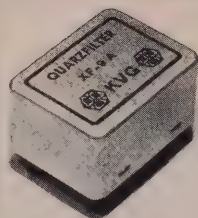

## CRYSTAL FILTERS and DISCRIMINATORS



by  
K.V.G.

### XF9-NB

We are pleased to announce the latest addition to the KVG high performance 9 MHz crystal filter line. The XF9-NB is a 500 Hz band width filter designed for CW reception and narrow band digital data circuits. Its characteristics almost eliminate the ringing effect present in less sophisticated narrow band filters. The XF9-NB, like all other KVG 9 MHz filters, has internal input and output transformers to facilitate matching its natural impedance to adjacent circuit stages.

Write for detailed specifications.

Export inquiries invited.

Price \$63.95

Postage 50¢

## VHF PREAMPLIFIERS

We are pleased to announce the introduction of VHF pre-amplifiers for the 50, 144 and 220 MHz bands. They consist of a two stage wide band amplifier (no tuning required) with twin outputs for feeding two independent receivers. They are especially useful for rejuvenating older converters/receivers. Additionally the twin output feature has many advantages for twin operating and similar multi-channel receiver situations. They are constructed on glass-epoxy G10 P.C. board mounted in our standard die-cast aluminum box.

|                   | MMA 50  | MMA 144 | MMA 220 |
|-------------------|---------|---------|---------|
| Freq. Range (MHz) | 50-54   | 144-148 | 220-225 |
| Nom. Gain         | 20dB    | 16dB    | 15dB    |
| N.F. (typical)    | 2.5dB   | 2.8dB   | 3.4dB   |
|                   | \$29.95 | \$29.95 | \$34.95 |

Power 12V D.C. at 20ma typical

1 1/4" x 2 1/2" x 4 1/2" plus connectors

Specifications apply to 50 ohm input/output system.

Shipping \$1.00.

## VHF CONVERTERS UHF

|                  | Mmc 50  | Mmc 144 | Mmc 220 | Mmc 432 | Mmc 1296  |
|------------------|---------|---------|---------|---------|-----------|
| RF Freq. (MHz) + | 50-54   | 144-148 | 220-224 | 432-436 | 1296-1300 |
| IF Freq. +       | 28-32   | 28-32   | 28-32   | 28-32   | 28-32     |
| N.F. (typical)   | 2.5dB   | 2.8dB   | 3.4dB   | 3.8dB   | 9.0dB     |
| Nom. Gain        | 30dB    | 30dB    | 26dB    | 28dB    | 20dB      |
|                  | \$53.70 | \$53.70 | \$64.45 | \$64.45 | \$85.95   |

Power 12V D. C.

1 1/4" x 2 1/2" x 4 1/2" + connectors

Very low N. F. units on special order.

+Other ranges, amateur & commercial, to order.

Shipping: Filters, \$.50: Converters, \$1.00

**si**

**SPECTRUM**


**INTERNATIONAL**

**BOX 1084 CONCORD**


**MASSACHUSETTS 01742**

**U. S. A.**


## WANTED FOR CASH

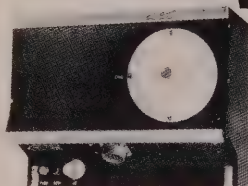

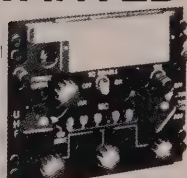**490-T Ant. Tuning Unit**  
(Also known as CU1658 and CU1669)




**ARC-51 Control Box**

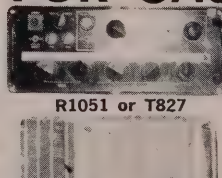

**R1051 or T827**

**ARC-51 Transceiver**

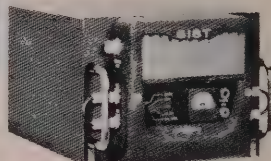

**618-T Transceiver**  
(also known as MRC95, ARC94, ARC102, or VC102)


Highest price paid for these units. Parts purchased. Phone Ted, W2KUW collect. We will trade for new amateur gear. GRC106 and PRC74 also required. See HR last issue for other equipment required.

### THE TED DAMES CO.

308 Hickory Street  
(201) 998-4246

Arlington, N.J. 07032  
Evenings (201) 998-6475

# Thousands...

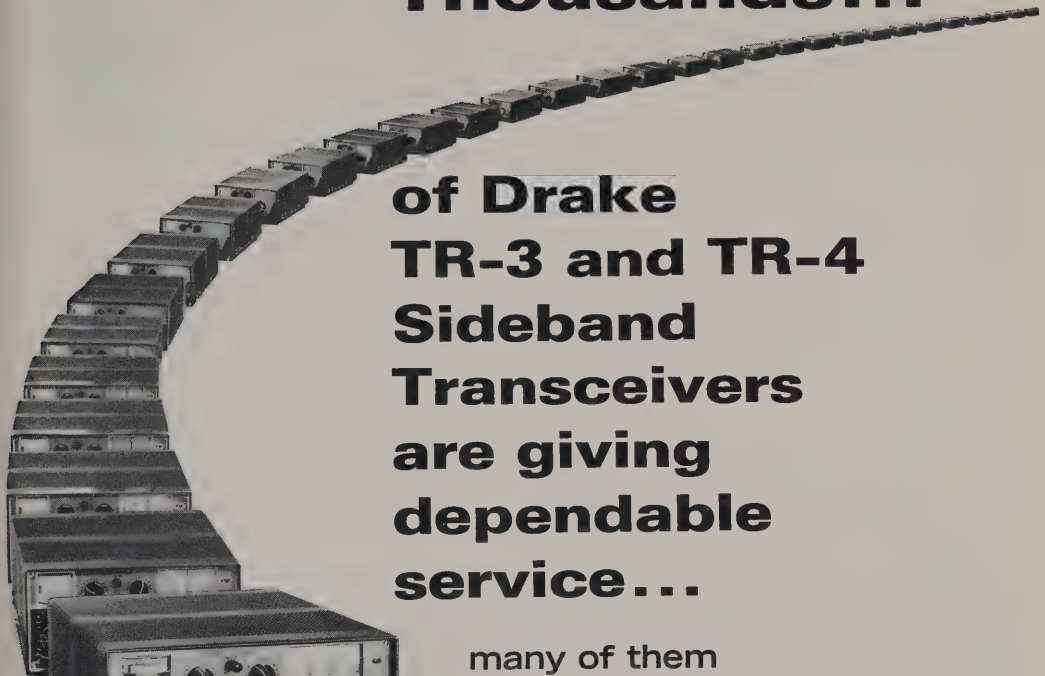

**of Drake  
TR-3 and TR-4  
Sideband  
Transceivers  
are giving  
dependable  
service...**

many of them  
since 1963!



And now **TR-4C**  
the Drake  
is already surpassing their record!

Now at your dealer's

**R. L. DRAKE COMPANY**

540 Richard St., Miamisburg, Ohio 45342  
Phone: (513) 866-2421 Telex: 288-017






## SPECIFICATIONS

*Include \$2.50 to cover  
Postage and Insurance*




**Phone:**  
**405-273-9024**

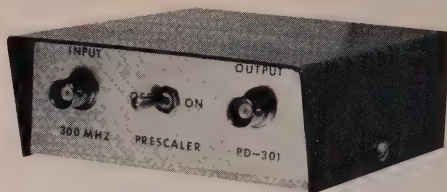

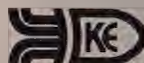**Add \$1.50 Postage & Insurance**

Model PD 301 is a 300 MHz prescaler designed to extend the range of your counter ten times. This prescaler has a built-in amp with a sensitivity of 50 mV at 150 MHz, 100 mV at 260 MHz, 175 mV at 300 MHz. The 95H90 scaler is rated at 320 MHz. To insure enough drive for all counters, a post amp. was built-in. The pre-amp has a self contained power supply regulated at 5.2V + .08%. (Input 50 Ohms, Output Hi Z)

All prescalers are shipped in a 4" by 4" by 1½" cabinet. All are wired and calibrated.



**K-ENTERPRISES 1401 E. Highland • Shawnee, Okla. 74801**

- Learn the truth about your antenna.
- Find its resonant frequency.
- Find R and X off-resonance.
- Independent R & X dials greatly simplify tuning beams, arrays.
- Compact, lightweight, battery operated.
- Simple to use. Self contained.
- Broadband 1-100 MHz.
- Free brochure on request.
- Order direct. \$39.95 PPD U.S. & Canada  
(add sales tax in Calif.)

BOX 455, ESCONDIDO, CA 92025

FREQUENCIES/CALL LETTERS/  
AREAS OF OPERATION

- Police
- Fire
- Ambulance
- Paramedic
- Rescue Squad
- Government

## 1975 EDITION

- 9 Volumes now available
- Price . . . \$4.95 per volume, plus postage and handling.
  - .80 per volume for first class or
  - .30 per volume for fourth class.
- New Jersey residents add 25¢ per volume for sales tax.
- VOLUME 1 . . . Connecticut, Maine, Massachusetts, New Hampshire, New York, Rhode Island, Vermont
- VOLUME 2 . . . Delaware, Maryland, New Jersey, Pennsylvania
- VOLUME 3 . . . Ohio, Michigan
- VOLUME 4 . . . Illinois, Indiana, Kentucky, Wisconsin
- VOLUME 5 . . . Iowa, Kansas, Minnesota, Missouri, Nebraska, North Dakota, South Dakota
- VOLUME 6 . . . District of Columbia, Florida, Georgia, North Carolina, South Carolina, Virginia, West Virginia
- VOLUME 7 . . . Alabama, Arkansas, Louisiana, Mississippi, Oklahoma, Tennessee, Texas
- VOLUME 8 . . . Arizona, Colorado, Idaho, Montana, New Mexico, Nevada, Utah, Wyoming
- VOLUME 9 . . . California, Oregon, Washington

Send Money Order or Check to:  
POLICE CALL MAGAZINE  
LEBANON, NEW JERSEY 08833

# an extraordinary combination of digitally synthesized receivers...

each with built-in capacity to satisfy  
a broad spectrum of singular applications.



ITT Mackay Marine 3020A and 3021A Radio Receivers feature solid state construction, dual conversion and super-heterodyne design providing continuous frequency coverage from 15kHz to 29.9999MHz. Frequency selection is accomplished by step tuning, while the 3021A Receiver uses sweep tuning. These receivers meet strict requirements of British MPT, German FTZ, Norwegian NTA, Dutch and Spanish PTT and Canadian DOC, and can be used wherever maximum reliability and ease of maintenance are required.

Write or call Ed Engebretson, General Sales Manager (K4IQD), today for complete information on these two quality, high performance receivers.

ITT Mackay Marine, 2912 Wake Forest Road, Raleigh, North Carolina 27611. Telephone: (919) 828-4441.

ITT Mackay Marine  
Mr. Ed Engebretson, General Sales Manager  
2912 Wake Forest Road  
Raleigh, North Carolina 27611

Please send complete FREE information on the exciting new:

- ☐ 3020A Step Tuning Receiver
- ☐ 3021A Sweep Tuning Receiver

NAME \_\_\_\_\_ TITLE \_\_\_\_\_

COMPANY \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

COUNTRY \_\_\_\_\_

Federal Supply Schedule Group 58 Part VII,  
Contract GS-OOS-24016

**ITT** Mackay Marine

# CRYSTALS



**\$3.95 ea.**

plus postage

Fla. residents 4% Sales Tax



2 Meter Amateur Crystals in the 144-148 MHz Band. For All SAVOY part numbers. Write for **FREE EQUIPMENT and PART NUMBER LIST.**

Most Amateur equipments can use SAVOY standard part number at the **LOW — \$3.95 price.**

If Standard Part numbers do not fit your equipment, send us crystal specifications you desire. Advise frequencies & quantities required. We will quote price & delivery.

Postage: (Continental U.S.A.)

PP or 1st Cl. & handling

Airmail & handling

add 10¢ per crystal

add 15¢ per crystal

Prices subject to change without notice

## Savoy Electronics, Inc.

P. O. Box 5727 — Ft. Lauderdale, Florida 33310

Tel: 305-563-1333

If you're a HAM and live or travel in New England, you'll eventually discover us. Why wait? Come in now and let us assist you in your equipment selection.

### NEW ENGLAND'S HAM HDQTRS.

Sells & Services:

ATLAS  
BOMAR CRYSTALS  
CUSHCRAFT  
DUPLEXER KITS  
EMERGENCY BEACON  
ITC

NEWTRONICS  
REGENCY  
STANDARD  
TEN-TEC  
VHF ENG.  
MANY OTHERS


Our large inventory also includes kits, amateur radio publications and the largest selection of used equipment in the Boston area.

Our business is devoted **entirely** to Amateur Radio!

## TUFTS RADIO ELECTRONICS

386 MAIN STREET  
MEDFORD, MASS. 02155

## LEARN RADIO CODE

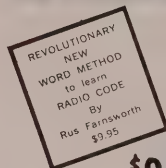

**\$9.95**

Album contains three 12" LP's 2½ hr. Instruction.

### THE EASY WAY!

- No Books To Read
- No Visual Gimmicks To Distract You
- Just Listen And Learn

Based on modern psychological techniques—This course will take you beyond 13 w.p.m. in **LESS THAN HALF THE TIME!** Available in Cassette also for only \$10.95.

## EPSILON [E] RECORDS

508 East Washington St., Arcola, Illinois 61910

## ALUMINUM TOWERS

- ★ TELESCOPING
- ★ WALL MOUNTED
- ★ GUYED
- ★ FREE STANDING

EXCELLENT FOR:

**HAM COMMUNICATIONS**

QUALITY MADE • LOW PRICED

ALUMA TOWER DIVISION

**FRED FRANK, INC.**

BOX 2806HR VERO BEACH, FLA. 32960

PHONE (305) 567-3415

SOME TERRITORIES AVAILABLE



# KLM ANTENNAS . . .

They're heard when others aren't

Some well known band openers are:

- KLM's 20 METER 5 ELEMENT "BIG STICK"
- KLM's 6 METER 8 & 11 ELEMENT
- KLM's 2 METER 12, 14 & 16 ELEMENT
- KLM's 220 MHz 14 ELEMENT


## AND NOW

Winner in the 1975 West Coast VHF-UHF Antenna Measuring Contest . . .

## KLM'S NEW 432 — 16 Element Long Boom (12')

Specifically Optimized for 432 MHz (430-440)

(8 will give you Eme capability)

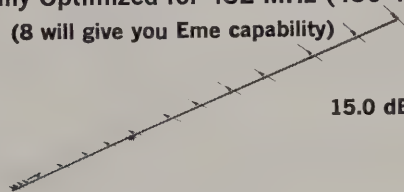

15.0 dB over dipole

Also . . . Brand New for the 420-450 MHz Band

### 4 NEW AMPLIFIERS

- PA 10-35C 10 WATTS INPUT 35 WATTS OUT
- PA 2-40C 2 WATTS INPUT 35 WATTS OUT
- PA 10-70C 10 WATTS INPUT 70 WATTS OUT
- PA 2-70C 2 WATTS INPUT 70 WATTS OUT

And . . . Don't forget our NEW ECHO II

2 METER SSB/CW TRANSCEIVER & LINEAR AMPS.

NEW ECHO II OPTIONS AVAILABLE:

|                                    |         |
|------------------------------------|---------|
| PREAMPS ASSEMBLED .....            | \$20.95 |
| PREAMPS INSTALLED IN ECHO II ..... | \$25.95 |
| USB/LSB ASSEMBLED .....            | \$22.95 |
| USB/LSB INSTALLED IN ECHO II ..... | \$27.95 |



See Your Local KLM Dealer  
For The New Spring '75 Catalog  
Or Write

## KLM ELECTRONICS

1600 DECKER AVE.  
SAN MARTIN, CA. 95046  
408-683-4240  
408-226-1780

# OPTOELECTRONICS, INC.

BOX 219, HOLLYWOOD, FLA. 33022  
PHONE (305) 921-2056



## — DIGITAL CLOCK & CLOCK-CALENDAR-ALARM KITS —

- 6 Digits Hrs-Min-Sec • Drilled Fiberglass PC Boards • 50 or 60 Hz. Op.
- Choice of Six Displays • All Kits Complete Less Case • Guaranteed Components

| Clock Kits     | Clock-Calendar-Alarm Kits | LED Display Options                |
|----------------|---------------------------|------------------------------------|
| 5314-A \$18.50 | 7001-A \$32.95            | RED .3" (6)SLA-1                   |
| 5314-AR 19.95  | 7001-AR 33.95             | RED .3" (6)MAN-7                   |
| 5314-AY 20.95  | 7001-AY 34.95             | YELLOW .3" (6)MAN-8                |
| 5314-AG 20.95  | 7001-AG 34.95             | GREEN .3" (6)MAN-5                 |
| 5314-B 22.95   | 7001-B 36.95              | RED .4" (6)MAN-64AL                |
| 5314-C 24.95   | 7001-C 38.95              | RED .6" & .3" (4)DL-747 & (2)MAN-7 |

### CLOCK-CALENDAR-ALARM KITS (IN ADDITION TO ABOVE) FEATURE:

- 28-30-31 Day Calendar • Time Base Oscillator for AC Failure Battery Back-Up
- Display Alternates Time & Date • AM/PM Indicator • 24 Hr. Alarm & 10 Min. Snooze

This Kit Uses The Fantastic CT-7001 Chip For The Person Wanting Everything In A Clock Kit. Instructions Include Info To Customize Circuit With Options Such As Aux. Timer, Alarm On IND, etc.

### — TERMS —

Kit orders and orders under \$15 please add \$1.00 per order. We pay all other shipping. Fla. res. add 4% tax. COD & credit card orders accepted by phone day or eve.

## CABINET

3" HIGH  
6 1/4" WIDE  
5 1/2" DEEP



GREAT FOR ANY OF THE ABOVE KITS

\$7.95

WHITE VINYL CASE  
Specify RED or GRAY  
PLEXIGLAS CHASSIS

\$6.50 WITH ANY CLOCK KIT

Chassis Serves As Base To Increase Contrast of Digital Displays. Use Gray With Any Color — Red With Red Displays Only (Red LED's with Red Chassis Brightest)

## MICROPROCESSOR

8 BIT  
CPU

8008

\$25.95

2/\$50.00

2102

1K RAM

\$3.95

10/\$37.

PLEXIGLAS FOR READOUT BEZELS 3" x 6" x 1/8" GRAY OR RED 75¢ ea. 2/\$1.25 Approx. Size



## JUMBO LED's Red-Green-Yellow

ANY MIX 6/\$1.00 100/\$14.00  
LED PANEL MOUNTS 6/45¢ 100/\$ 6.50

Bi-Polar LED's Lights Red One Polarity Green Rev. \$1.25

## 25 AMP FULL WAVE BRIDGE 100 PIV



\$1.95 ea.

3/\$5.00

### — DIODE PACKS —

IN4001 50/\$2.50  
IN4007 50/\$7.00  
IN4148 50/\$3.00

### — IC SPECIALS —

1 ea. 5 for  
CT-7001 Clock-Cal. \$5.95 \$27.00  
MM-5314 Clock 3.95 18.00  
TCA430 Tone Gen. 2.95 13.00  
555 Timer .75 3.00  
4250 P. OP Amp 1.25 5.00

— REGULATORS —  
723 TO-100 ±40V .75 3.00  
723 M-DIP ±40V .75 3.00  
309 TO-3 5V 1.50 6.50  
340K-12 TO-3 12V 1.95 8.50


## SUPER BRIGHT 7-SEG LED



MAN-64AL  
15MA/SEG  
COMMON ANODE  
14 PIN DIP  
.4" CHAR. HT.

\$1.95

10/\$18

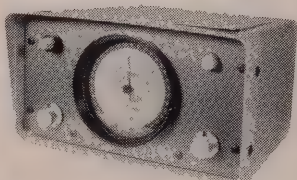

OLD OLD OLD  
RELIABLE RELIABLE  
\$495.00 RX 1 ROTATOR \$495.00

10 YEARS OF PROVEN SERVICE. THE HEAVY DUTY ROTATOR THAT WILL TURN ANY BEAM ARRAY YOU WANT TO INSTALL. CONTROL BOX TO MATCH S LINE. 115VAC SELSYN IND. 380 DEGREES ROTATION. LIMIT SWITCH UNIT IS 9 1/2" DIA. 28" IN HEIGHT.


Mastercharge &  
BankAmericard accepted.



Designed Built Backed  
by ANTENNA MART  
Box 7, Rippey, Iowa 50235
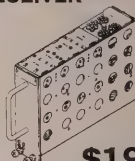
## ARR-52 SOLID STATE VHF RECEIVER

Easily converted to 2-meter FM. Now set for 163-173 MHz, 16 channels. \$19.95 postpaid continental US. Includes schematic diagram and conversion details. As described in the Surplus Sidights Column, (Pg. 58 Oct. CQ).



\$19.95

OVER 300 SOLD POSTPAID  
BankAmericard & COD Welcome

## Electronic Equipment Bank, Inc.

516 Mill Street, N.E. Vienna, Virginia 22180  
(703) 938-3350

## DUPLER KITS

PROVEN DESIGN. HUNDREDS SOLD IN US, CANADA, EUROPE. CONSTRUCTION WELDED ALUMINUM IRIDITE & SILVER PLATED. SEE JAN. 74 QST RECENT EQUIPMENT. ALL PARTS PROFESSIONAL QUALITY. EVERYTHING SUPPLIED. NO SPECIAL TOOLS. RECEIVER & TRANSMITTER CAN BE USED FOR TUNE UP.

MOD. 62-1 6 CAVITY 135-165 MHz POWER 250W  
ISOLATION GREATER THAN 100dB 600 kHz.  
INSERTION LOSS .9 dB MIN. TEMP STABLE  
OVER WIDE RANGE PRICE \$349.00

MOD. 42-1 4 CAVITY SAME AS 6 CAVITY EXCEPT  
ISOLATION GREATER THAN 80 dB 600 kHz  
INSERTION LOSS .6 dB MAX. PRICE \$249.00

### NORTH SHORE RF TECHNOLOGY


9 SOUTH ST SALEM MASS 01970  
TEL. (617) 745-4177

# SAVE \$\$\$ AT THE FM SUPERMARKET OF VALUES!!

YOU CAN INDEED SAVE \$\$\$.. ALL OF THE ITEMS WE ARE OFFERING THIS MONTH ARE AT THE LOWEST PRICES WE'VE SEEN ANYWHERE. DON'T DELAY . . . AT SUCH PRICES WE DON'T EXPECT STOCK TO LAST TOO LONG . . . ORDER NOW.
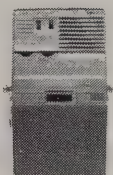
## GENERAL ELECTRIC VOICE COMMANDER III

SOLID STATE XCVR  
IDEAL FOR STRIPPING  
CONVERTIBLE TO 2 MTR  
1 WATT TRANSMIT  
NICADS INCLUDED  
UNCHECKED BUT COMPLETE



**ONLY  
\$29.95**

+ shipping

### Options Available

|                    |        |
|--------------------|--------|
| Schematics .....   | \$3.00 |
| Extra Nicad .....  | \$7.50 |
| External Mic. .... | \$7.50 |

## DON'T MISS OUT ON 220 MHz

220'S REALLY GROWING. IN AREAS LIKE CHICAGO 223.5 IS A BUSY SIMPLEX CHANNEL. HERE'S YOUR CHANCE TO GET IN ON THE FUN WITH LITTLE INVESTMENT AND YET WITH A QUALITY RADIO. CHECK THESE FEATURES:



## COBRA VHF 200

All solid state fm XCVR  
10 watts output  
12 channels (223.5 supplied)  
Individual trimmers all xtals  
.5uv receiver or less  
Uses same xtals as Midland

Special group price available.  
Call for details.

**ONLY \$189.95** + shipping

## PROTECT YOUR MOBILE INVESTMENT

SELF CONTAINED, COMPACT AUTO THEFT ALARM AT UNBELIEVABLY LOW PRICE. PROTECT YOUR VALUABLE MOBILE. NO SWITCHES TO INSTALL FOR INTERIOR PROTECTION. ANY INTERIOR LIGHT GOING ON TRIGGERS THE ALARM. NOT AFFECTED BY AUTO CLOCKS. CHECK THESE FEATURES:



**ONLY  
\$29.95**  
+ shipping

4 WIRE HOOK UP  
BUILT IN YELP SIREN (110 DB)  
BUILT IN SENSING CIRCUIT  
USUAL INSTALL TIME 1 HOUR OR LESS  
PRICED LESS THAN MOST SIRENS ONLY.

**TERMS OF SALE:** Sales to licensed Radio Amateurs for use on Amateur freqs only. All prices FOB Oak Park, IL. Check with order, COD or you can charge to your BankAmericard or Master Charge.

**STORE HOURS:** Mon.-Thurs. 9:30-6:00, Fri. 9:30-8:00, Sat. 9:30-3:00. Closed Sun. & Holidays  
INQUIRIES WITHOUT ZIP CODE OR CALL . . . NO ANSWER

**WANTED:** Good used FM & test equipment. No quantity too large or small. Finders fees too.



## SPECTRONICS INC.

1009 GARFIELD STREET  
OAK PARK, ILL. 60304  
(312) 848-6778





## "MINI-PORTABLE" DIPOLE KIT



Reg. ~~\$49.95~~

**\$29.95\***


Go Mobile!  
"RESONATORS"  
40 or 20 Meters

**\$9.95 ea.**  
Prepaid  
in Cont'l USA

- Mounts vertical or horizontal - Electrical 1/2 wave length
- For mast, windowsill, boat, mobile home, or auto
- Quick erect - Up to 500 watt PEP. Hi-Q helical resonators
- Tuneable tip rod - 15' approximate length - 40 or 20 meter band models

\* add \$5.00 for prepaid shipping

# RADIO KING

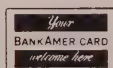

25326 CRENSHAW BLVD., TORRANCE, CALIF. 90505

PHONE: (213) 534-4456



NEW !

### 500 MHZ PRESCALER MODULE

Only 35 mv. required at 500 Mhz.  
20 mv. at 150 Mhz.

Miniature size: 1.5 x 1.5 x .4 inches  
Fits right into existing equipment

F/10 output, TTL compatible

Overload Protected up to 2 volts input

Requires 12 to 15 VDC at 100 ma. max.

Measures a 1 watt transmitter from 6 feet  
using a 1/4 wave antenna at 500 Mhz.

PS-M Prescaler Module wired & tested \$ 99.00

Still available: Prescalers with 110 VAC power supplies, 150 mv. sensitivity, F/10 and F/100 outputs, 3 x 4 x 1.5 inches  
PS-K kit...\$89.00 PS-A...\$109.00

All orders please add \$.85 for shipping  
Calif. residents add 6% sales tax

**LEVY ASSOCIATES**

P.O. Box 961 R  
Temple City, CA 91780

## CATALOG

### GOVERNMENT SURPLUS ELECTRONIC EQUIPMENT


# For 1975

**FREE** UPON REQUEST! Write for  
Copy of Catalog WS-75 Now!

Address: Attention Dept. HR

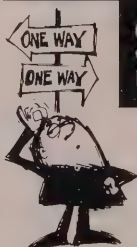**FAIR RADIO SALES**

1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802



**Confused? There is only one  
way to go for high-quality FM  
kits!**

VHF & UHF FM TRANSMITTERS  
VHF & UHF FM RECEIVERS  
VHF & UHF CONVERTERS  
VHF & UHF PREAMPLIFIERS  
SCAN ADAPTERS  
RCVR ALIGNMENT OSCILLATORS

Designs featured in Ham Radio Articles

— Send SASE for catalog —

**HAMTRONICS, INC.**

182 BELMONT RD., ROCHESTER, N. Y. 14612

# THIS PAGE IS YOUR ORDER BLANK!

## ORDER NOW AND SAVE!

### Specials at Unbeatable Prices



GENAVE, 4141 Kingman Dr., Indianapolis, IN 46226 (317+546-1111)

HEY, GENAVE! Thanks for the nice prices! Please send me:



#### GTX-200-T Operate Auto-Patch

2-meter FM, 100 channels. 30 watts  
(incl. 146.94 MHz)


Special Price **\$259<sup>95</sup>**



#### GTX-200

2-meter FM, 100 channels. 30 watts  
was \$299.95 (Incl. 146.94 MHz)

NOW **\$219<sup>95</sup>**

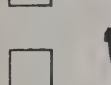

#### GTX-100

1 1/4-meter FM, 100 channels. 12 watts  
was \$309.95 (Incl. 223.5 MHz)

VERY SPECIAL **\$199<sup>95</sup>**



#### GTX-10

2-meter FM,  
10 channels,  
10 watts


~~\$169<sup>95</sup>~~  
WOW! **\$139<sup>95</sup>**



#### GTX-2

2-meter FM, 10 channels. 30 watts  
was \$299.95 (Incl. 146.94 MHz)

NOW **\$199<sup>95</sup>**

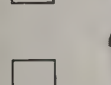

#### GTX-600

6-meter FM, 100 channels. 35 watts  
was \$309.95 (Incl. 52.525 MHz)

SPECIAL NOW **\$199<sup>95</sup>**

- |   |            |          |
|---|------------|----------|
| <input type="checkbox"/> PSI-11 Battery Pack (with charger)         | @ \$109.95 | \$ _____ |
| <input type="checkbox"/> ARX-2 2-M Base Antenna                     | @ \$29.95  | \$ _____ |
| <input type="checkbox"/> Lambda/4 2-M Trunk Antenna                 | @ \$29.95  | \$ _____ |
| <input type="checkbox"/> TE-I Tone Encoder Pad                      | @ \$59.95  | \$ _____ |
| <input type="checkbox"/> TE-II Tone Encoder Pad                     | @ \$49.95  | \$ _____ |
| <input type="checkbox"/> PSI-9 Port. Power Package (less batteries) | @ \$29.95  | \$ _____ |
| <input type="checkbox"/> PS-1 AC Power Supply                       | @ \$69.95  | \$ _____ |

and the following standard crystals @ \$4.50 each: \_\_\_\_\_ \$ \_\_\_\_\_

Non-standard crystals @ \$6.50 each: \_\_\_\_\_ \$ \_\_\_\_\_

(allow 8 weeks delivery.)

For factory crystal installation add \$8.50 per transceiver.

IN residents add 4% sales tax:

CA residents add 6% sales tax:

All orders shipped post-paid within continental U.S.

NAME \_\_\_\_\_ PHONE \_\_\_\_\_

ADDRESS \_\_\_\_\_ CITY \_\_\_\_\_ STATE & ZIP \_\_\_\_\_

Payment by: ☐ Certified Check/Money Order ☐ Personal Check ☐ C.O.D. Include 20% Down.

Note: Orders accompanied by personal checks will require about two weeks to process.

☐ 20% Down Payment Enclosed. Charge Balance To:

☐ BankAmericard # \_\_\_\_\_ Expires \_\_\_\_\_

☐ Master Charge # \_\_\_\_\_ Expires \_\_\_\_\_ Interbank # \_\_\_\_\_

Prices and specifications subject to change without notice.

# NEW ENGLAND'S LARGEST FLEA MARKET!

— AT THE —

## NASHOBA VALLEY HAMFEST

SATURDAY, SEPT. 27, 1975 — WESTFORD, MASS. — 4-H FAIRGROUNDS

### PROGRAM AT FAIRGROUNDS INCLUDES:

9/26 FRI. NITE 6:00 P.M.-?

BARBECUE & CAMPING

9/27 SAT. 8:00 A.M.-5:00 P.M.

FLEA MARKET

EQUIP. EXHIBITS

TECH. TALKS

FOX HUNT (2 Meter)

PRIZES (All Profits Converted Into Prizes)

FOOD & REFRESHMENTS




10% BEER COURTESY OF  
RMS & HAM RADIO

### TALK-INS:

146.04/.64

146.52, 146.94, 449.05

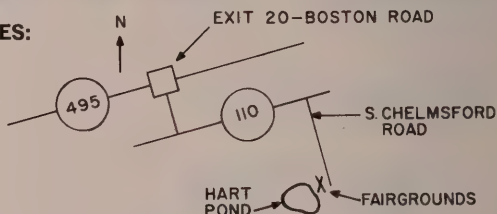

NOTE: LOOK FOR HAMFEST  
SIGNS ON RT. #110.

|                                  |        |
|----------------------------------|--------|
| FLEA MARKET SPACE .....          | \$2.00 |
| GENERAL ADMISSION .....          | \$1.00 |
| YL/XYL & Children under 12 ..... | FREE   |

DEALERS WRITE FOR DETAILS TO:

NASHOBA VALLEY HAMFEST

675A GREAT RD.

LITTLETON, MASS. 01460

617-486-4973

## RMS CORPORATION

THE ELECTRONIC STORE

675A GREAT ROAD (ROUTE 119)

LITTLETON, MASS.

(617) 486-4973

ICOM

MATRIC-KEYERS

HUSTLER

ANTENNA SPECIALISTS

CONSIGNMENT EQUIP.

LARSEN

KLM

RADIO PUBLICATIONS

LARGE INV. COMPONENTS

USED EQUIP.

I-495 to Rte. 119 Groton Exit 19

2 miles on Right

PLAN NOW! SEE US AT

NASHOBA VALLEY HAMFEST

SEPT. 27, 1975 — AD THIS PAGE

Is your old gear  
collecting dust?

**BUYERS & SELLERS**  
RADIO BROKERAGE

Buyers buy free; sellers pay 10% if a  
sale is made (as a result of our service).

617-536-8777

W F Sun 12pm-6pm EST  
T Th Sat 6pm-12am EST

**BUYERS & SELLERS**

P.O. Box 73  
Boston, Mass 02215

See us at Nashoba Valley Hamfest



Radio Amateurs  
Reference Library  
of Maps and Atlas

**WORLD PREFIX MAP** — Full color, 40" x 28", shows  
prefixes on each country . . . DX zones, time zones,  
cities, cross referenced tables ..... **\$1.25**

**RADIO AMATEURS GREAT CIRCLE CHART OF THE  
WORLD** — from the center of the United States! Full  
color, 30" x 25", listing Great Circle bearings in de-  
grees for six major U.S. cities: Boston, Washington,  
D. C., Miami, Seattle, San Francisco & Los Angeles.  
..... **\$1.25**

**RADIO AMATEURS MAP OF NORTH AMERICA!** Full  
color, 30" x 25" — includes Central America and the  
Caribbean to the equator, showing call areas, zone  
boundaries, prefixes and time zones, FCC frequency  
chart, plus useful information on each of the 50  
United States and other Countries. .... **\$1.25**

**WORLD ATLAS** — Only atlas compiled for radio ama-  
teurs. Packed with world-wide information — includes  
11 maps, in 4 colors with zone boundaries and coun-  
try prefixes on each map. Also includes a polar pro-  
jection map of the world plus a map of the Antarctica  
— a complete set of maps of the world. 20 pages.  
size 8 3/4" x 12" ..... **\$2.50**

Complete reference library of maps — set of 4 as listed  
above ..... **\$3.75**

See your favorite dealer or order direct.

Mail orders please include 75¢ per order for postage and handling.

**WRITE FOR  
FREE  
BROCHURE!**

RADIO AMATEUR




**callbook INC.**

Dept. E 925 Sherwood Drive  
Lake Bluff, Ill. 60044


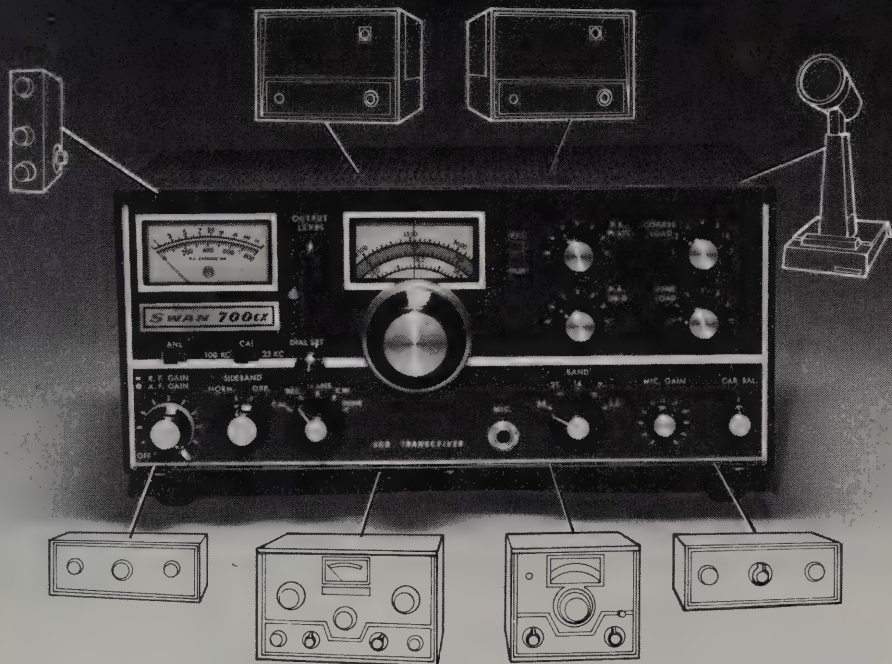
# When you start your top-performance ham station, start with our 700CX.



## It's the way to grow.

Everybody wants the ultimate ham station, but the only way most of us are going to get it is to start now and grow into it.

And the best way to start is with our 700CX.

Then you'll have an excellent transceiver with 700 solid watts P.E.P. input of SSB power at the lowest cost per watt—about a buck—of any comparable equipment.

And when you're ready to add capability and features, plug in or hook up Swan accessory equipment for easy expandability.

For instance, just plug in our 510-X crystal oscillator when you want extra frequency coverage. If your kind of traffic calls for separate transmit and receive frequencies, our 508 VFO is made for your station. Want VOX? Plug in the Swan VX-2 and start talking. Or hook up our FP-1 telephone patch in minutes.

And when you're ready for that big jump to all-the-law-allows, our 2000-watt P.E.P. input Mark II linear amp is waiting in the wings.

Add our complete selection of power supplies, microphones and other options and you've got everything you need for a full-house rig in matching specs and matching decor.

So your ham station will look and per-

form like it belongs together.

With the 700CX you'll never be troubled by things like cross-modulation and front-end overload because the design is excellent. All bands from 10 to 80 meters with selectable upper or lower sideband, AM, or CW with sidetone.

Get started on your dream rig today. See the 700CX at your nearest Swan dealer or order direct from our factory.

**700CX Champion Transceiver . . . . \$649.95**

**117-XC 110V AC Power Supply . . . \$159.95**  
(includes Speaker and Cabinet)

**117-X 110V AC Power Supply . . . \$114.95**  
(less Speaker and Cabinet)

**510-X Crystal Oscillator . . . . . \$ 67.95**

**508 External VFO . . . . . \$269.95**

**VX-2 Plug-In VOX . . . . . \$ 44.95**

**FP-1 Telephone Patch . . . . . \$ 64.95**

**Mark II Linear Amplifier . . . . . \$849.95**  
(complete with 110/220 VAC power supply and tubes)


Dealers throughout the world  
or order direct from

**SWAN<sup>®</sup>**  
**ELECTRONICS**  
A subsidiary of Cubic Corporation

Home Office: 305 Airport Road • Oceanside, CA 92054  
Telephone: (714) 757-7525
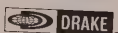
# SEE YOU SEPT. 6th & 7th AT RADIO EXPO 75

WHILE YOU'RE IN THE AREA . . . VISIT THE NATION'S LEADING FM SPECIALISTS AND CHICAGOLAND'S #1 AMATEUR OUTLET. WE'RE EASY TO GET TO. ONLY MINUTES AWAY FROM CHICAGO LOOP. CHOOSE FROM A WIDE SELECTION OF FAMOUS BRANDS.



## SPECIAL EXPO BONUS

. . . DURING SEPTEMBER YOUR EXPO 75 TICKET LETS YOU SAVE ON NEARLY EVERY ITEM IN OUR STORE. HERE ARE JUST A FEW OF THE WAYS TO SAVE:

WITH EXPO 75 TICKET YOU SAVE . . .

**20% . . . OFF** CATALOG PRICE OF ANY USED MOTOROLA TUBE TYPE TRANSCEIVER

**20% . . . OFF** NORMAL PRICE OF USED MOBILE & BASE PARTS

**\$10-25.00 . . . OFF** OUR EVERY DAY LOW PRICES FOR NEW TRANSCEIVERS, TRANSMITTERS, OR RECEIVERS.

**PLUS** SIMILAR SAVINGS ON ANTENNAS, COAX & ACCESSORIES.



## SPECTRONICS INC.

1009 GARFIELD STREET  
OAK PARK, ILL. 60304  
(312) 848-6778

**STORE HOURS:** Mon. thru Thurs. 9:30-6:00  
Friday 9:30-8:00, Sat. til 3:00.  
Closed Sunday and Holidays.



**DON'T MISS THAT  
CW QSO!!!**

**15 WATTS  
FULL  
BREAK-IN**



## CW • TRANSMITTER MODEL 50

- Built-in Antenna Relay
- 160, 80, or 40M Plug-in Coil
- Crystal Control
- Zener Regulated Chirpless Keying
- Clean Output — "T" Network
- Built-in 115 VAC Supply

MODEL 50K - BASIC KIT ..... \$39.95

ADD-ON OPTIONS: SIDETONE (200-21K).....\$ 5.95  
KEYER (200-22K).....\$ 13.95

MODEL 50W - BASIC WIRED ..... \$49.95

MODEL 50WS (WITH SIDETONE) ..... \$59.95

MODEL 50WK (WITH KEYER) ..... \$69.95


MODEL 50WSK (WITH SIDETONE & KEYER) ..... \$79.95

ORDER DIRECT OR WRITE FOR BROCHURE  
AND NAME OF NEAREST DEALER.



PHONE: (814) 432-3647  
BOX 185-A • FRANKLIN, PA. 16323

## BC-348 RECEIVER

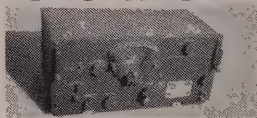


6 BANDS 200-500 KC 1.5-18 MHZ  
CRYSTAL PHASING, ANTENNA ALIGN.  
BEAT OSCILLATOR, AUDIO GAIN CONTROL  
AVC-MVC PHONE - C.W. PHONE - SPEAKER JACKS  
220 V.D.C. 70 M.A. & 24 V.D.C.  
18 x 10 1/2 x 9 1/2, WT. 40 LBS.

USED, CHECKED, WITH DYNAMOTOR  
NO C.O.D.'s PLEASE

**\$49.95**
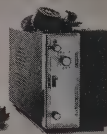
## KOLAR, INC.

4484 E. TENNESSEE ST., TUCSON, AZ. 85714  
TELEPHONE: AREA 602-748-1900



**DELUXE PORTA-PAK**

**\$59.95**

ups prepaid

**REGULAR PORTA-PAK**

**\$39.95**

ups prepaid

## PORTA-PAK

P. O. BOX 67

SOMERS, WISCONSIN 53171




## NEW KITS!

## NEW KITS!

### JAMES ELECTRONICS

P. O. BOX 822 BELMONT, CALIFORNIA 94002  
(415) 592-8097

#### DIGITAL VOLTMETER

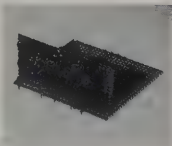


This is a 3 1/2 digit, 0-2 volt Digital Voltmeter, with a .5% full scale accuracy. It is based around the Siliconix LD110, LD111 DVM chip set. The voltmeter uses MAN7 readouts (.3" high) to provide a highly readable display. The unit requires the following supply voltages: 12, -12, 5. The unit comes complete with all components to build the unit pictured at the left, that is a complete DVM less power supply.

**\$39.95 Per Kit**

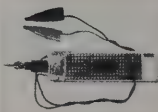
#### LOGIC PROBE

The Logic Probe is a unit which is for the most part indispensable in trouble shooting logic families: TTL, DTL, RTL, CMOS. It derives the power it needs to operate directly off of the circuit under test, drawing a scant 10 mA max. It uses a MAN3 readout to indicate any of the following states by these symbols: (H) - 1 (LOW) - 0 (PULSE) - P. The Probe can detect high frequency pulses to 45 MHz. It can't be used at MOS levels or circuit damage will result.



**\$9.95 Per Kit**

#### DIGITAL COUNTER

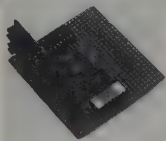


This is a 4 digit counter unit which will count up to 9999 and then provide an overflow pulse. It is based around the Mostek MK5007 digital counter chip. The unit performs the following functions: Count input, RESET, Latch, Overflow. The counter operates up to 250 kHz. The counter is an ideal unit to be used as a frequency counter, where the only extra components needed would be a timebase, divider chain and gate. The unit requires 5V, and -12V. The unit comes complete as shown on the left less power supply.

**\$29.95 Per Kit**

## ONE KIBOYTE

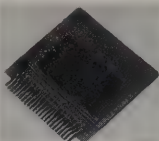
## RANDOM ACCESS MEMORY

This memory card is for the most part a universal unit that can be used in almost any microcomputer from a HOMEBREW to an ALTAIR 8800. It uses an array of 2102 1k x 1 static random access memories to produce a 1024 x 8 memory compatible with most standard microcomputer systems. We provide everything from the super low noise vector logic card, to fine quality low profile sockets, to the eight 2102's. We even include timing diagrams and tantalum bypass capacitor.



**\$69.95 Per Kit**

#### 5 VOLT 1 AMP T<sup>2</sup>L SUPPLY

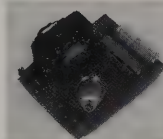


5 VOLT 1 AMP  
T<sup>2</sup>L SUPPLY

This is a standard TTL power supply using the well known LM309K regulator IC to provide a solid 1 AMP of current at 5 volts. We try to make things easy for you by providing everything you need in one package, including the hardware for only:

**\$9.95 Per Kit**
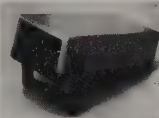
#### PLASTIC INSTRUMENT CASE

These cases are fine quality units made by a German manufacturing firm which fit to the dimensions of our DVM and COUNTER kit with room enough left for power supply or batteries. Excellent for many other projects as well. Dimensions 2" x 3-1/8" x 5-7/8".



**\$5.95 Per Case**

Satisfaction Guaranteed. \$5.00 Min. Order. U.S. Funds.  
Add \$1.25 for Postage — Write for FREE 1975 Catalog  
California Residents — Add 6% Sales Tax


# JAMES

P.O. BOX 822, BELMONT, CA. 94002  
PHONE ORDERS — (415) 592-8097

## CASHARROONIE

Money! You can get top dollars now for U.S. surplus electronics, particularly Collins. Write or call now for your bigger than ever quote. Space Electronics Corp., 76 Brookside Ave., Upper Saddle River, N.J. 07458 (201) 327-7640.

### ELPROCON 1 WATT 2 METER TRANSMITTER

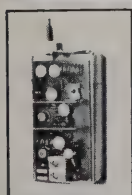

- TWO CHANNEL CAPABILITY
- FREQUENCY RANGE 144-148 MHz
- POWER OUTPUT 1 WATT INTO 50 OHM LOAD
- SUPPLY VOLTAGE 12 VDC
- MULTIPLICATION FACTOR 8X
- NARROW BAND FM ± 5 KHZ
- RUGGED BALANCED EMITTER OUTPUT TRANSISTOR
- SIZE 3 3/4" X 1 7/8"
- TESTED & FULLY ASSEMBLED (Less Xtals)
- \$29.50 postpaid in U.S.

**ELPROCON**  
DEPT. DS - 1907 W. CAMPBELL  
PHOENIX, ARIZONA 85015

## ATTENTION HAMS!

Would you like to be able to put your ideas to use instead of just thinking about them? Contract this service to start your ideas to reality. WE CAN DO:

- Analyze your circuit with a computer to see how it will work under different conditions before it is constructed.
- Design completely from your ideas any piece of equipment you could dream up.
- Construct any piece of equipment you desire.
- Supply parts to builders of their own equipment.

You will own ALL rights to any design work contracted for and could market your own ideas. Even make money.


I will be pleased to hear from you.

DENNIS J. REGAN, K6RGS

RADIO AMATEUR ENGINEERING SERVICE  
5105 Brockton Ct. Bakersfield, CA 93309  
Telex: NR 682-455 Phone: 805/831 2222



## AMPLIFIERS with VERSATILITY

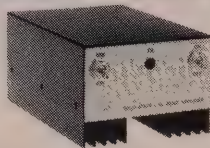

- Selectable biasing for true linear use.
- No tuning across entire Amateur band.
- Fully VSWR and reverse voltage protected.
- Switchable from Linear SSB to Class C.

Announcing the newest additions to the growing line from SCS, leader in linearized Power Amplifiers for the discriminating amateur.

### 2 METER

|           |          |                     |
|-----------|----------|---------------------|
| 2M10-140L | \$199.95 | 10W IN, 140W OUT    |
| 2M30-140L | \$179.95 | 25-30W IN, 140W OUT |
| 2M10- 70L | \$139.95 | 10W IN, 70W OUT     |

### 220 MHZ

|             |          |                     |
|-------------|----------|---------------------|
| 1.3M10-120L | \$219.95 | 10W IN, 120W OUT    |
| 1.3M30-120L | \$199.95 | 25-30W IN, 120W OUT |
| 1.3M10- 60L | \$159.95 | 10W IN, 60W OUT     |

Write now or contact your nearest dealer!

### SPECIALTY COMMUNICATIONS SYSTEMS

4519 Narragansett Avenue, San Diego, CA 92107

Louis N. Anciaux, WB6NMT

(Dealer inquiries invited.)

714-222-8381

### MEMORY

82S129

- 1024 bit ROM (256x4 PROM)
- access time 50 NS
- Power dissipation .5 MW/BIT
- Tri-state output
- Field programmable
- 16 pin DIP

Each \$5.00 8 for \$34.95

2N3565 NPN TO-106  
30v Beta 150 min.  
500 mw.

Each \$.15

10 pak \$1.00



### DIP RC NETWORKS

14 and 16 pin IC packages containing precision resistors and capacitors.  
NO SCHEMATICS AVAILABLE

Sample indicates most contain 10 to 15R and 1 or 2C.

Assortment of 15 \$1.00



### VOLTAGE REGULATORS TO-3

1 AMP POSITIVE

1 AMP NEGATIVE

|         |     | EACH   | 10 PAK  |        |      | EACH   | 10 PAK  |
|---------|-----|--------|---------|--------|------|--------|---------|
| LM 309K | 5V  | \$1.25 | \$10.00 | LM 320 | 5V   | \$1.95 | \$17.50 |
| 7806    | 6V  | 1.50   | 13.00   | LM 320 | 5.2V | 1.95   | 17.50   |
| 7812    | 12V | 1.95   | 17.50   | LM 320 | 12V  | 1.95   | 17.50   |
| 7815    | 15V | 1.95   | 17.50   | LM 320 | 15V  | 1.95   | 17.50   |
| 7824    | 24V | 2.25   | 20.00   |        |      |        |         |

### FALL SALE!

With a \$25.00 prepaid order we will include a CT5001 4 function, 12 digit calculator IC with data. Offer expires October 31, 1975

All merchandise is new unused surplus and is sold on a money back guarantee. Five dollar minimum order. Free first-class postage on all orders. California residents please add sales tax.

**SEND FOR  
FREE FLYER**


Write to: **VALU-PACK**

**box AF Carmichael, Ca. 95608**
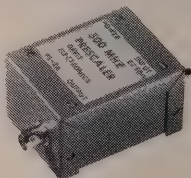
## 500 MHZ PRESCALER

Extend the range of your present frequency counter to measure through 500 MHZ (typically 525 MHZ). Works into any standard counter rated for 5 MHZ or higher. A must for work on 2 meters, 432 MHZ and commercial high bands.

- 150 mv sensitivity
- Input overload protected
- 50 ohm Input Z
- Small size  
2 3/4 x 2 1/8 x 1 5/8"
- BNC connectors
- Divide by 100 or 10
- Light blue case
- Model Ps 2A \$99.95



Prescaler is shipped assembled, tested and ready to operate. Complete with line cord power supply.

### DAVIS ELECTRONICS

636 Sheridan Dr., Tonawanda, N.Y. 14150 716/874-5848-9

### TIRED OF IGNITION NOISE?

End your problems now with our SHIELDED IGNITION SYSTEMS. Easily installed kit provides all items necessary to reduce ignition noise to less than 1 "S" Unit. Kits for 1965-1975 U.S. autos except 1975 GM.

**\$30.95** — Kit for 6 cyl. U.S. Auto

**\$35.95** — Kit for 8 cyl. U.S. Auto


- Add \$4.98 for Electronic Ignition Systems.
- Mass. residents add applicable Sales Tax —
- Specify Year, Mfg., Engine, Model and 5/8" or 13/16" Hex Size of Spark Plugs —
- Order now or send SASE for details —

### SUMMIT ENTERPRISES

20 Eider Street  
Yarmouth Port, Mass. 02675  
617-398-3837
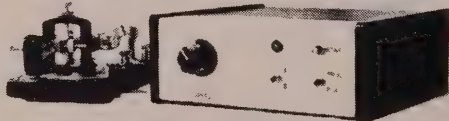
## \* SEPTEMBER SPECIAL — Are you ready for your next contest?

LOW COST PROGRAMMABLE ELECTRONIC KEYS WITH MEMORY.



### NEW LOW PRICE!

Complete Kit for only **\$59.97 ppd.**  
ASSEMBLED unit **\$79.50 ppd.**

This keyer stores one or two code messages for broadcast at any time. **FEATURES:** Dot and Dash Memory, Two Independent 256 Bit RAM Memories, Keys up to —150 Volts, Self Completing Characters, 6 to 60 WPM, Iambic Keying.


Dual lever **PADDLE** supplied for \$20.00 extra This Month Only.

## NEW ENGLAND DIGITAL ELECTRONICS

BOX 684 KENMORE STATION • BOSTON, MASS. 02215

# PHOTO ETCH
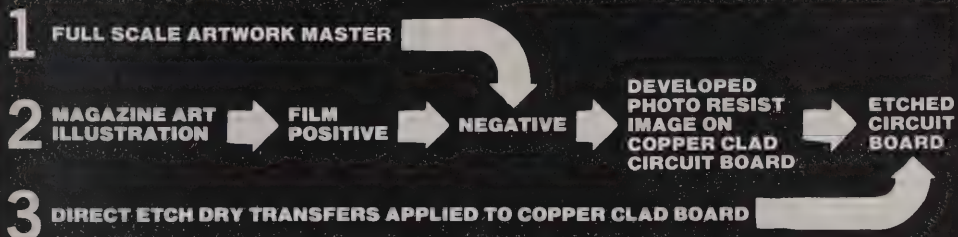
## PRINTED CIRCUIT KIT MAKES PRINTED CIRCUITS THREE WAYS!



**NO** CAMERA  
DARKROOM  
FILM CUTTING  
TRACING

**USES DATAK'S POS-NEG PROCESS**  
*The revolutionary photographic way  
that makes PERFECT printed circuits  
from original art or a printed page.*

KIT CONTAINS: 5" x 6" steel printing frame, 4 sheets 5" x 6" photocopy film, yellow filter, chemicals for 1 pint film developer and 1 pint film fixer, 5" x 6" copper clad board, 3" x 4 1/2" copper clad board, spray can of photo etch resist, 1 pint resist developer, 2 sheets 8 1/2" x 11" layout film, 1 roll 1/16" printed circuit tape, 1 roll 1/32" printed circuit tape, 8 sheets dry transfer direct etch PC patterns including pads, transistors, round can and flat pack ICs, DIP ICs, edge card connectors, lines, circles, jogs, etc., 1/4 lb anhydrous ferric chloride to make 1 pint etchant, instructions.

**ER-4 COMPLETE PHOTO ETCH SET . . . . . postpaid \$24.95**  
**AT YOUR DISTRIBUTOR OR DIRECT (N. J. residents add sales tax)**

**The DATAK corp. • 65 71st St. • Guttenberg, N. J. 07093**



### 10 CHANNEL SCANNER

For All Regency HR series 2, 2A, & 2B  
MT-15, MT-25, & AQUAFONE Transceiver

#### FEATURES:

- Selectable Priority Channel (Selected By Channel Selector Switch)
- 10 Second Delay Before Scan Resumes After Transmit
- 2 Second Delay Before Scan Resumes After Signal Loss
- Plugs Into Existing Crystal Sockets. Simple 5 Wire Hook-Up Without Major Modification To Radio
- Simple Modification For Selective Channel Bypass
- Optional Digital Channel Display

SCANN 10B 10 Channel Scanner \$52.50  
(Wired Only)

D10B Digital Channel Display \$21.75  
(Wired Only)

NET PRICE FOR BOTH \$74.25

HR-2B With Both Installed \$299.99

6T-HR2-3 Crystal Deck (6 more FQ's in HR2, HR-2A) Kit \$11.50, Wired \$15.50

HF 144 U MOSFET Preamp Kit \$11.95, Wired \$17.95

**Topeka FM Communications & Electronics**  
125 Jackson  
Topeka, Kansas 66603  
913-233-7580

### UNIVERSAL TOWERS FREE STANDING ALUMINUM TOWER

10' to 100'  
Prices from \$110.00 (30')

**MOST  
POPULAR  
HAM TOWER  
EVER MADE!**

REQUEST  
**NEW CATALOG  
OF  
TOWERS &  
ANTENNAS**



**Midwest Ham Headquarters**

For Over 36 Years

HAMS! Write For Free Catalog and Wholesale Prices!

**ELECTRONIC DISTRIBUTORS, INC.**

1960 Peck Muskegon, MI 49441


Tel: 616-726-3196 TELEX: 22-8411



**ROMS! RAMS!  
MEMORIES!**



# flea market

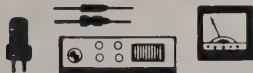

**RATES** Non-commercial ads 10¢ per word; commercial ads 35¢ per word both payable in advance. No cash discounts or agency commissions allowed.

**HAMFESTS** Sponsored by non-profit organizations receive one free Flea Market ad (subject to our editing). Repeat insertions of hamfest ads pay the non-commercial rate.

**COPY** No special layout or arrangements available. Material should be typewritten or clearly printed and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** can not check out each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue.

**DEADLINE** 15th of second preceding month.

**SEND MATERIAL TO:** Flea Market, Ham Radio, Greenville, N. H. 03048.

**YAESU OWNERS** — Present or Prospective — Listen for FT Net: Saturday 1700 GMT, 14.325±. Discuss new equipment, modifications, questions, answers. International Fox-Tango Club. SASE brings complete club information and free sample Newsletter. Milt Lowens, W42AOQ, 3977F Sedgwick Ave., Bronx, N. Y. 10463.

**RADIO MUSEUM NOW OPEN.** Free admission. 25,000 pieces of equipment from 1850 telegraph instruments to amateur and commercial transmitters of the 1920's. Amateur Station W2AN. Write for information. Antique Wireless Association, Main St., Holcomb, N. Y. 14469.

**RTTY — NS-1 PLL TU** (HR 2/75) Undrilled board \$4.75 ppd. Wired/tested \$29.95 ppd. Nat Stinnette Electronics, Tavares, FL 32778.

**FINDLAY HAMFEST** — Sept. 7 — Riverside Park, Findlay, Ohio. For advance drawing tickets write Clark Foltz, W8UN, 122 W. Hobart, Findlay, 45840.

**ENGRAVED RADIO LICENSE.** Exact reproduction in solid brass. Permanent identification. Send good Xerox copy, with \$5.00, to Metal Art Graphics, 1136 Potomac Ave., Hagerstown, Md. 21740.

**SELLING** Collins made R-1150 SSB receiver, 2-30 MHz, accuracy 1 x 10-8 per day, sensitivity 1 uv, \$425. AN/URM-25F AM generator, 10 kHz to 50 MHz, crystal calibrator, precision shielded attenuator, \$160. AN/URM-26B AM generator, 4-405 MHz, piston attenuator, \$225. AN/URM-120 wattmeter, in line, 2 to 1000 MHz, 10W to 1000W, \$125. Manuals included. James Walter, 2697 Nickel, San Pablo, Ca. 94806.

**FIGHT TVI** with the RSO Low Pass Filter. For brochure write: Taylor Communications Manufacturing Company, Box 126, Agincourt, Ontario, Canada. MIS 384.

**\$2.00 BUYS 2" x 8" ENGRAVED ACRYLIC CALL PLATE.** 2 lines add \$.50 Woodgrain or colors below. White letters. Pins \$1.00, 1" x 3", 2 lines. Blue, red, black. Guaranteed. Order, or request brochure. Fast service. Holly, Box 3926-F, Hollywood, Florida 33023.

**DANE COUNTY SWAPFEST.** Dane Co. Expo Center, Madison, Wis. Sept. 28, 8 a.m. Box 3403, Madison, Wisc. 53704 for information.

**SELL:** Spectrum Analyzer, Polarad model TSA, with three plug-in units. Frequency range 10MHz to 22.5 GHz. \$450.00, R. Smith, P. O. Box 528, Moss Beach, Calif. 94038 (near San Francisco) (415) 728-5086.

**RADIO ARCHIVES,** amateur anecdotes solicited for (SASE subscription) monthly PR newsletter. Electronic Avocations, 3207 4th St. N., Minneapolis, Minn. 55412.

**"HOW-TO BUILD DIGITAL EQUIPMENT"** New, fast, inexpensive way. Detailed instructions, plans — \$1.95. Guaranteed. Creative Resources, Box 58872, Houston, Texas 77058.

**50 FREE INTERNATIONAL QSL EXCHANGE COUPONS** — Send large self addressed stamped envelope, or 2 stamps. Swaney, Box 54, Goose Creek, SC. 29445.

**CASH PAID** for current Motorola 2 way radios, parts & acc. also HT 100 + 220. Contact Frank DiRico, 416 Adams Street, Quincy, Massachusetts 02169. 617-542-9050.

**TELETYPEWRITER PARTS,** gears, manuals, supplies, tape, toroids. SASE list. Typetronics, Box 8873, Ft. Lauderdale, FL 33310. Buy parts, late machines.

**THE KNIGHT RAIDERS VHF CLUB'S** auction and flea market will be held on October 4th, Saturday, at St. Joseph's Church of East Rutherford, Hackensack Street, East Rutherford. Free admission, free parking, refreshments available. Talk-in will be on 146.52 and 146.94. Flea market tables: \$5.00 for a full table, \$3.00 for a half table. Reserve your tables in advance by writing to The Knight Raiders VHF Club, Inc., K2DEL, P. O. Box 1054, Passaic, New Jersey 07055.

**MANUALS** for most ham gear made 1940/65, some earlier. Send SASE for specific quote. Hobby Industry, W0JJK, Box H-864, Council Bluffs, Iowa 51501.

**AMAZING, NEW, UNIQUE, EASY,** method of mastering the Morse Code. Send \$5.95 to GENERAL, Dept. 979, Box 137, Northbridge, CA 91324.

**WANTED:** tubes, transistors, equipment, what have you? Bernard Goldstein, W2MNP, Box 257, Canal Station, New York, N. Y. 10013.

**RADIO CONTROL EQUIP.:** E-K 4 channel, on 53.5 MHz. Transmitter, 2 receivers, 2 batteries, 8 servos. A steal at \$185.00 plus shipping. J. D. Wothe, 20 N Passage, Fairport, N. Y. 14450.


**EXCLUSIVELY HAM TELETYPE** 21st year, RTTY Journal, articles, news, DX, VHF, classified ads. Sample 30¢. \$3.00 per year. Box 837, Royal Oak, Michigan 48068.

**FOR SALE:** Late 51S1 and 55G1. Also late KWM-2, 512B-4 and power supply. KH6FMT, Box 758, Koloa, HI. 96756. (808) 742-2002.

**PC's,** Send large S.A.S.E. for list. Semtronics, Rt. #3, Box 1, Bellaire, Ohio 43906.

**MANUALS** for Govt. surplus gear, only \$6.50 each: URM-25D, R-220/URR, SP-600JX, TT-63A/FGC, TS-497B/URR TS-382D/U, ALR-5, URM-32, TS-173/UR, TS-174/U, TS-175/U, BC-779B, TS-34A/AP, CV-591A/URR, TS-413A/U, SG-3/U, TS-452B/U, LM-21, PRC-10, BC-639A, LP-5, OS-8B/U, OS-8A/U, OS-8C/U, TV-2/U, OS-46/U, CV-278/GR. Immediate delivery. Thousands more in stock. Send 50¢ (coin) for 22-page catalog. W3IHD, 7218 Roanne Drive, Washington, D. C. 20021.

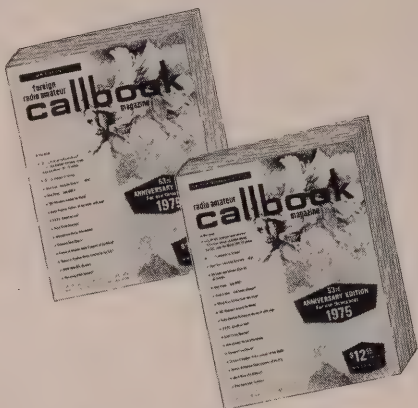**TELL YOUR FRIENDS** about Ham Radio Magazine.



There's  
nothing  
like it

## RADIO AMATEUR callbook

*Respected worldwide as  
the only complete authority  
for radio amateur  
QSL and QTH information.*

The new 1975 U. S. Callbook has nearly 300,000 W & K listings. It lists calls, license classes, names and addresses plus the many valuable back-up charts and references you come to expect from the Callbook.

Specialize in DX? Then you're looking for the new, larger than ever 1975 Foreign Callbook with almost 235,000 calls, names and addresses of amateurs outside of the USA.

**United States  
Callbook**  
All W & K Listings  
**\$12.95**  
with  
3 Service Editions  
**\$18.95**

**Foreign Radio  
Amateur Callbook**  
DX Listings  
**\$11.95**  
with  
3 Service Editions  
**\$17.95**

Order from your favorite electronics dealer or direct from the publisher. All direct orders add 75¢ shipping and handling per Callbook.

**WRITE FOR  
FREE  
BROCHURE** RADIO AMATEUR  
**callbook INC.**  
Dept. E 925 Sherwood Drive  
Lake Bluff, Ill. 60044

**"HAM BUY LINES".** Send name and address for literature. Iacopelli, 1720 77 St., Brooklyn, N. Y. 11214.

**HOME BREWERS:** Stamp brings list of high quality components. CPO Surplus, Box 189, Braintree, Mass. 02184.

**CANADIAN JUMBO SURPLUS** and Parts Catalogs. Bargains Galore. Send \$1. ETCO-HR, Box 741, Montreal "A" H3c 2V2.

**TEST EQUIPMENT:** Tektronix 545 scope \$595. H/P 608B signal generator \$295. Need R-390 recvr. E. P. Reeves, W7CHG, 1659 Wetmore, Tucson, Arizona 85705.

**CINCINNATI HAMFEST:** 38th annual — Sunday, September 21, 1975 at the New Stricker's Grove on State Route 128, one mile west of Ross (Venice), Ohio. Flea market, contests, model aircraft flying, food and beverages all day. Advanced Tickets \$7.00, covers everything; \$8.00 at gate. For tickets or further information: Carl J. Dettmar, W8NCV, 8630 Cavalier Drive, Cincinnati, Ohio 45231.

**WANTED:** Ham Radio Magazine, March & November '71, February '72, May & August '73, February & October '74, January & May '75. Will pay a fair price. Edward A. Stoltzfus, P. O. Box 73, Parkersburg, PA 19365.

**SELL** — Quality nylon cable ties 6 inch for \$2.75 pp/hundred. New Manuals for AN/ARC-3, AN/ARC-12, AN/TRC-1 for \$5.00 pp. W4VQD/Q, 106 Sheridan Ct., Leavenworth, Ks. 66048.

**SALE:** Communicator VFO, Globe VFO, HyGain 6-2 antenna, reasonable. WA2EUS, 110 Lafayette St., Copiague, N. Y. 11726.

**VERY in-ter-est-ing!** Next 5 big issues \$1. "The Ham Trader," Sycamore IL 60178

**ITALIAN STAMPS** for collection. I send you for dispatch same value of FET MOSFET IC TRANSISTOR, only by Air, registered small packet, sample, gift, no parcel post, not insured! Send to Bruni - Poste Campomiccio - I-05100 Terni - succ. 7 - Italy.

**PORTA-PAK** the accessory that makes your mobile really portable. \$59.95 and \$39.95. Dealer inquiries invited. P. O. Box 67, Somers, Wisc. 53171.

**JAPANESE TRANSISTORS** — All Transistors original factory made. Over 500 types available. Write for free catalog. West Pacific Electronics, P. O. Box 25837, W. Los Angeles, CA 90025.

**QRP TRANSMATCH** for HW7, Ten-Tec, and others. Send stamp for details to Peter Meacham Associates, 19 Loretta Road, Waltham, Mass. 02154.

**INTERNATIONAL friendship, emergency communication public service, monthly publication "World-radio",** trial subscription - two issues \$1, 2509-C Donner, Sacramento, CA 95818.

**SOCIETY OF WIRELESS PIONEERS** offers Life Membership to active and former C.W. operators on comm'l., military, gov't., etc. wireless/radio circuits. Contact: Society of Wireless Pioneers, Dept. H, P. O. Box 530, Santa Rosa, California 95402.

**FOR SALE:** Swan 250C, 6-meter transceiver with P/S speaker, remote VFO, noise blander & TV2D 2-meter transverter, mint condition. K3IPM, 215-355-2867. Stanley Smith, 133 Hogeland Rd., Southampton, Pa. 18966.

**NOW PAYING \$2000.00** and up for ARC-94/618T ARC-102/618T. \$1200.00 and up for ARC-51BX. \$1500.00 and up for 490T-1 antenna couplers. We also need these control boxes — C-6287/ARC-51BX, C-6476/ARC-51BX, C-714E-2. We also need R-1051 receivers, RT-662/GRC-106 transceivers. We buy all late aircraft and ground radio equipment. Also pack radios. We are buyers not talkers. Bring your equipment in, you are paid on the spot. Ship it in, you are paid within 24 hours. We pay all shipping charges. If you want the best price for your equipment, call us. Call collect if you have, and want to sell or trade. We also sell. What do you need? D & R Electronics, R.D. #1, Box 56, Milton, Pa. 17847. Phone — 717-742-4604 - 9:00 a.m.-9:00 p.m.

**RECIPROCATING DETECTOR,** write Peter Meacham Associates, 19 Loretta Road, Waltham, Mass. 02154.



**WANT:** Non-working R-390-A receiver, also will recalibrate the vfo from same for \$40.00 postpaid. Make it track within one KC. Want 390-A parts. W4AIS, 306 Thornwood Dr., Taylors, S. C. 29687.

**FREE BARGAIN CATALOG.** LEDs, xtals, microphones, headsets, IC's, relays, ultrasonic devices, precision trimmer capacitors, unique components. Chaney's, Box 15431, Lakewood, Colo. 80215.

**OSCAR SLIDES,** set of 5, \$1.25. Launch and spacecraft. Proceeds AMSAT. K6PGX, P. O. Box 463, Pasadena, CA 91102.

**RTTY DEMODULATORS:** ST-6, 170/425/850 shift, AK-1, Hal case, \$290; ST-5 with autostart, \$125; ST-5 with autostart, AK-1, \$170. All three new, tuned, complete; UPS prepaid 48. Fred Firestone, WB9IEE, 806 N. School St., Normal, IL 61761. 309/452-4032.

**RECONDITIONED TEST EQUIPMENT** for sale. Catalog \$50. Walter, 2697 Nickel, San Pablo, CA. 94806.

**SPRING MILL (INDIANA) HAMFEST,** Sunday, October 12, 1975 at Spring Mill State Park near Mitchell, IN. Prizes, flea market, entertainment. Write The Hoosier Hills Ham Club, P. O. Box 375, Bedford, IN 47421.

**MANUFACTURERS, Distributors!** The Memphis Hamfest will be bigger than ever. The dates are Saturday and Sunday, October 4 and 5. Best location possible — State Technical Institute, Interstate 40 at Macon Road. Security. Contact Chairman, Harry Simpson W4SCF, Box 27015, Memphis, TN 38127, phone 901 358-5707.

**CALIFORNIA QSO PARTY.** October 4 & 5, sponsored by the Northern California Contest Club. The biggest party ever — all 58 of California's counties represented, 200 different W6 stations to participate. Join us.

**MOBILE IGNITION SHIELDING** provides more range with no noise. Available most engines in assembled or kit forms, plus many other suppression accessories. Free literature. Estes Engineering, 930 Marine Dr., Port Angeles, WA. 98362.

**GREATER SYRACUSE (NEW YORK) HAMFEST,** Saturday, October 11, 1975, 9 a.m. to 6 p.m. at the Syracuse Auto Auction, 4 miles south of Syracuse on U.S. Route 11 between Nedrow and La Fayette, New York. Exhibitors, flea market, contests, speakers, forums, panels and Eyeball QSO's. Lunch counter, nearby campsite. Apple Festival for whole family. Talk in 31/91. Donation \$2.00 at door — before October 1st, \$1.50. For information contact WA2UBT, Allen Brown, 128 Atkinson Avenue, Syracuse, New York 13207.

**QSL'S — BROWNIE W3CJ1** — 3035B Lehigh, Allentown, Pa. 18103. Samples with cut catalog 35¢.

**PENNSYLVANIA QSO PARTY,** September 13 & 14, 1975. All amateurs are invited to participate. Write to the sponsors, Nittany Amateur Radio Club, P. O. Box 60, State College, Penn. 16801 for complete rules, scoring and other details.

**MEMPHIS** is beautiful in October! The Memphis Hamfest, bigger and better than ever, will be held at State Technical Institute, Interstate 40 at Macon Road, on Saturday and Sunday, October 4 and 5. Demonstrations, displays, MARS meetings, Flea Market, XYL entertainment, prizes. Informal dinners Saturday night. Dealers and Distributors welcome. Talk-in on 3980, 34-94 and MARS. Contact Harry Simpson W4SCF, Box 27015, Memphis, TN 38127 or telephone 901 358-5707.

**TEXAS — The Tidelands Amateur Radio Society's** Annual Hamfest is Sunday, October 5, 1975, 9 a.m. 'til ? at the Galveston County Park, League City. Advance registration \$1.50, \$2.00 at door. Free parking, swap booths and refreshments available. Main drawing for prizes at 3:00 p.m. for info send S.A.S.E. to Luke Sterling, 105 Seabreeze Drive, League City, Texas 77573.

**NEW CANADIAN MAGAZINE.** "Electronics Work Shop". \$5.00 yearly, sample \$1.00. ETCOB, Box 741, Montreal, H3C 2V2.

**TRAVEL-PAK QSL KIT** — Send call and 25¢; receive your call sample kit in return. Samco, Box 203, Wynantskill, N. Y. 12198.

# FREE

**DATA SHEETS  
WITH EVERY ITEM  
749 IC WITH  
EVERY \$10 ORDER\***

- REDUCE YOUR PROJECT COSTS
- MONEY-BACK GUARANTEE
- 24-HOUR SHIPMENT
- ALL TESTED AND GUARANTEED

## TRANSISTORS (NPN):

|  |          |
|--|----------|
| 2N3563 TYPE RF Amp & Osc to 1 GHz (pl.2N918)         | 6/\$1.00 |
| 2N3565 TYPE Gen. Purpose High Gain (T0-92/106)       | 6/\$1.00 |
| 2N3567 TYPE High-Current Amplifier/Sw 500 mA         | 4/\$1.00 |
| 2N3866 TYPE RF Power Amp 1.5 W @ 450 MHz             | \$1.50   |
| 2N3903 TYPE GP Amp & Sw to 100 mA and 30 MHz         | 6/\$1.00 |
| 2N3919 TYPE RF Power Amp 10-25 W @ 3-30 MHz          | \$3.00   |
| 2N4274 TYPE Ultra-High Speed Switch 12 ns            | 4/\$1.00 |
| MPS6515 TYPE High-Gain Amplifier hFE 250             | 3/\$1.00 |
| Assort. NPN GP TYPES, e.g. 2N3694, 2N3903, etc. (15) | \$2.00   |
| 2N3638 TYPE (PNP) GP Amp & Sw to 300 mA              | 4/\$1.00 |
| 2N4249 TYPE (PNP) Low-Noise Amp 1μA to 50mA          | 4/\$1.00 |

## FET's:

### N-CHANNEL (LOW-NOISE)

|  |          |
|--|----------|
| 2N4091 TYPE RF Amp & Switch (T0-18/106)              | 3/\$1.00 |
| 2N4416 TYPE RF Amplifier to 450 MHz (T0-72)          | 2/\$1.00 |
| 2N5163 TYPE Gen. Purpose Amp & Sw (T0-106)           | 3/\$1.00 |
| 2N5486 TYPE RF Amp to 450 MHz (plastic 2N4416)       | 2/\$1.00 |
| E100 TYPE Low-Cost Audio Amplifier                   | 4/\$1.00 |
| ITE4868 TYPE Ultra-Low Noise Audio Amp               | 2/\$1.00 |
| TI574 TYPE High-Speed Switch 4052                    | 3/\$1.00 |
| Assort. RF & GP FET's, e.g. 2N5163, MPF102, etc. (8) | \$2.00   |

### P-CHANNEL:

|  |          |
|--|----------|
| 2N4360 TYPE Gen. Purpose Amp & Sw (T0-106) | 3/\$1.00 |
| E175 TYPE High-speed Switch 12552 (T0-106) | 3/\$1.00 |

## SEPTEMBER SPECIALS:

|   |           |
|---|-----------|
| 1N4154 DIODE 30 V/10mA-1N914 except 30 V                | 25/\$1.00 |
| 2N2222 NPN TRANSISTOR GP Amp & Switch                   | 5/\$1.00  |
| 2N2907 PNP TRANSISTOR GP Amp & Switch                   | 5/\$1.00  |
| 2N3553 RF Power Amp 5 W @ 150 MHz, 10 W @ 50 MHz        | \$2.00    |
| 2N3904 NPN TRANSISTOR GP Amp & Switch                   | 5/\$1.00  |
| 2N3906 PNP TRANSISTOR GP Amp & Switch                   | 5/\$1.00  |
| 2N5108 RF Power Amp 2 W @ 450, 1 W @ 1 GHz              | \$2.50    |
| E101 N-CHANNEL FET Low Current, Low Vp Amp/Sw           | 3/\$1.00  |
| MPF102 N-CHANNEL FET RF Amp-200 MHz                     | 3/\$1.00  |
| 340 T 1A VOLT. REG.-Specify 5, 6, 12, 15 or 24 V-W/Ckts | \$1.75    |
| 2556 DUAL 555 TIMER 1μsec to 1 hour (DIP)               | \$1.00    |
| 8038 WAVE FORM GENERATOR □ ◀ /Wave W/Ckts               | \$4.50    |
| MM5316 DIGITAL CLOCK-Snooze/Alarm/Timer                 |           |
| Hrs, Mins, Secs, 4 or 6 Digit-With Specs/Schematics     | \$5.50    |

## LINEAR IC's:

|   |          |
|---|----------|
| 308 Micro-Power Op Amp (T0-5/MINI-DIP)            | \$1.00   |
| 309 K Voltage Regulator 5 V @ 1 A (T0-3)          | \$1.50   |
| 324 Quad 741 Op Amp, Compensated (DIP)            | \$1.75   |
| 380 2.5 Watt Audio Amplifier 34 dB (DIP)          | \$1.29   |
| 555X Timer 1 μs-1 hr. Dif. pinout from 555 (DIP)  | \$ .85   |
| 709 Popular Op Amp (DIP/T0-5)                     | \$ .29   |
| 723 Voltage Regulator 3-30 V @ 1-250mA (DIP/T0-5) | \$ .58   |
| 739 Dual Low-Noise Audio Preamp/Op Amp (DIP)      | \$1.00   |
| 1458 Dual 741 Op Amp (MINI-DIP)                   | \$ .65   |
| 741 Freq. Comp. OP AMP (DIP/T0-5/MINI-DIP)        | 3/\$1.00 |

## DIODES:

|   |           |
|---|-----------|
| ZENERS—400mW, Specify Voltage 3.3, 3.9, 4.3, 5.1, 6.8, 8.2, 9.1, 10, 12, 15, 18, 22, 24, 27 or 33V (±10%) | 4/\$1.00  |
| 1N3600 TYPE Hi-Speed Sw 75 V/200 mA   | 6/\$1.00  |
| 1N3893 TYPE RECTIFIER Stud Mount 400 V/12 A   | 2/\$1.00  |
| 1N914 or 1N4148 TYPE Gen. Purp. 100V/10mA   | 15/\$1.00 |
| D5 VARACTOR 5-50 W Output @ 30-250 MHz, 7-70 pF   | \$5.00    |
| F7 VARACTOR 1-3 W Output @ 100-500 MHz, 5-30 pF   | \$1.00    |

\*MAIL NOW! FREE DATA SHEETS supplied with every item from this ad. FREE ON REQUEST—749 Dual Op Amp (\$1.00 value) with every order of \$10 or more, postmarked prior to 10/30/75.

**ORDER TODAY**—All items subject to prior sale and prices subject to change without notice. All items are new surplus parts — 100% functionally tested.

**WRITE FOR FREE CATALOG** offering hundreds of semiconductors not listed here. Send 10¢ stamp.

**TERMS:** All orders must be prepaid. We pay postage. \$1.00 handling charge on orders under \$10. Calif. residents add 6% sales tax. Foreign orders — add postage. COD orders — add \$1.00 service charge.

# ADVA

ELECTRONICS  
BOX 4181 AS, WOODSIDE, CA 94062  
Tel. (415) 851-0455



## Hale Electronics Brings You . . .

### REPEATER ID'er



**MODEL IDC-100**

- All solid state fully automatic repeater identifier and ID control mtd on 3" x 6" PC board
- Includes CW ID memory, interval timer, hvy duty xmitter-hold switch, tone generator, CW speed and audio level controls.
- Unique activity sensing circuit allows ID only at end of transmission - no ID over conversation
- Requires 5vdc @ 200 ma, regulated
- Wired, tested and programmed

**\$46.50**

### CG-256 RTTY/CW Generator



Directly compatible with ST-6 in either RTTY or CW mode. (Photo shows CG-256-R which includes reed relay.)  
CG-256 Kit (open collector/TTL output) \$23.50  
With Reed Relay, add \$3.00; Wired & Tested, add \$8.45  
Board with Programmed Memory & Manual \$16.50  
Write for more details & spec. sheet.

Call/write for details on reg. pwr. supply kit & HP-2A Preamp for 2 mtrs (\$9.95 kit, \$13.95 wired & tested).  
(Mo. res. add 4% sales tax) Prices ppd US & Canada

## Hale Electronics

P. O. Box 682 — Cape Girardeau, Mo. 63701  
Tel. 314-334-0420

## CFP ENTERPRISES

IS

**MOVING**

We're gearing up to serve you better than ever with new facilities and new hours. **Jim Beckett, WA2KTJ**, is back to staff this new operation and is looking forward to meeting you.

Contact us now for service aimed at solving your radio equipment needs. We'll continue to bring you our present lines and back them up with service facilities.

**Opening date** is expected to be **September 2!**

## CFP Communications

Division of CFP Enterprises  
211 NORTH MAIN STREET  
HORSEHEADS, NEW YORK 14845

Phone: 607-533-4297  
607-739-0187

**WANTED:** November 1970 HAM RADIO to complete my collection. Write Richard Rosen, 420 Riverside Drive, Apt. 12D, New York, N. Y. 10025.

**COMING TO FLORIDA?** Use our Club station or your own rig and our all-band antennas to work DX or your home town. All hams welcome. Details — H. E. Saxton, W4QED, c/o Spanish River Inn, Delray Beach, Fla. 33444.

**PACK RAT HAMARAMA**, Sunday October 5 at Bucks County Drive-In Theater located on Rt. 611 in Warrington, PA, (near exit 27 of Penn. Turnpike and north of Willow Grove, PA). Sponsored by the Mt. Airy Radio Club. For further information and flier with map — SASE to K3MXM — Lee A. Cohen, 8242 Brookside Road, Elkins Park, PA 19117.

**DO-IT-URSELF DXPEDITION** — Stay at ZF1SB — Cayman Is. Vertical antenna and Caribbean at your doorstep. Diving/fishing if band folds. Write Spanish Bay Reef Resort, Box 800K, Grand Cayman, B. W. I.

**FISHER SCIENTIFIC CO.** and Subsidiaries is attempting to compile a roster of Ham's that are employed by them. If you are employed by them, of a subsidiary, please contact Fred Shetler, K3VMS at the Instrument Manufacturing Division, Indiana, Pa. 15701. We are interested in your handle, call, position held, and address of home QTH.

**160 METER TOP LOADING SECTIONS** for vertical antennas, \$34.50 ppd. 80 meter sections, \$31.50 ppd. Details write Bill Turney, WAØRFF, 1414 East 9th, Hutchinson, Kansas 67501.

**CLEVELAND'S LARGEST ELECTRONIC HAMFEST** and Flea Market will be held Saturday, September 27th, at the Cuyahoga County Fairgrounds in Berea. Easy access from Hopkins Airport, Interstate I-71, I-90, and the Ohio Turnpike. Listen for the Buckeye Belles or Chix and "Talk In" from the East on 146.76, South on 82, West on .88, and locally on .52 and .94. Eastcars, Midcars on 40 and 80 M and 52.525 for farther out. Tickets \$1.50 before Sept. 24th — \$2.00 at 8:00 when gates open. Flea market parking earlier — bring your own tables. For early tickets and information on motels and camp grounds, send a check and S.A.S.E. to: Cleveland Hamfest Association, Box 43413, Cleveland, Ohio 44143.

**HAM RADIO** has all the license manuals you need! Write for details.

**BUY—SELL—TRADE.** Write for monthly mailer. Give name, address, call letters. Complete stock of major brands. New and reconditioned equipment. Call us for best deals, we buy Collins, Drake, Swan, etc. SSB & FM. Associated Radio, 8012 Conser, Overland Park, Ks. 66204. 913-381-5901.

**FERRITE BEADS:** Ferroxcube beads w/specification and application sheet — 10 @ \$1.00 postpaid. Includes latest catalog. CPO Surplus, Box 189, Braintree, Mass. 02184.

**MOTORHOME FOR SALE.** 25 ft. Sportscoach (RB) 1973, excellent condition, many extras. Antennas - 2 mtr, TV, (2) HF - 4 KW generators, sleeps six. \$1,500 down, assume loan. Send SASE for more info. W6KHS, 212 Magellan St., Capitola, CA 95010.

**QUANNAPOWITT RADIO ASSOCIATION** annual auction, greatest and oldest in N. E., Saturday, October 4th, St. Joseph's Parish Hall, Wakefield, Mass., 10 A.M. - 4 P.M., doors open 9 A.M., 10% commission, no minimum. Door prizes, special prizes. Talk-in 146.52.

**SB-104 OWNERS CLUB** — Covers related Heathkit equipments. Send SASE for details to Chuck Harrison, RD 2, Box 1, Main Street, North Stonington, CT 06359.

**HT220 HI-BAND**, 4 freq. universal \$250.00. D. M. Herlihy, 2338 Berry St., Lemon Grove, Cal. 92045.

**1N5231B ZENER** 5.1v 10/\$1.00 1N4007 .11 ea., Resistors 1/4W 5% .04 ea. FREE CATALOG. Orders below \$8.00 add \$.50 Postage. NuData Electronics, 104 N. Emerson St., Mt. Prospect, Ill. 60056.

**YOUR AD belongs here too.** Commercial ads 35¢ per word. Non-commercial ads 10¢ per word. Commercial advertisers write for special discounts for standing ads not changed each month.

# BULLET ELECTRONICS

## MINI POWER SUPPLY KIT

Build your own +5 volt power Module at a fraction of commercial cost!

+5 volt regulated @ 400 MA with overload protection low ripple for TTL work!

**4.95**  
Complete

- Drilled & Plated Board
- All Components
- Complete Instructions
- Transformer

## LOUD!

### 10 WATT WARBLE ALARM KIT

All the components you need to build a dual tone warble alarm but the speaker.

NO PC BOARD NEEDED **\$2.00**

### 10.7 MHZ CERAMIC FILTER

**\$1.69**



Miniature Size  
No Tuning Required

3DB Bandwidth: 220 KHZ  
50DB Bandwidth: 700 KHZ (Max)  
Insertion Loss : 10 DB (Max)  
Impedance : 330 ohms


The bandwidth can be narrowed by loading filter with a higher impedance

## RCA CA3043 GREEN PHOSPHOR READOUT

High Gain, IF AMP,  
FM Detector Limiter,  
AF Pre Amp

99¢ with Specs

2N3055 69¢  
2N4443 69¢  
400V 8A SCR

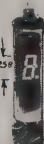

1.4V Filament  
24V segment  
Low Current  
(40 ma per readout)  
DG8F  
79¢ each

10 for \$7.00

- 48 HOUR MAIL SERVICE
- CASH REFUNDS ON OUT-OF-STOCK ITEMS

- QUALITY PARTS — NO JUNK!
- COMPLETE SATISFACTION OR MONEY BACK

## POWER SUPPLY SPECIAL

We brought a large quantity of parts to make a quality power supply for TTL & linear work.




+5V 1.5A  
±15V 150 ma  
1% regulation  
low ripple

- YOU GET:
- Drilled & Plated Board
  - All components including transformer
  - Complete instructions

**12.95**

## 60HZ CRYSTAL TIME BASE KIT

Use with mos clock chips requiring 60HZ

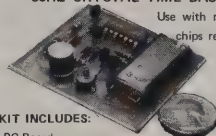

**\$9.95**

## KIT INCLUDES:

- PC Board
- 7.68kc xtal
- Transistors, resistors, etc.
- Mos binary divider

for 12 Volt operation

## HEATshrink TUBING

### 1 FOOT CUT LENGTHS


assorted sizes: 1/4, 1/8

& 1/16 **PACK of 10**  
**49¢**

CMOS Decade Counter/  
7 Seg. Decoder

CD4033  
14 Pin Dip Limited Qty  
**\$1.95 each**
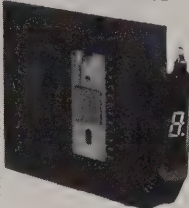
## UNIVERSAL BCD UP/DOWN COUNTING MODULE WITH LATCH



Low Current  
Actual size  
2"x 2-3/8"

+12vps Required  
+24vdc

**4.95**  
6 for \$25


- Drilled & Plated PC Board
- MOS Counting Chip
- .25 inch Character Phosphor Readout
- Presettable +N Counting to 1MHZ
- Up or Down Counting
- Board fits standard edge connectors
- Complete Instructions
- Application & Project notes
- Units can be Cascaded

Send 25¢ for Catalog • POSTAGE PAID ON ALL  
FREE WITH ORDER ORDERS OVER \$5.00

**BULLET ELECTRONICS**  
P. O. BOX 1465  
LAKE WORTH, FLORIDA  
33460

NO C.O.D.'S  
CHECK OR MONEY ORDER  
INCLUDE 50¢ for handling on all orders less than \$5.00.

## FREQUENCY STANDARD

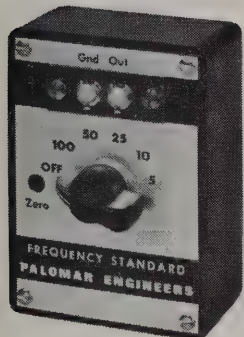


*Only*  
**\$37.50**  
(less batteries)  
POSTPAID USA

- Precision crystal
- Fully guaranteed

- Markers at 100, 50, 25, 10 or 5 kHz selected by front panel switch.
- Zero adjust sets to WWV. Exclusive circuit suppresses unwanted markers.
- Compact rugged design. Attractive, completely self contained.
- Send for free brochure.

**PALOMAR ENGINEERS**

BOX 455, ESCONDIDO, CA 92025

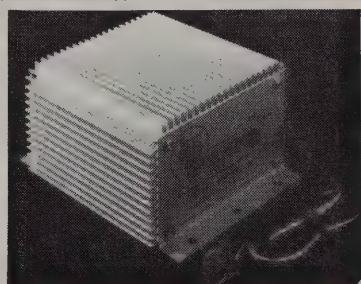

## THE TIGER

### 15% Savings on Gas

A Capacitive Discharge Ignition system absolutely guaranteed **NOT** to interfere with your radios & equally guaranteed to improve your auto's operation and gas mileage.


No rewiring necessary. Engine cannot be damaged by improper installation. Either of three models fits any vehicle or stationary engine with 12 volt negative ground, alternator or generator system. Uses standard coil & distributor now on your engine. Dual switch permits motor work or tune-up with any standard test equipment.

Write for free booklet that not only is the BEST description of CDIs, but also explains the need for such a system. Current prices assured til Jan. '76.

## D-D ENTERPRISES

P.O. Box 7776  
San Francisco, CA 94119



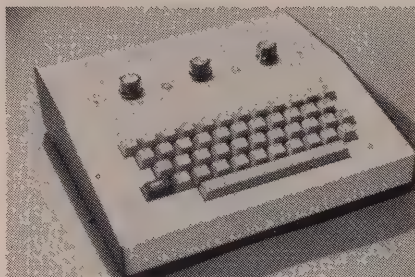

## INFO-TECH MORSE KEYBOARD

### FEATURES:

- VARIABLE SPEEDS FROM 8 TO 35 WPM
- ADJUSTABLE WEIGHT
- 64 CHARACTER RUNNING MEMORY WITH BUFFER FULL INDICATOR
- BOTH GRID BLOCK AND CATHODE KEYING
- ADJUSTABLE GAIN SIDE TONE MONITOR
- CAN STORE 64 CHARACTERS FOR DELAYED TRANSMISSION
- INCLUDES THE FOLLOWING SPECIAL KEYS: BK, BT, AR, SK, CQ AND DE
- 'N' KEY ROLLOVER TO AVOID MISSED CHARACTERS
- FULL ONE YEAR WARRANTY . . .

AND BEST OF ALL . . . ONLY \$239.50

Delivered in the Cont. USA

SEND FOR DATA SHEET FOR ADDITIONAL INFORMATION  
WATCH FOR INFO-TECH'S NEW FAMILY OF DIGITAL  
SYSTEMS . . . COMING SOON . . .

RTTY KEYBOARD, RTTY TO VIDEO DISPLAY,  
AND MORSE TO VIDEO DISPLAY.

## INFO-TECH

P. O. BOX 84  
CHESTERFIELD, MO. 63017

## THE ULTRA-BAL 2000


NOW -----An extremely rugged, weather-proof BALUN!

- Full 2KW, 3-30 MHz., 1:1 or 1:4 ratios.
- Special Teflon insulation. May be used with tuned lines and tuners.
- With dipole insulator and hang-up hook.

ONLY \$9.95ppd.(state ratio)

At your dealer or order direct

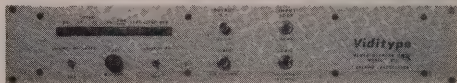**K.E. Electronics** Box 1279, Tustin Calif. 92680



## RTTY VIDEO DISPLAY UNIT

1000 CHARACTERS - ANY TV SET

**VIDITYPE**

MODEL 872 \$550

WRITE FOR BROCHURE

## LELAND ASSOCIATES

18704 GLASTONBURY RD.  
DETROIT, MI. 48219

## VHF/UHF

Ten meters through 432 MHz. A post card will bring our full 1974 Catalog.



**JANEL laboratories**

260 NW POLK AVE.  
CORVALLIS, OREGON 97330  
Telephone: 503-757-1134

## CONVERTERS PREAMS



- STABILITY
- HIGH QUALITY
- QUICK DELIVERY

Write or Call


## R/T LABS., INC.

4126 COLERAIN AVE., CINCINNATI, OHIO 45223  
513/681-3444
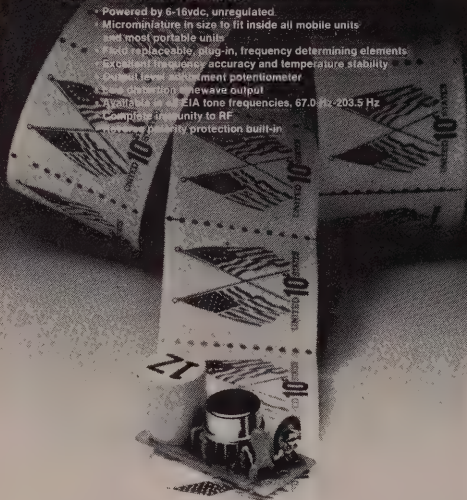
## ME-3 microminiature tone encoder

Compatible with all sub-audible tone systems such as: Private Line, Channel Guard, Quiet Channel, etc.

- Powered by 6-16Vdc, unregulated.
- Microminiature in size to fit inside all mobile units and most portable units.
- Field replaceable, plug-in, frequency determining elements.
- Excellent frequency accuracy and temperature stability.
- Output level adjustable potentiometer.
- Tone distortion less than 0.5%.
- Available in 4 EIA tone frequencies, 67.0 Hz, 203.5 Hz.
- Complete immunity to RF.
- Shock and vibration protection built-in.



\$29.95 each

Wired and tested, complete with K-1 element

**communications specialists**

P. O. BOX 183  
BREA, CALIFORNIA 92621  
(714) 998-3021

K-1 FIELD REPLACEABLE,  
PLUG-IN, FREQUENCY  
DETERMINING ELEMENTS  
\$3.00 each

# Webster

radio

Everything from Set to Signal!

2602 E. Ashlan, Dept. H  
Fresno, Calif. 93726  
(209) 224-5111

FREE gift! Just for  
writing for your free  
YAESU catalog.



FT101E Yaesu \$749.00  
with New Speech Processor

## • NEW! SILVERPLATE • NEW!

- SINGLE SOLUTION • NO MIXING • NO FUSS • NO LETHAL CHEMICALS • FAST ACTING ON COPPER • BRASS • BRONZE • BRUSH ON OR DIP • RINSE AND DRY • IDEAL FOR THOSE COMPLICATED JOBS • 6 LIQUID OZ. BOTTLE SILVERPLATES UP TO 1800 SQUARE INCHES OF METAL • \$7.00

• ABAR RESEARCH •

11118 PARKER STREET, MOKENA, IL. 60448

## CASH FOR 2-WAY FM RADIO

MOTOROLA, GE, RCA, ETC. EQUIPMENT  
MOBILES, BASES, PORTABLES, MOBILE-TELEPHONES  
REPEATERS, REMOTE CONTROLS, TONE EQUIPMENT

2-WAY TEST EQUIPMENT

Operational Units Only  
Commissions/Finders Fees  
**CAL-COM SYSTEMS, INC.**

701-51A KINGS ROW, SAN JOSE, CALIFORNIA 95112  
Telephone 24 Hours 408/998-4444



# VANGUARD NOW HAS THE WORLD'S LARGEST SELECTION OF FREQUENCY SYNTHESIZERS FROM \$129.95

*You'll never  
have to buy Crystals  
again!*



**AVAILABLE FOR  
AIRCRAFT, FIRE, POLICE  
AND AMATEUR FREQUENCIES**

## Check these features:

- Smallest size of any commercially available synthesizer — only 1-3/8" x 3-3/4" x 7".
- Excellent spectral purity since no mixers are used.
- .0005% (5 parts per million) accuracy over the temperature range of -10 to +60 C.
- Immune from supply line voltage fluctuations when operated from 11 to 16 volts D.C.
- Up to 8000 channels available from one unit. Frequency selected with thumbwheel switches.
- Available from 5 MHz to 169.995 MHz with up to 40 MHz tuning range and a choice of 1, 5 or 10 kHz increments (subject to certain restrictions depending on the frequency band selected).
- Top quality components used throughout and all ICs mounted in sockets for easy servicing.
- All synthesizers are supplied with connecting hardware and impedance converters or buffers that plug into your crystal socket.

SEND NO MONEY.  
WE SHIP C.O.D.  
ORDER BY PHONE  
AND SAVE TIME.

*We ship open account only to U.S. and Canadian government agencies, universities and selected AAA rated corporations.*

Vanguard frequency synthesizers are custom programmed to your requirements in 1 day from stock units starting as low as \$129.95 for transmit synthesizers and \$139.95 for receive synthesizers. Add \$20.00 for any synthesizer for 5 kHz steps instead of 10 kHz steps and add \$10.00 for any tuning range over 10 MHz. Maximum tuning range available is 40 MHz but cannot be programmed over 159.995 MHz on transmit or 169.995 MHz on receive (except on special orders) unless the I-F is greater than 10.7 MHz and uses low side injection. Tuning range in all cases must be in decades starting with 0 (i.e. — 140.000 — 149.995 etc.). The output frequency can be matched to any crystal formula. Just give us the crystal formula (available from your instruction manual) and we'll do the rest. We may require a deposit for odd-ball formulas. On pick-up orders please call first so we can have your unit ready.

## VANGUARD LABS

Call 212-468-2720 between 9:00 am and 4:00 pm  
Monday through Friday  
196-23 JAMAICA AVE. HOLLIS, N. Y. 11423

# SAROC

Amateur Radio's  
Prestige Convention

Hotel Sahara  
Las Vegas

Special Air Fares  
from selected cities

**SAROC**  
Box 945  
89005

## JANUARY 8-11, 1976


## DYCOMM for RF POWER



ECHO III REPEATER



MODEL 34 WATTMETER

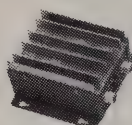

A4950



A8949

### A COMPLETE LINE OF FM AMPLIFIERS model — power output — gain — price

#### 6 METER FM

A4950 - 50W - 10db - \$183.  
A4960 - 50W - 8db - \$192.  
A8949 - 100W - 10db - \$270.  
450 - UHF

#### 2 METER FM

MODEL C - 25W - 4db - \$69.  
MODEL D - 50W - 7db - \$99.  
SUPER D KIT - 80W - 3.5db - \$60.  
MODEL DS - 80W - 3.5db - \$139.  
MODEL E - 35W - 10db - \$80.  
SUPER E KIT - 40W - 11db - \$60.  
MODEL ES - 40W - 11db - \$115.  
10-0 - 100W - 7db - \$209.  
1-10-0 - 100W - 14db - \$226.  
35-0 - 100W - 4db - \$185.

OTHER PRODUCTS  
ECHO III FM REPEATER - \$949.  
MODEL 34 WATTMETER - \$70.




**DYNAMIC**

**COMMUNICATIONS**

948 AVE. "E" P.O. BOX 10116  
RIVIERA BEACH, FLA. 33404  
(305) 844-1323



## More Details? CHECK-OFF Page 110

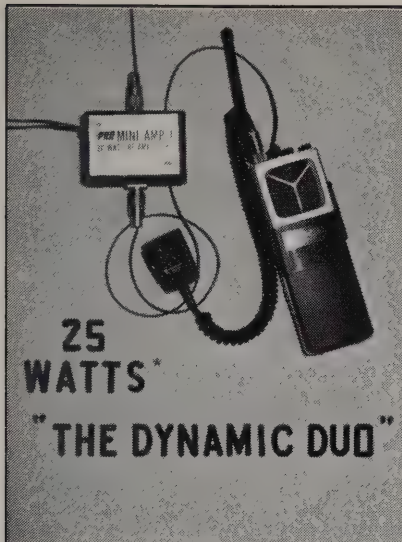

## WELCOME TO THE WORLD OF VHF VERSATILITY!

The MINI-AMP I expands the versatility of your handi talki or low-power rig to equal that of a good mobile/base rig. Look at the advantages this kit offers:

1. Low cost/watt — **\$49.95** plus postage (12 oz.)
2. Interfaces with any rig from **100mW** to 3 watts+
3. Can be used on motorcycles, in boats, planes, cars, campers, or anywhere where 12 volts DC is available.
4. Super compact — only 3" x 4" x 2".
5. Light weight — only 12 oz. Easily concealed in car or boat to reduce the possibility of theft.

If you are constantly worried about your mobile rig being stolen, conceal our Mini-Amp I under your dash, seat, etc. and use your handi-talki for maximum portability and security.

These are just some of the reasons that we feel our Mini-Amp I is the most practical and versatile amplifier on the market. For answers to any further questions, you may call our toll free number, 800-453-5717. I will be happy to help you.

*Terrell F. Bird*  
WA7VRM

**PRA**  
INDUSTRIES

COMMUNICATIONS  
DIVISION

2285 SOUTH MAIN ST., SUITE 1  
SALT LAKE CITY, UTAH 84115



20 WATTS/12VDC  
25 WATTS/13.5VDC

P. S. Watch for 100 Watt amplifier coming soon.

## REPEATER IDENTIFIER

*Specifically designed  
for rigorous environments*

### FEATURES

Wide temp tolerance:  $-40^{\circ}\text{F}$  to  $+185^{\circ}\text{F}$   
Maximum reliability: high noise immunity of CMOS IC's. Rugged transistor switch. Code speed & ID interval factory set with fixed resistor

Minimum power requirement: 100  $\mu\text{A}$  standby & 2MA while identifying.  
Voltage from 5V to 15V DC

Adaptability: 125 bit diode matrix can be reprogrammed by user

Conservatively priced at **\$95.00**. Only \$80.00 less cabinet. PPD

TRI-LINE CO. Tel: (714) 564-4185  
Box 8, La Quinta, Ca 92253

Enclosed is \$.....Please send ID-2A  
with/without cabinet


Call Letters .....

Name .....

Address .....

City/State/Zip .....

## — CLEAN SIGNAL — — ALL CHANNELS —

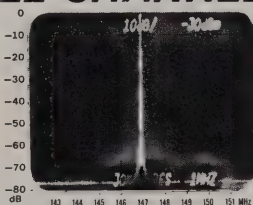

Actual Spectrum Analyzer Photograph  
of an RP Synthesized Radio

ONLY RP GIVES YOU BOTH  
PLUS

- SUPER ACCURACY (.0005%)
- FULL 2M FM COVERAGE

144-148 MHz

WORKS WITH MOST FINE AMATEUR  
OR COMMERCIAL GRADE RADIOS

## MFA-22 SYNTHESIZER

SEND FOR  
FULL DETAILS


**R<sub>p</sub> Electronics**

810 DENNISON DRIVE  
BOX 1201  
CHAMPAIGN, IL 61820  
Phone: 217-352-7343





## INTERNATIONAL MORSE DECODER

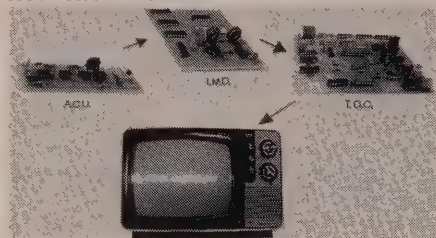

### International Morse Decoder

International Morse Code IN  
Parallel ASCII OUT

**\$73**

### Television Display Circuit

ASCII IN; Display a single row of up to 30 characters on your TV screen; No connection to TV set required.

**\$118**

### Audio Converter Unit

Couple your receiver to the International Morse Decoder; Two stage active filter plus level detector; Can also be used to drive an audio oscillator for static free CW reception

**\$19**

The above circuit boards are shipped assembled and tested



PIÑON  
ELECTRONICS

P. O. BOX 2192

MESA, ARIZONA 85204

## WE'RE FIGHTING INFLATION NO PRICE RISE IN '75

### FOR FREQUENCY STABILITY

Depend on JAN Crystals. Our large stock of quartz crystal materials and components assures Fast Delivery from us!

### CRYSTAL SPECIALS

#### Frequency Standards

100 KHz (HC 13/U).....\$4.50

1000 KHz (HC 6/U).....4.50

Almost all CB sets, TR or Rec.....\$2.50  
(CB Synthesizer Crystal on request)

Amateur Band in FT-243.....ea. \$1.50  
.....4/\$5.00

80-Meter.....\$3.00 (160-meter not avail.)

Crystals for 2-Meter, Marine, Scanners, etc. Send for Catalog.

For 1st class mail, add 20¢ per crystal. For Airmail, add 25¢. Send check or money order. No dealers, please.



Div. of Bob Whan & Son Electronics, Inc.  
2400 Crystal Dr., Ft. Myers, Fla. 33901  
All Phones: (813) 936-2397

Send 10¢ for new catalog with 12 oscillator circuits and lists of frequencies in stock.



Aha, the SECRET of PC Board success finally revealed. A perfectly balanced lighting tool combining magnification with cool fluorescence. Excellent for fine detail, component assembly, etc. Lens is precision ground and polished.

Regularly \$67.00. Now, over 30% discount (only **\$46.00**) to all licensed Hams, verified in Callbook. Uses T-9 bulb (not supplied).

Include \$3.00 U.S. postage, or \$4.00 in Canada. \$5.00 elsewhere. California Residents include 6% sales tax.

Or send stamped envelope for free brochure of other incandescent or fluorescent lamps suitable for all engineers, architects, students, etc.

## D-D ENTERPRISES

DEPT. A, P.O. BOX 7776  
SAN FRANCISCO, CA 94119

## NOW THE ONLY NATIONAL AMATEUR RADIO NEWSLETTER WITH THE LATEST ...

- FROM
- FCC
  - ARRL
  - INDUSTRY
  - PROPAGATION
  - CONTESTS
  - DX

ISSUE\*

AFTER ISSUE

AFTER ISSUE!

\*52 issues  
per year

A four page, instant  
newsletter in the mail  
when it happens, not  
weeks later

1 year \$12.00 US, Canada & Mexico — \$15.00 Worldwide

**hr REPORT**  
GREENVILLE, NH 03046

## Drake In stock for immediate shipment.

|  |          |
|--|----------|
| R4-C Receiver .....                        | \$549.00 |
| SPR-4 Solid State Gen. Cov. Receiver ..... | \$599.00 |
| T-4XC Transmitter .....                    | \$580.00 |
| MS-4 Speaker .....                         | \$24.95  |
| AC-4 Power Supply .....                    | \$120.00 |
| WV-4 Wattmeter 20-200 MHz .....            | \$74.00  |

Globalman EK-108D Electronic Keyer, wired, complete with paddle. .... \$74.95  
Collins phone patches, removed from equipment, nice condition with schematic ..... \$24.95  
Collins 516-F2 A.C. Power Supply — Used, good cond., lab tested O.K. .... \$110.00

**ANTENNAS — TA-36, TH6-DXX, in stock, write or call.**

|  |         |
|--|---------|
| Savoy DGA-2M, 2 meter collinear .....  | \$29.95 |
| Trunk lip bracket for DGA-2M .....   | \$14.95 |
| HyGain 1/4 wave 2M grd plane .....   | \$13.00 |
| Hustler 4, BTW Vertical Antenna .....  | \$79.95 |
| HyGain 18V 10-80 m. vertical .....   | \$33.00 |
| HyGain BN86 Deluxe Balun .....   | \$15.95 |
| HyGain 18 AVT/WB 10-80 meters vertical .....   | \$97.00 |
| Newtronics CGT-144 5.2 dB gain, Trunk lip mount .....  | \$39.95 |
| Newtronics G6-144A fixed station antenna 6dB gain .....                                      | \$52.00 |
| Gold Line Single Pole, 5 position coaxial switch, wall bracket or panel mount, 1 KW AM ..... | \$17.95 |
| Times Wire & Cable, T-4-50, RG-8 foam .....  | 28¢/ft. |

**Bird** We are official distributors for Bird Wattmeters and elements.

## C.D. Ham II Rotator

**New Improved** \$159.95 net **SAVE \$20 \$139.95**

8 conductor cable for HAM II or CD-44 16¢/ft.

|   |             |
|---|-------------|
| IC-230 — Call or write .....  | \$489.00    |
| Johnson small matchbox, Millen KW Transmatch. Astatic D-104 Mike .....                                    | new \$26.10 |
| Astatic UG-8 Stand for D-104 .....  | new \$19.95 |
| B & W 850A or 852 for PiNet Band switching inductor for .....   | \$66.75     |
| B & W 334A Dummy Load-Wattmeter 0-300MHz 52Ω, 0-10, 100, 300, 1000 watts .....                            | \$149.95    |
| B & W 374 Dummy Load-Wattmeter 0-300MHz, 52Ω 0-15, 50, 300, 1500 watts .....                              | \$175.00    |
| Sockets for 8072, 8121, 8122 .....  | \$3.95      |
| EBG Jr-2 meter FM synthesized XCVR .....  | \$599.00    |
| MC Jones Mod. 575.5 Micro Match SWR bridge, N Connectors. Use with 200 μa meter. New value \$100.00 ..... | \$24.95     |
| Kenwood TS-520 .....  | \$629.00    |

## New Arrivals!

Ameco 2 and 6 Meter Xmitter TX-62  
Heathkit SB600, SB610, SB630.  
RME — VHF-126  
Standard, Base Station, SR-C14, 22 Channel, 2 Meter FM, 10 watts

## New Item!

DX Engineering Speech Compressor for Collins 32S xmtr \$98.50; for Collins KWM2 \$98.50; for Drake TR4(C) \$128.50.

## New Item!

**SOLID PORCELAIN INSULATORS** newly arrived! With coax use as center insulator — open wire feed — can be used with homemade RG8 Balun — Handles up to 5 KW input. Furnished with instructions ..... \$3.00

Johnson 154-10 or equal. Single section 23 thru 347 pF for KW transmatch. Replaces Millen 16520 ..... \$35.00  
Johnson 229-202 18 mH variable inductor 10 to 80M for KW transmatch ..... \$35.00  
Johnson 229-203 28 mH variable inductor 10 to 160M for KW transmatch ..... \$37.00  
B & W Minductors - Air-Dux coil stock

Stocking TEN-TEC — Fast Availability!

**VENUS** Finest SSTV, Latest Models, SS-2, SLOW SCAN MONITOR KIT ..... \$269.00

**C1, FAST SCAN/SLOW SCAN CAMERA & CONVERTER** ..... \$469.00

**We have VIBROPLEX in stock!**

Gold-Line In line Wattmeter — 144-162 MHz, 0-50W., 50Ω ..... \$17.50  
Gold-Line Matcher-reflected Power Meter, 144-220 MHz, 100W. .... \$35.00

## NPC POWER SUPPLIES

|  |         |
|--|---------|
| 115 VAC Input - 12 VDC 4 amps out .....  | \$29.95 |
| Same as above but regulated .....  | \$47.95 |
| Model 108R — 115 VAC/13.6 VDC 8 amps continuous 12 amps surge. Regulated ..... | \$69.95 |

**CONSTANT VOLTAGE TRANSFORMER.** Input 115 VAC @ 60Hz output, 24V @ 15 amps with matching AC capacitor ..... \$19.95  
Hammarlund Dual Section 320/320 per section Xmit'g Capacitor ..... \$29.95  
Tubes for worldwide and domestic, commercial service. Large stocks of meters and capacitors.  
ITC 2000 FM, SSB & CW Synthesized 2 meter transceiver ..... \$695.00  
R-389 Receiver. 15-1500 kcs, mechanical digital readout, motorized tuning ..... \$375.00  
Ameco Model PT Preamp, factory wired ..... \$69.95  
Regency HR-6 6 mtr FM transcvr, new cnd \$199  
Heath Warrior HA-10 Amplifier with 4 811A's and power supply ..... \$185.00  
Swan 700-CX with matching 117XC power supply and speaker, plus WM-1500 Wattmeter. All mint, like new ..... \$650.00  
Realistic DX-160 Solid-State General Coverage Receiver with SP-150, like new ..... \$120.00

Recently received! 2500 meters. What do you need? Lots of other goodies.

## Barry Extra

Strain-axial antenna connector for all

SBE Linear Systems Slow Scan TV Monitor, Model SBI-MTV & SBE Slow Scan TV Camera, Model SBI-CTV. Orig. boxes — both mint condition — Write or call.

**BARRY BUYS UNUSED TUBES AND VACUUM CAPACITORS.** Send Your List. Tube Headquarters. Diversified Stock. Heavy inventory of Eimac tubes, chimneys, sockets, etc. 3-500Z or 3-400Z Specify \$50.00.

**BARRY** 512 Broadway NY, NY 10012

DEPT. H-9 **ELECTRONICS**

212 WA-5-7000

TELEX 12-7670

Add shipping-excess refunded-Quoted FOB N.Y.C.

September Hours

Saturday, 10 a.m. - 2 p.m.

Monday-Friday, 9 a.m. - 6:30 p.m.

## WN1USO

JOHN YOUNG

8460 North River Road  
Mesa, Arizona 80950

## AMATEUR RADIO CALL LABELS

HAM IT UP with these Combination Call and Address Labels — Black Print on Silver Foil — 1" x 1 1/2". These Deluxe Self-Stick Labels add your personal touch to the Amateur Radio Field — Up to four 22 character lines plus Call Letters.

300 Labels \$4.75 ppd

500 Labels \$6.25 ppd

SKANDIA, INC., Dept. 7Y  
Londonderry, N. H. 03053

Call Letters .....

Name .....

Address .....

City .....

State .....

Zip .....

# Advertisers check-off

... for literature, in a hurry —  
we'll rush your name to the companies  
whose names you "check-off"

Place your check mark in the space between  
name and number. Ex: Ham Radio ☒ 234

## INDEX

|                    |     |                          |     |
|--------------------|-----|--------------------------|-----|
| Abar               | 325 | K-Enterprises            | 071 |
| Adva               | 265 | K. E.                    | 072 |
| Aldelco            | 347 | KLM                      | 073 |
| Antenna Mart       | 009 | Kenwood                  | 341 |
| Atlas              | 198 | Kolar                    | 334 |
| Barry *            |     | Larsen                   | 078 |
| Budwig             | 233 | Leland                   | 193 |
| Bullet             | 328 | Levy                     | 291 |
| Buyers & Sellers   | 329 | MFJ                      | 082 |
| CFP                | 022 | Matric                   | 084 |
| Cal-Com            | 282 | M-Tech                   | 357 |
| Clegg              | 027 | Nashoba Valley Hamfest * |     |
| Continental        |     | National                 |     |
| Specialties        | 348 | Semiconductor            | 323 |
| Comm. Spec.        | 330 | N. E. Digital            | 336 |
| Corbin             | 349 | Northshore               |     |
| Curtis             | 034 | RF Technology            | 296 |
| Cush Craft         | 035 | Optoelectronics          | 352 |
| D-D                | 269 | PRA Industries           | 316 |
| Dames              | 324 | Pagel                    | 092 |
| Data               | 277 | Palomar                  | 093 |
| Data Signal        | 270 | Pinon                    | 337 |
| Davis              | 332 | Police Call Mag.         | 199 |
| Dentron            | 259 | Poly Paks                | 096 |
| Digital Tech.      | 350 | Porta-Pak                | 274 |
| Drake              | 039 | RMS                      | 239 |
| Dycomm             | 040 | RP                       | 098 |
| E S Ent.           | 208 | R/T Labs                 | 358 |
| Ehrhorn            | 042 | Radio Engineering        |     |
| Eimac              | 043 | Service                  | 353 |
| Electronic Dist.   | 044 | Callbook                 | 100 |
| Elect. Equip. Bank | 288 | Radio King               | 354 |
| ELPROCON           | 301 | Regency                  | 102 |
| Epsilon            | 046 | SAROC                    | 146 |
| Fair               | 048 | Savoy                    | 105 |
| Fred Franke        | 289 | Skandia                  | 338 |
| Genave             | 168 | Southwest Tech.          | 263 |
| HR Report          | 150 | Space Electronics        | 107 |
| Hal                | 057 | Specialty Comm.          |     |
| Hale               | 302 | Systems                  | 318 |
| Halstead Press     | 308 | Spectronics, FM          | 191 |
| Ham Radio          | 150 | Spectrum                 | 108 |
| Hamtronics         | 246 | Summit                   | 339 |
| Heath              | 060 | Swan                     | 111 |
| Heights            | 061 | Teco                     | 113 |
| Henry              | 062 | Topeka FM                | 115 |
| Hewlett Packard    | 281 | Tri-Line                 | 355 |
| Hy-Gain            | 064 | Tri-Ex                   | 116 |
| ITT,               |     | Tufts                    | 321 |
| Mackay Marine      | 184 | Unibit                   | 356 |
| Icom               | 065 | VHF Engineering          | 121 |
| Info-Tech          | 351 | Valu-Pak                 | 264 |
| International      |     | Vanguard                 | 346 |
| Crystal            | 066 | Webster                  | 255 |
| James              | 333 | Weinschenker             | 122 |
| Jan                | 067 | Wilson                   | 123 |
| Janel              | 068 | Yaesu                    | 127 |

\*Please contact this advertiser directly

Limit 15 inquiries per request.

## September 1975

Please use before October 31, 1975

Tear off and mail to  
**HAM RADIO MAGAZINE — "check off"**  
Greenville, N. H. 03048

NAME.....  
STREET.....  
CITY.....  
STATE.....ZIP.....


CALL.....

# Advertisers iNdex

|                                     |            |
|-------------------------------------|------------|
| Abar Research                       | 104        |
| Adva Electronics                    | 101        |
| Aldelco                             | 106        |
| Antenna Mart                        | 88         |
| Atlas Radio Co.                     | 15         |
| Barry                               | 109        |
| Budwig Manufacturing Co.            | 106        |
| Bullet                              | 103        |
| Buyers & Sellers                    | 92         |
| CFP Communications                  | 102        |
| Cal-Com Systems, Inc.               | 104        |
| Clegg Division of ISC               | 27         |
| Continental Specialties Corp.       | 80, 81     |
| Communications Specialists          | 104        |
| Cush Craft                          | Cover II   |
| D-D Enterprises                     | 103, 108   |
| Dames, Ted                          | 97         |
| Data Corp.                          | 92         |
| Data Signal, Inc.                   | 65, 72     |
| Davis Electronics                   | 96         |
| Dentron Radio Co.                   | 56, 57     |
| Digital Techniques                  | 106        |
| Drake Co., R. L.                    | 83         |
| Dycomm                              | 105        |
| E S Enterprises                     | 71         |
| Ehrhorn Technological Operations    |            |
| Eimac, Div. of Varian Assoc.        | Cover IV   |
| Electronic Distributors             | 97         |
| Electronic Equipment Bank, Inc.     | 88         |
| ELPROCON                            | 95         |
| Epsilon Records                     | 86         |
| Fair Radio Sales                    | 90         |
| Fred Franke, Inc.                   | 86         |
| General Aviation                    | 91         |
| HR Report                           | 108        |
| Hal Communications Corp.            | 2          |
| Hale Electronics                    | 102        |
| Ham Radio                           | 106        |
| Hamtronics, Inc.                    | 90         |
| Heaths Company                      | 76, 77     |
| Heights Manufacturing Co.           | 73         |
| Henry Radio Stores                  | Cover III  |
| Hy-Gain Electronics Corp.           | 111        |
| ITT, Mackay Marine                  | 85         |
| Icom                                | 5          |
| Info-Tech                           | 104        |
| International Crystal Mfg. Co. Inc. | 53         |
| James Electronics                   | 78, 79, 95 |
| Jan Crystals                        | 108        |
| Janel Labs                          | 104        |
| K-Enterprises                       | 84         |
| K. E. Electronics                   | 104        |
| KLM Electronics                     | 87         |
| Kenwood Communications Inc.         | 112        |
| Kolar, Inc.                         | 94         |
| Larsen Electronics                  | 70         |
| Leland Associates                   | 104        |
| Levy Associates                     | 90         |
| MFJ Enterprises                     | 43         |
| Matric                              | 94         |
| M-Tech                              | 106        |
| Nashoba Valley Hamfest              | 92         |
| New England Digital Electronics     | 96         |
| Northshore RF Technology            | 88         |
| Optoelectronics                     | 88         |
| PRA Industries                      | 107        |
| Palomar Engineers                   | 84, 103    |
| Pinon Electronics                   | 108        |
| Police Call Magazine                | 84         |
| Poly Paks                           | 98         |
| Porta-Pak                           | 94         |
| RMS Corporation                     | 92         |
| RP Electronics                      | 107        |
| R/T Labs, Inc.                      | 104        |
| Radio Amateur Engineering Service   | 95         |
| Radio Amateur Callbook, Inc.        | 92, 100    |
| Radio King                          | 90         |
| Regency Electronics, Inc.           | 75         |
| SAROC                               | 105        |
| Savoy Electronics                   | 86         |
| Skandia, Inc.                       | 109        |
| Southwest Technical Products        | 74         |
| Space Electronics Corp.             | 95         |
| Specialty Communications Systems    | 96         |
| Spectronics, FM                     | 89, 94     |
| Spectrum                            | 82         |
| Summit Enterprises                  | 96         |
| Swan Electronics                    | 7, 93      |
| Teco/Tucker Electronics             | 69         |
| Topeka FM Communications            | 97         |
| Tri-Line Co.                        | 107        |
| Tri-Ex Tower Corp.                  | 21         |
| Tufts Radio Electronics             | 86         |
| VHF Engineering, Div. of            |            |
| Brownian Elect. Corp.               | 47         |
| Valu-Pak                            | 96         |
| Vanguard Labs                       | 105        |
| Webster Radio                       | 104        |
| Weinschenker                        | 106        |
| Wilson Electronics                  | 61         |
| Yaesu Musen USA                     | 35, 106    |


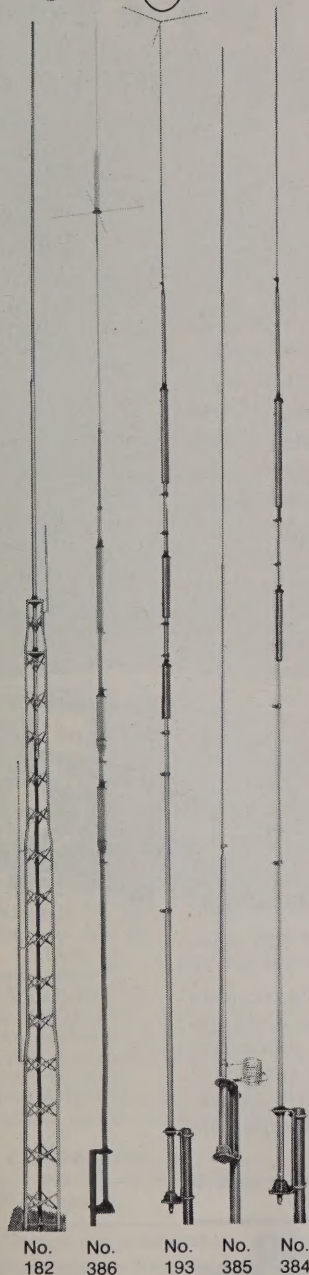
# No room? Get a ###hy-gain vertical antenna!



Even if you're limited to just a few square feet of real estate, you've got room for a high performance Hy-Gain multi-band vertical. Great coverage in minimum ground space, or roof mount for optimum performance using Hy-Gain 12RMQ or 14RMQ Roof Mount/Radial Kit. All these antennas are entirely self-supporting.

## 18HT Hy-Tower 6 thru 80 meters

Unquestionably the finest multi-band omnidirectional vertical antenna available. Entire structure is radiating element with automatic band switching. All hardware iridited. Unique stub decoupling for 50 ohm input on all bands. Also operates 160 meters with loading coil. Takes maximum legal power with ease. No roof mount. Ht. 50'. Wt. 100 lbs.

**Order No. 182**

## 18AVT/WB 10 thru 80 meters

True  $\frac{1}{4}$  wave resonance on all bands, automatic band switching and optimum wide-band performance combine to make the 18AVT/WB one of the most popular amateur antennas. Three heavy duty Hy-Q Traps, top loading coil, extra heavy duty construction. Roof mount with 14RMQ. Ht. 25'. Wt. 10.7 lbs.

**Order No. 386**

## 18V 10 thru 80 meters

Low cost, high efficiency, and quality construction make the 18V ideal for budget-conscious HAMs. Easily tuned to any 10-80 meter band by adjusting feed point at base inductor. Highly portable. Roof mount with 14RMQ. Ht. 18'. Wt. 4.6 lbs.

**Order No. 193**

## 14AVQ/WB 10 thru 40 meters

Improved for even greater wide-band performance! Three separate Hy-Q Traps with oversize coils for extremely high Q.  $\frac{1}{4}$  wave resonance on all bands. Outstanding low angle radiation pattern. Roof mount with 14RMQ. Ht. 18'. Wt. 8.6 lbs.

**Order No. 385**

## 12AVQ 10, 15 and 20 meters

Inexpensive tri-band vertical for performance with minimum investment in space and equipment. Low radiation angle. Roof mount with 12RMQ. Ht. 13'6". Wt. 6.8 lbs.

**Order No. 384**

For prices and information, contact your local Hy-Gain distributor or write Hy-Gain.

###hy-gain

Hy-Gain Electronics Corporation; 8601 Northeast Highway Six; Lincoln, NE 68507; 402/464-9151; Telex 48-6424.  
Branch Office and Warehouse; 6100 Sepulveda Blvd., #322; Van Nuys, CA 91401; 213/785-4532; Telex 65-1359.  
Distributed in Canada by Lectron Radio Sales, Ltd.; 211 Hunter Street West; Peterborough, Ontario.

# KENWOOD

...Why settle  
for less!

There are several good transceivers on the market today. But if you compare them carefully... study the specifications, note the important features, and finally talk to some Kenwood owners, you will have to come to the same conclusion that thousands of others have come to... you can't buy a better rig for the money than a Kenwood. Every unit is built with pride and designed to give top performance year after year. Join the switch to Kenwood.



The TS-520 shown  
with the VFO-520 and SP-520

The TS-520 is the final word in SSB transceivers... the "hottest little rig on the air." It is a compact, mostly solid state, all-in-one transceiver with built-in AC/DC power supply and speaker. It operates SSB and CW on 80 thru 10 meters. Features include 2-position ALC and double split frequency controlled operation.

Available at select Kenwood dealers throughout the U.S.

Distributed by




**TRIO-KENWOOD  
COMMUNICATIONS INC.**

116 East Alondra / Gardena, California 90248



# the new look of a proven performer

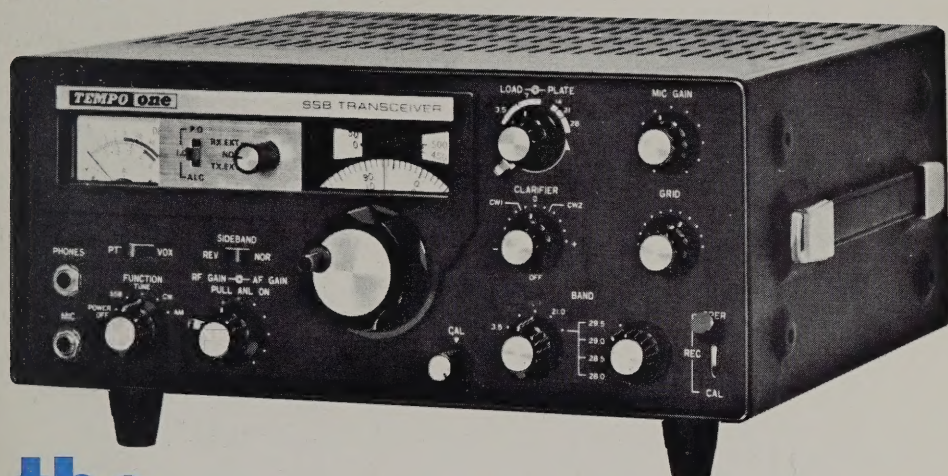

## the tempo 'ONE' SSB TRANSCEIVER

*... a proven name, a proven value. Look at the specifications, look at the price tag, ask any of the thousands of Tempo ONE owners about its reliability... and the reason for its unparalleled popularity will be obvious.*

### SPECIFICATIONS

**FREQUENCY RANGE:** All amateur bands 80 through 10 meters, in five 500 khz. ranges: 3.5-4 mhz., 7-7.5 mhz., 14-14.5 mhz., 21-21.5 mhz., 28.5-29 mhz. (Crystals optionally available for ranges 28-28.5, 29-29.5, 29.5-30 mhz.)

**SOLID STATE VFO:** Very stable Colpitts circuit with transistor buffer provides linear tuning over the range 5-5.5 mhz. A passband filter at output is tuned to pass the 5-5.5 mhz. range.

**RECEIVER OFFSET TUNING (CLARIFIER):** Provides  $\pm 5$  khz. variation of receiver tuning when switched ON.

**DIAL CALIBRATION:** Vernier scale marked with one kilohertz divisions. Main tuning dial calibrated 0-500 with 50 khz. points.

The Tempo line is available  
at select dealers throughout the U.S.

**FREQUENCY STABILITY:** Less than 100 cycles after warm-up, and less than 100 cycles for plus or minus 10% line voltage change.

**Modes of Operation:** SSB upper and lower sideband, CW and AM.

**INPUT POWER:** 300 watts PEP, 240 watts CW

**ANTENNA IMPEDANCE:** 50-75 ohms

**CARRIER SUPPRESSION:** -40 dB or better

**SIDE BAND SUPPRESSION:** -50 dB at 1000 CPS

**THIRD ORDER INTERMODULATION PRODUCTS:** -30 dB (PEP)

**AF BANDWIDTH:** 300-2700 cps

**RECEIVER SENSITIVITY:**  $1/2 \mu\text{v}$  input S/N 10 dB

**AGC:** Fast attack slow decay for SSB and CW.

**SELECTIVITY:** 2.3 khz. (-6 dB), 4 khz. (-60 dB)

**IMAGE REJECTION:** More than 50 dB.

**AUDIO OUTPUT:** 1 watt at 10% distortion.

**AUDIO OUTPUT IMPEDANCE:** 8 ohms and 600 ohms

**POWER SUPPLY:** Separate AC or DC required. See AC "ONE" and DC "ONE" below.

**TUBES AND SEMICONDUCTORS:** 16 tubes, 15 diodes, 7 transistors

TEMPO "ONE" TRANSCEIVER \$399.00

AC/ONE POWER SUPPLY

117/230 volt 50/60 cycle... \$99.00

DC/1-A POWER SUPPLY 12 volts DC \$120.00

Prices subject to change without notice.

## Henry Radio

11240 W. Olympic Blvd., Los Angeles, Calif. 90064  
931 N. Euclid, Anaheim, Calif. 92801  
Butler, Missouri 64730

213/477-6701  
714/772-9200  
816/679-3127





# **EIMAC has powered communications via this satellite for 30 years.**

The first moonbounce signal was heard nearly 30 years ago when the U.S. Signal Corps Engineering Laboratory (under the direction of W4ERI, the Project Officer) received echoes from the moon on 111.5 MHz. A pair of EIMAC 1000Ts, driven by EIMAC 450THs, were used in the transmitter. The first radio amateur EME (Earth-Moon-Earth) echoes were received by W4AO and W3GKP twenty-five years ago. Again, EIMAC was there.

The first two-way moonbounce QSO took place 15 years ago between W6HB and W1BU. EIMAC klystrons were used at both stations. From these early, controlled experiments, EME communication quickly grew as interested VHF operators turned to this new and exciting mode of communication.

Today, aided by EIMAC tubes, moonbounce QSO's are commonplace on the 144 MHz and 430 MHz bands using CW and SSB modes. On 2 meters, for example, W6PO has worked 7 countries and 28 states via moonbounce using an EIMAC 8877 in his transmitter. On 432 MHz, VE7BBG has worked 5 continents using two EIMAC 4CX250Bs.

VHF moonbounce is here! Interested? Send your QSL card for EIMAC's Amateur Service Bulletin AS-49 and get the latest information on this fascinating mode of communication. EIMAC, Division of Varian, 301 Industrial Way, San Carlos, California 94070. (415) 592-1221.

Photo courtesy of NASA

